




Retiming

Shao-Yi Chien

Introduction (1/2)

■ Retiming

 - A transformation technique used to **change the locations of delay elements** in circuit without affecting the input/output characteristics







Introduction (2/2)

- Applications of retiming
 - Reducing the clock period
 - Reducing the number of registers
 - Reducing the power consumption
 - Logic synthesis

Reducing the Clock Period

 


 Critical path= $3u.t.$
 Min. clock period= $3u.t.$




Critical path= $2u.t.$
 Min. clock period= $2u.t.$

Reducing the Number of Registers

 

Number of registers: 4

 


Number of registers: 5



Reducing the Power Consumption

 - Placing registers at the inputs of nodes with large capacitances can reduce the switching activities at these nodes





Quantitative Description of Retiming


- Map circuit $G \rightarrow G_r$
- Retiming can be presented with $r(V)$, V is one of the nodes in the circuit

- For an edge $U \xrightarrow{e} V$


$$w_r(e) = w(e) + r(V) - r(U)$$

- $w(e)$: weight (delay) of the edge e in the origin circuit
- $w_r(e)$: weight of the edge e in the retimed circuit

An Example (1/2)

 

Origin DFG

 

Retimed DFG with

$$r(1)=0$$


$$r(2)=1$$

$$r(3)=0$$


$$r(4)=0$$

An Example (2/2)
 
$$\begin{aligned} 2 \rightarrow 1 &: 1 + r(1) - r(2) \geq 0 \\ 1 \rightarrow 3 &: 1 + r(3) - r(1) \geq 0 \\ 3 \rightarrow 2 &: 0 + r(2) - r(3) \geq 0 \\ 4 \rightarrow 2 &: 0 + r(2) - r(4) \geq 0 \\ 1 \xrightarrow{(1)} 4 &: 2 + r(4) - r(1) \geq 0 \end{aligned}$$



$$w_r(e) \geq 0 \quad \forall e \in G$$

 

$$\begin{aligned} w_r(2 \xrightarrow{e} 1) &= w(2 \xrightarrow{e} 1) + r(1) - r(2) \\ &= 1 + 0 - 1 = 0 \end{aligned}$$

- A retiming solution is feasible if

$$w_r(e) \geq 0 \quad \forall e \in G$$



Properties of Retiming (1/2)

- The weight of the retimed path

$p = V_0 \xrightarrow{e_0} V_1 \xrightarrow{e_1} \dots \xrightarrow{e_{k-1}} V_k$ is given by

$$w_r(p) = w(p) + r(V_k) - r(V_0)$$

□ Prof:

$$\begin{aligned} w_r(p) &= \sum_{i=0}^{k-1} w_r(e_i) \\ &= \sum_{i=0}^{k-1} (w(e_i) + r(V_{i+1}) - r(V_i)) \\ &= \sum_{i=0}^{k-1} w(e_i) + \left(\sum_{i=0}^{k-1} r(V_{i+1}) - \sum_{i=0}^{k-1} r(V_i) \right) \\ &= w(p) + r(V_k) - r(V_0). \end{aligned}$$



Properties of Retiming (2/2)

- Retiming does not change the number of delays in a cycle
- Retiming does not alter the iteration bound in a DFG
- Adding the constant value j to the retiming value of each node does not change the mapping from G to G_r

$$w_r(e) = w(e) + (r(V) + j) - (r(U) + j) = w(e) + r(V) - r(U).$$

Solving Systems of Inequalities (1/3)

- Given a set of M equalities in N variables, use **shortest path algorithm** to solve the results

Solving Systems of Inequalities (2/3)

- Step 1: draw a constraint graph
 - Draw the node i for each of the N variables r_i , $i=1,2,\dots,N$
 - Draw the node $N+1$
 - For each inequality $r_i - r_j \leq k$, draw the edge $j \rightarrow i$ from the node j to node i with length k
 - For each node i , $i=1,2,\dots,n$, draw the edge $N+1 \rightarrow i$ from the node $N+1$ to the node i with length 0



Solving Systems of Inequalities (3/3)

- Step 2: solve using a shortest path algorithm
 - The system of inequalities has a solution if and only if the constraint graph contains no negative cycles
 - If a solution exists, one solution is where r_i is the minimum-length path from the node $N+1$ to the node i

Example


$$r_1 - r_2 \leq 0$$

$$r_3 - r_1 \leq 5$$

$$r_4 - r_1 \leq 4$$

$$r_4 - r_3 \leq -1$$

$$r_3 - r_2 \leq 2.$$

 

Bellman-Ford shortest path algorithm:

$$\mathbf{R}^{(6)} = \begin{bmatrix} \infty & \infty & 5 & 4 & \infty \\ 0 & \infty & 2 & 1 & \infty \\ \infty & \infty & \infty & -1 & \infty \\ \infty & \infty & \infty & \infty & \infty \\ \boxed{0} & \boxed{0} & \boxed{0} & \boxed{-1} & \infty \end{bmatrix}$$



$$r_1=0, r_2=0, r_3=0, r_4=-1$$



Retiming Techniques


- Cutset retiming and pipelining
- Retiming for clock period minimization
- Retiming for register minimization



Cutset Retiming

- A special case of retiming that only affects the weights of the edges in the cutset
- For the disconnected subgraph $G1$ and $G2$
 - Adding k delays to each edge from $G1$ to $G2$
 - Removing k delays from each edge from $G2$ to $G1$

An Example of Cutset Retiming

 



Feasibility of Cutset Retiming

- For each edge from G1 to G2

$$w_r(e_{1,2}) \geq 0 \Rightarrow w(e_{1,2}) + k \geq 0$$


- For each edge from G2 to G1

$$w_r(e_{2,1}) \geq 0 \Rightarrow w(e_{2,1}) - k \geq 0$$

$$- \min_{G_1 \xrightarrow{e} G_2} \{w(e)\} \leq k \leq \min_{G_2 \xrightarrow{e} G_1} \{w(e)\}$$



Special Case of Cutset

Retiming: Single Node Cutset

 

- Choose a node as a cutset
- Subtract one delay from each edge outgoing from the node
- Add one delay from each edge incident into the node

 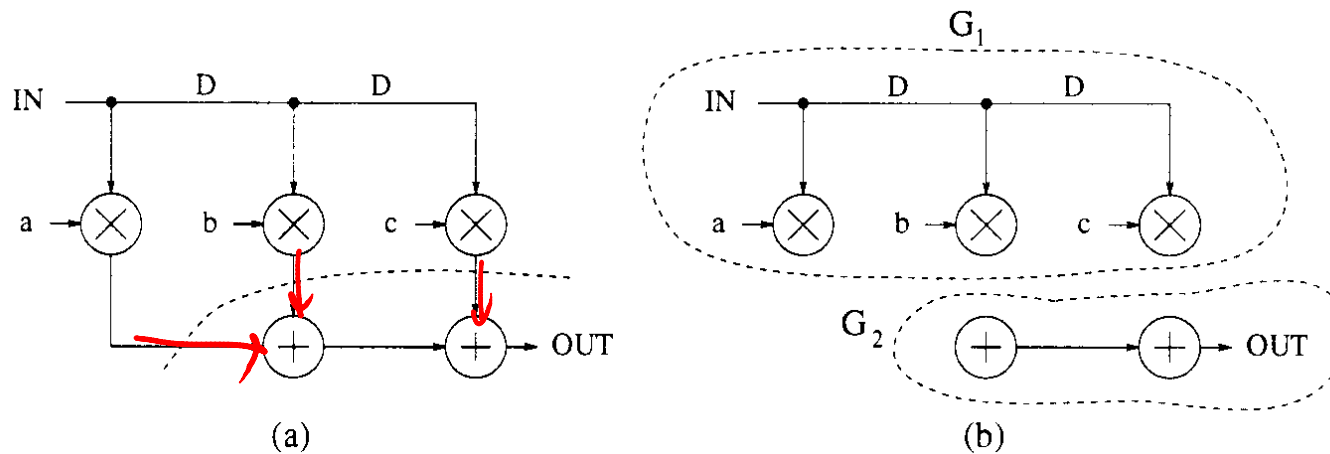Special Case of Cutset Retiming: Pipelining




$K=2$




Special Case: Combining with Slow-Down (1/2)

- Create N-slow version of the DFG first
 - Replace each delay element with N delays
- In an N-slow system, N-1 null operations (or 0 samples) must be interleaved after each useful signal sample to preserve the functionality

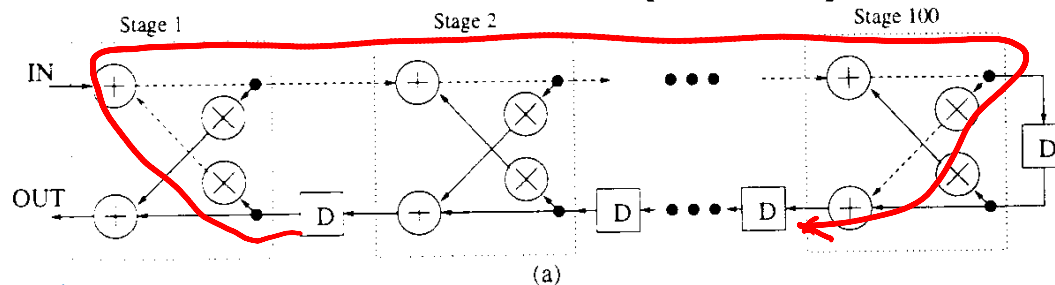
Special Case: Combining with Slow-Down (2/2)



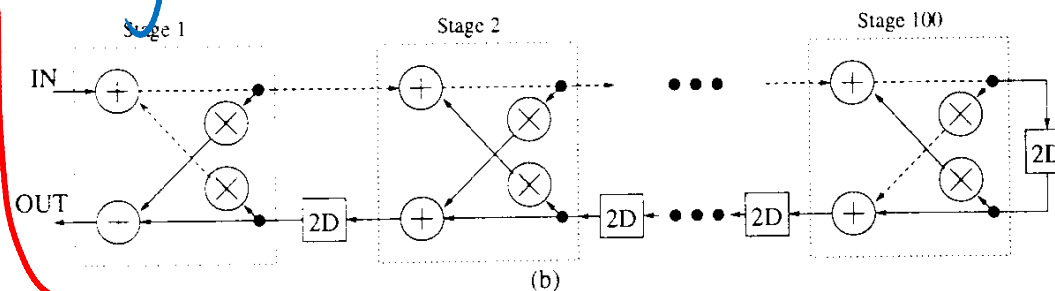Assume addition: 1 u.t.,
multiplication: 2 u.t.
Critical path is 105 u.t.
Minimum sample period
is 105 u.t.



2-slow version

 

Retimed version. The
critical path is 6 u.t. The
minimum sample period
is 12 u.t.

x₀

interleaving

x₀

x₁

x₁

x₂


x₂

x₃

x₃

 Example: Reduce the Critical Path of a Recursive DFG

- For the IIR filter $y(n+1)=ay(n)+bu(n)$
 $T_M=3u.t.$, $T_A=1u.t.$



- Critical path=?
- Iteration bound=?
- Can we reduce the sampling period to $2u.t.$?


Example: Reduce the Critical Path of a Recursive DFG

■ Employ **look-ahead transformation**

□ Consider more than one iterations


$$\begin{aligned}\square y(n+2) &= ay(n+1) + bu(n+1) \\ &= a[ay(n)+bu(n)] + bu(n+1) \\ &= a^2y(n)+abu(n)+bu(n+1)\end{aligned}$$

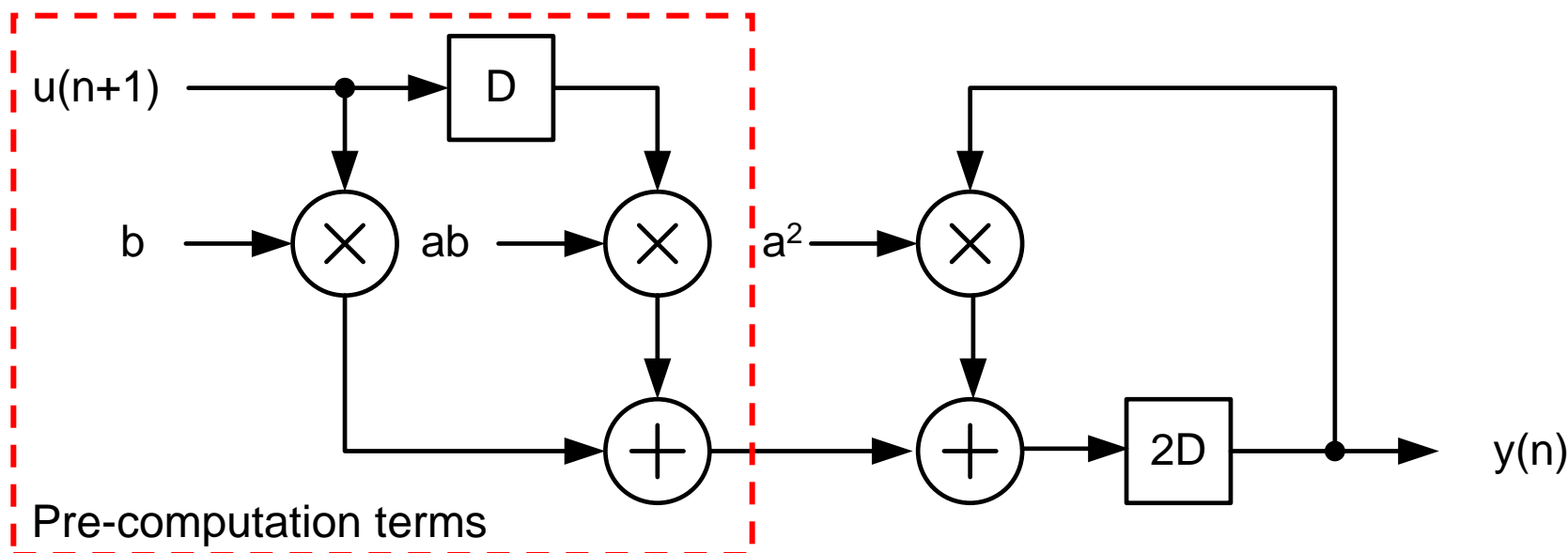Example: Reduce the Critical Path of a Recursive DFG



- Critical path=?
- Iteration bound=?
- Can we reduce the sampling period to $2u.t.$?

Remarks

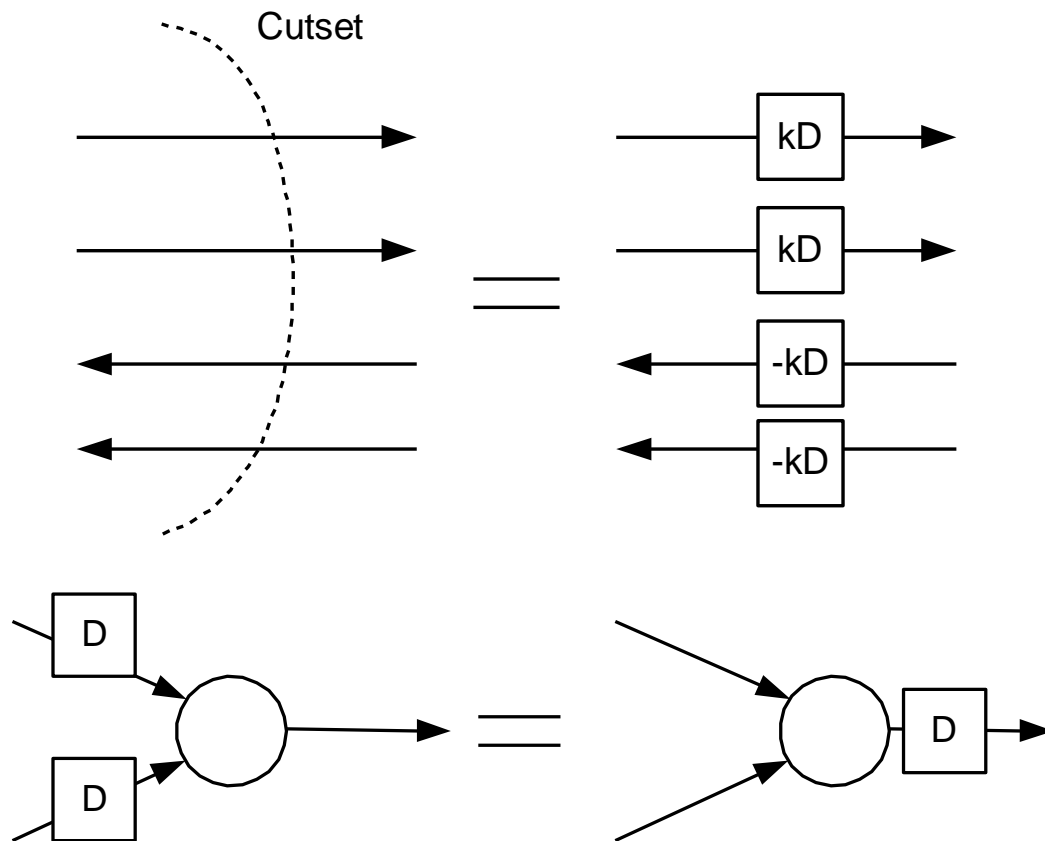




Retiming for Clock Period Minimization (1/7)

- Minimum feasible clock period or critical path

$$\Phi(G) = \max\{t(p) : w(p) = 0\}.$$

 

- Define two quantities, $U \rightarrow V$

- Minimum number of registers of $U \rightarrow V$

$$W(U, V) = \min\{w(p) : U \xrightarrow{p} V\}$$

- Maximum computation time of $U \rightarrow V$

$$D(U, V) = \max\{t(p) : U \xrightarrow{p} V \text{ and } w(p) = W(U, V)\}$$



Retiming for Clock Period Minimization (2/7)

$$S_{uv}' = \min \{ \sum w'(e) \}$$

$$= \min \{ \sum (Mw(e) - t(u)) \}$$

Method to compute $W(U, V)$ and $D(U, V)$

1. Let $M = t_{max}n$, where t_{max} is the maximum computation time of the nodes in G and n is the number of nodes in G .
2. Form a new graph G' which is the same as G except the edge weights are replaced by $w'(e) = Mw(e) - t(U)$ for all edges $U \xrightarrow{e} V$.

3. Solve the all-pairs shortest path problem on G' . Let S'_{UV} be the shortest path from U to V .


$$\left[\frac{S_{uv}}{M} \right] = \left[\frac{\sum (Mw(e) - t(u))}{M} \right] = \left[\sum (w(e) - \frac{t(u)}{M}) \right] = \left[\sum w(e) - \frac{\sum t(u)}{M} \right]$$

4. If $U \neq V$, then $W(U, V) = \left[\frac{S'_{UV}}{M} \right]$ and $D(U, V) = MW(U, V) - S'_{UV} + t(V)$. If $U = V$, then $W(U, V) = 0$ and $D(U, V) = t(U)$.

$$= \sum w(e)$$

Retiming for Clock Period Minimization (3/7)


$$M = t_{max} \cdot n = 2 \cdot 4 = 8$$

 

G

$$Mw(e) - t(u)$$

$$8 \times 2 - 1 = 15$$

 

G'




Retiming for Clock Period Minimization (4/7)

$$W(U, V) = \left\lceil \frac{S'_{UV}}{M} \right\rceil$$

S'_{UV}	1	2	3	4	$W(U, V)$	1	2	3	4
1	12	5	7	15	1	0	1	1	2
2	7	12	14	22	2	1	0	2	3
3	5	-2	12	20	3	1	0	0	3
4	5	-2	12	20	4	1	0	2	0
 
$$\left\lceil \frac{15}{8} \right\rceil = 2$$



$D(U, V)$	1	2	3	4
1	1	4	3	3
2	2	1	4	4
3	4	3	2	0
4	4	3	6	2

$D(U, V)$
 $= M W(U, V) - S'_{UV} + t(V)$

$$\left\lceil \frac{20}{8} \right\rceil = 3$$

$$8 \times 2 - 15 + 2 = 3$$

$$8 \times 3 - 20 + 2 = 6$$



Retiming for Clock Period Minimization (5/7)

■ Constraints

If the desired clock period is c

- $w_r(e) \geq 0$
1. (feasibility constraint) $r(U) - r(V) \leq w(e)$ for every edge $U \xrightarrow{e} V$ of G .
and
 2. (critical path constraint) $r(U) - r(V) \leq W(U, V) - 1$ for all vertices U, V in G such that $D(U, V) > c$.



$$W(U, V) + r(V) - r(U) \geq 1$$



Retiming for Clock Period Minimization (6/7)

■ If $c=3$

$$\begin{aligned}
 r(1) - r(3) &\leq 1 \\
 r(1) - r(4) &\leq 2 \\
 r(2) - r(1) &\leq 1 \\
 r(3) - r(2) &\leq 0 \\
 r(4) - r(2) &\leq 0,
 \end{aligned}$$

Feasibility constraints

$$\begin{aligned}
 r(1) - r(2) &\leq 0 \\
 r(2) - r(3) &\leq 1 \\
 r(2) - r(4) &\leq 2 \\
 r(3) - r(1) &\leq 0 \\
 r(3) - r(4) &\leq 2 \\
 r(4) - r(1) &\leq 0 \\
 r(4) - r(3) &\leq 1.
 \end{aligned}$$

Critical path constraints

$c = 2 ?$


$r(1) - r(3) \leq 0$

$r(1) - r(4) \leq 1$

$r(3) - r(2) \leq -1$

$r(4) - r(2) \leq -1$

 Retiming for Clock Period Minimization (7/7)





Constraint graph



$$r(1)=r(2)=r(3)=r(4)=0$$

How about $c=2$?

Retiming for Register Minimization (1/2)

  

$$R_V = \max_{V \rightarrow e} \{w_r(e)\}$$

Ex: $R_U=7$

$$COST = \sum R_V$$



Retiming for Register Minimization (2/2)

■ Minimize $COST = \sum R_V$ subject to

1. (fanout constraint) $R_V \geq w_r(e)$ for all V and all edges $V \xrightarrow{e} ?$.
2. (feasibility constraint) $r(U) - r(V) \leq w(e)$ for every edge $U \xrightarrow{e} V$.
3. (clock period constraint) $r(U) - r(V) \leq W(U, V) - 1$ for all vertices U, V such that $D(U, V) > c$.