



# Folding


Shao-Yi Chien



# Introduction

- Folding transform is used to systematically determine the control circuits in DSP architectures where multiple algorithm operations are **time-multiplexed** to a single functional unit
  - Trading area for time in a DSP architecture
  - Reducing the number of hardware functional units by a factor of  $N$  at the expense of increasing the computation time by a factor of  $N$


# An Example of Folding

 

Scheduling

Cycle	Adder Input (left)	Adder Input (top)	System Output
0	$a(0)$	$b(0)$	—
1	$a(0) + b(0)$	$c(0)$	—
2	$a(1)$	$b(1)$	$a(0) + b(0) + c(0)$
3	$a(1) + b(1)$	$c(1)$	—
4	$a(2)$	$b(2)$	$a(1) + b(1) + c(1)$
5	$a(2) + b(2)$	$c(2)$	—

# Folding Transform

 

$$D_F(U \xrightarrow{e} V) = [N(l + w(e)) + v] - [Nl + P_U + u] = Nw(e) - P_U + v - u$$

- (1)  $U$  is executed in  $H_U$  and  $V$  is executed in  $H_V$
- (2) Data leave  $H_U$  at  $Nl+u$ , and reach  $H_V$  at  $Nl+v$
- (3)  $H_U$  is pipelined by  $P_U$  stages




# Folding Transform

## ■ Folding set

- Ex: a folding set  $S_1 = \{A_1, \phi, A_2\}$  for  $N=3$  for a functional unit means  $A_1$  is executed at time  $3l+0$  ( $S_1|0$ ), and  $A_2$  is executed at time  $3l+2$  ( $S_1|2$ )
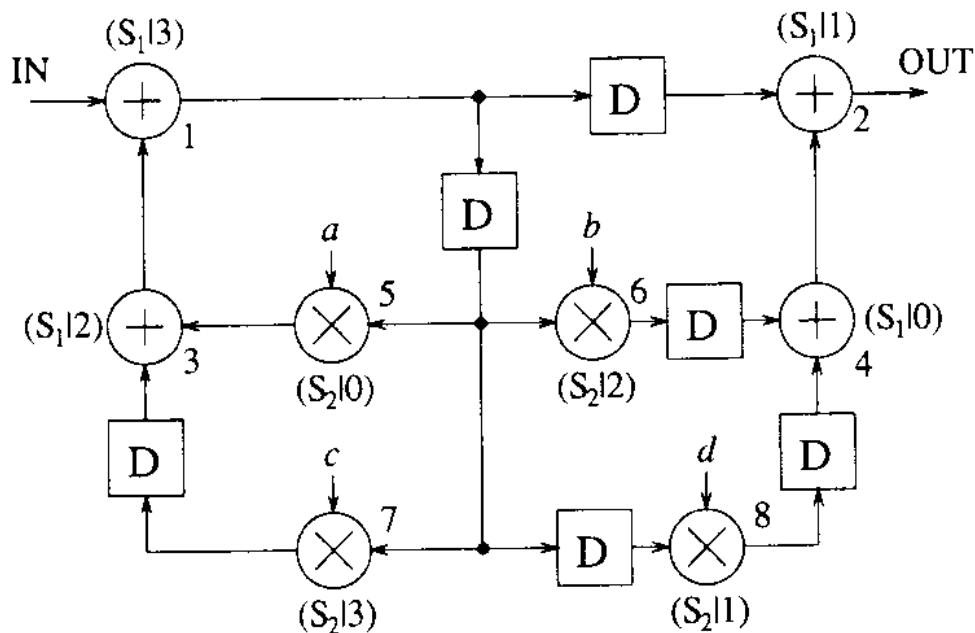
# Folding Transform

$$D_F(U \xrightarrow{e} V) = [N(l + w(e)) + v] - [Nl + P_U + u] = Nw(e) - P_U + v - u$$



$$\begin{aligned} D_F(1 \rightarrow 2) &= 4(1) - 1 + 1 - 3 = 1 \\ D_F(1 \rightarrow 5) &= 4(1) - 1 + 0 - 3 = 0 \\ D_F(1 \rightarrow 6) &= 4(1) - 1 + 2 - 3 = 2 \\ D_F(1 \rightarrow 7) &= 4(1) - 1 + 3 - 3 = 3 \\ D_F(1 \rightarrow 8) &= 4(2) - 1 + 1 - 3 = 5 \\ D_F(3 \rightarrow 1) &= 4(0) - 1 + 3 - 2 = 0 \\ D_F(4 \rightarrow 2) &= 4(0) - 1 + 1 - 0 = 0 \\ D_F(5 \rightarrow 3) &= 4(0) - 2 + 2 - 0 = 0 \\ D_F(6 \rightarrow 4) &= 4(1) - 2 + 0 - 2 = 0 \\ D_F(7 \rightarrow 3) &= 4(1) - 2 + 2 - 3 = 1 \\ D_F(8 \rightarrow 4) &= 4(1) - 2 + 0 - 1 = 1. \end{aligned}$$


$S_1 = \{4, 2, 3, 1\}$  for one adder with 1 stage pipelining  $P_A = 1$

$S_2 = \{5, 8, 6, 7\}$  for one multiplier with 2 stages pipelining  $P_M = 2$

$N = 4$



# Folding Transform

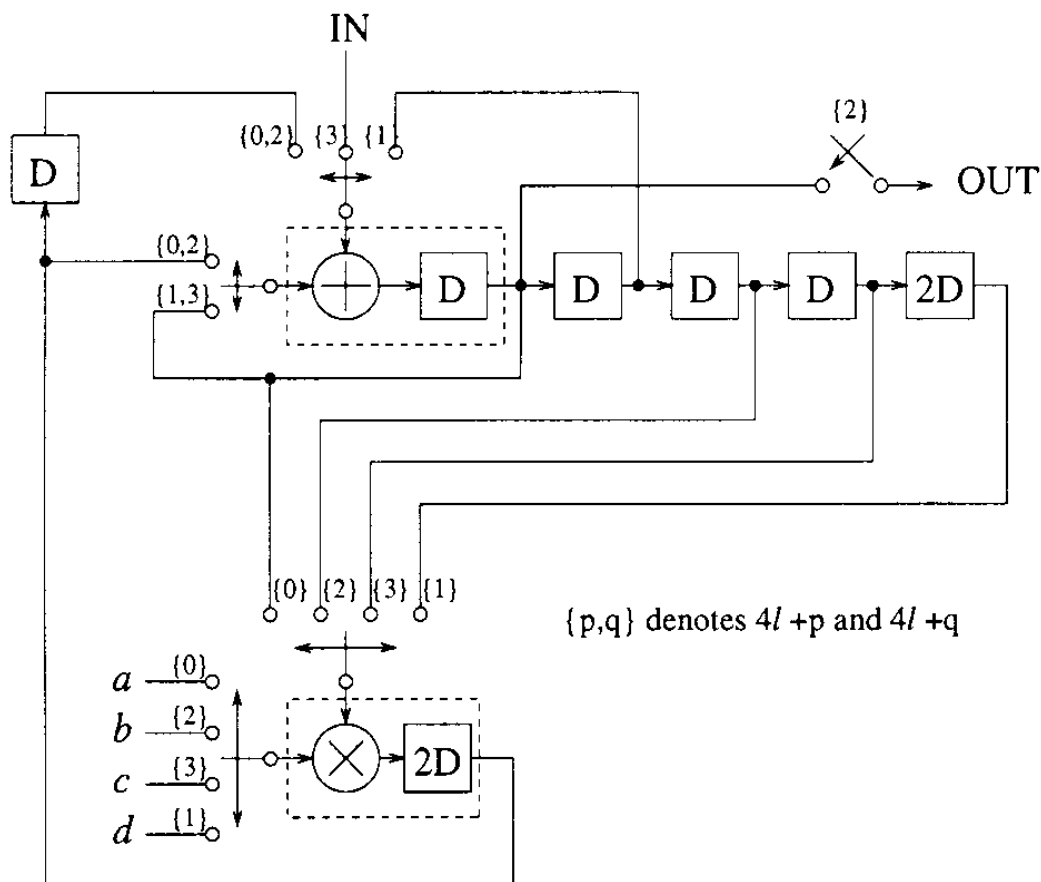

$$\begin{aligned}
 D_F(1 \rightarrow 2) &= 4(1) - 1 + 1 - 3 = 1 \\
 D_F(1 \rightarrow 5) &= 4(1) - 1 + 0 - 3 = 0 \\
 D_F(1 \rightarrow 6) &= 4(1) - 1 + 2 - 3 = 2 \\
 D_F(1 \rightarrow 7) &= 4(1) - 1 + 3 - 3 = 3 \\
 D_F(1 \rightarrow 8) &= 4(2) - 1 + 1 - 3 = 5 \\
 D_F(3 \rightarrow 1) &= 4(0) - 1 + 3 - 2 = 0 \\
 D_F(4 \rightarrow 2) &= 4(0) - 1 + 1 - 0 = 0 \\
 D_F(5 \rightarrow 3) &= 4(0) - 2 + 2 - 0 = 0 \\
 D_F(6 \rightarrow 4) &= 4(1) - 2 + 0 - 2 = 0 \\
 D_F(7 \rightarrow 3) &= 4(1) - 2 + 2 - 3 = 1 \\
 D_F(8 \rightarrow 4) &= 4(1) - 2 + 0 - 1 = 1.
 \end{aligned}$$



# Retiming for Folding (1/6)

- Realizable folding:  $D_F(U \xrightarrow{e} V) \geq 0$
- Once valid folding sets have been assigned, retiming can be used to either satisfy this property or determine that the folding sets are not feasible





# Retiming for Folding (2/6)

## ■ Retiming constraints:

$$w_r(e) = w(e) + r(V) - r(U),$$

$$D'_F(U \xrightarrow{e} V) \geq 0$$


$$Nw_r(e) - P_U + v - u \geq 0.$$

$$N(w(e) + r(V) - r(U)) - P_U + v - u \geq 0.$$

$$r(U) - r(V) \leq \frac{D_F(U \xrightarrow{e} V)}{N}.$$

$$r(U) - r(V) \leq \left\lfloor \frac{D_F(U \xrightarrow{e} V)}{N} \right\rfloor$$

# Retiming for Folding (3/6)

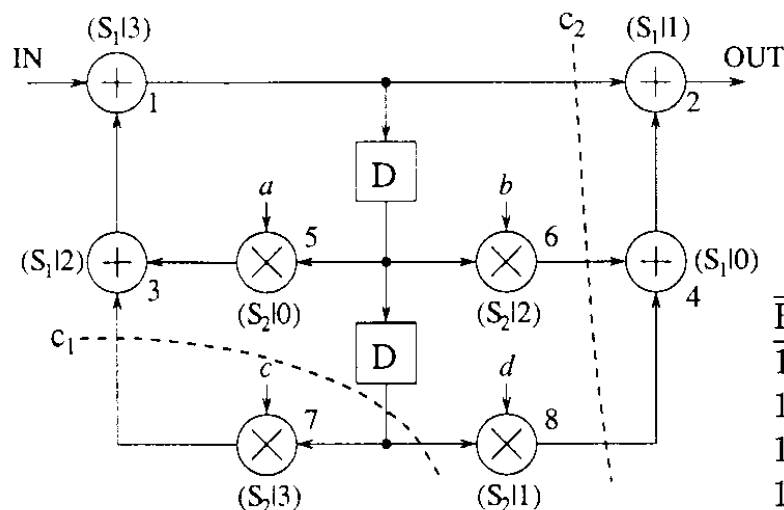


$$r(U) - r(V) \leq \left\lfloor \frac{D_F(U \xrightarrow{e} V)}{N} \right\rfloor$$

Edge	Folding Equation	Retiming for Folding Constraint
1 → 2	$D_F(1 \rightarrow 2) = -3$	$r(1) - r(2) \leq -1$
1 → 5	$D_F(1 \rightarrow 5) = 0$	$r(1) - r(5) \leq 0$
1 → 6	$D_F(1 \rightarrow 6) = 2$	$r(1) - r(6) \leq 0$
1 → 7	$D_F(1 \rightarrow 7) = 7$	$r(1) - r(7) \leq 1$
1 → 8	$D_F(1 \rightarrow 8) = 5$	$r(1) - r(8) \leq 1$
3 → 1	$D_F(3 \rightarrow 1) = 0$	$r(3) - r(1) \leq 0$
4 → 2	$D_F(4 \rightarrow 2) = 0$	$r(4) - r(2) \leq 0$
5 → 3	$D_F(5 \rightarrow 3) = 0$	$r(5) - r(3) \leq 0$
6 → 4	$D_F(6 \rightarrow 4) = -4$	$r(6) - r(4) \leq -1$
7 → 3	$D_F(7 \rightarrow 3) = -3$	$r(7) - r(3) \leq -1$
8 → 4	$D_F(8 \rightarrow 4) = -3$	$r(8) - r(4) \leq -1$


# Retiming for Folding (4/6)
 
## ■ Constraint graph


- $r(1)=-1$
- $r(2)=0$
- $r(3)=-1$
- $r(4)=0$
- $r(5)=-1$
- $r(6)=-1$
- $r(7)=-2$
- $r(8)=-1$




# Retiming for Folding (5/6)

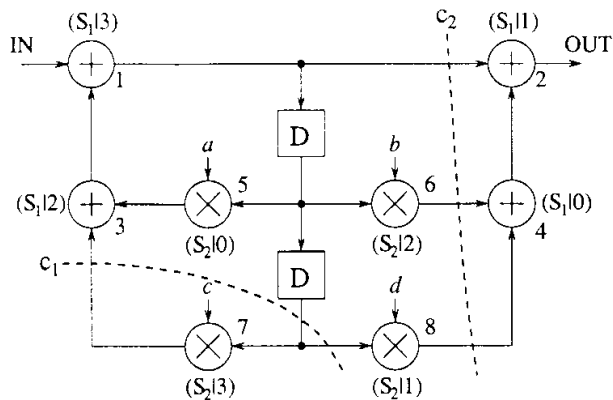

Retiming

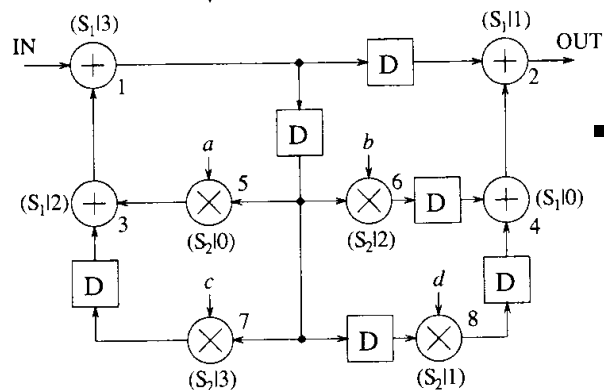


Folding

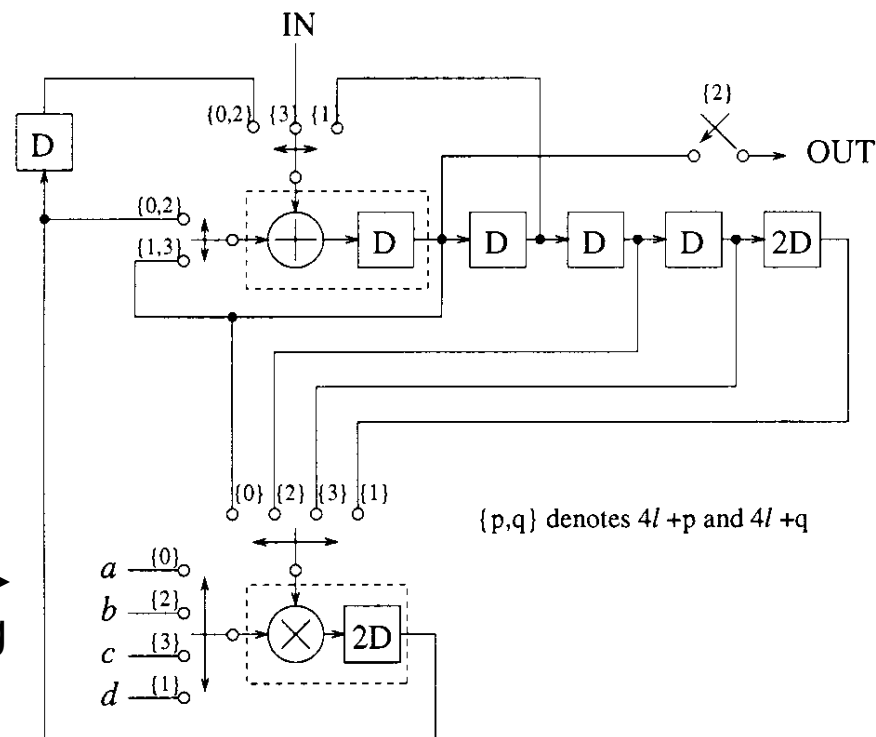
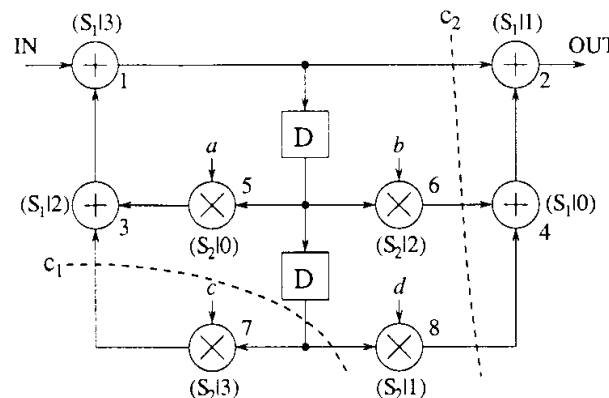
# Retiming for Folding (6/6)

- Another point of view
  - Apply cutset retiming at  $c_1$  and  $c_2$  to add/subtract  $w$  delays
  - $\rightarrow$  add/subtract  $Nw$  on  $D_F$
  - To make  $D_F \geq 0$



Edge	Folding Equation	Retiming for Folding Constraint
1 $\rightarrow$ 2	$D_F(1 \rightarrow 2) = -3$	$r(1) - r(2) \leq -1$
1 $\rightarrow$ 5	$D_F(1 \rightarrow 5) = 0$	$r(1) - r(5) \leq 0$
1 $\rightarrow$ 6	$D_F(1 \rightarrow 6) = 2$	$r(1) - r(6) \leq 0$
1 $\rightarrow$ 7	$D_F(1 \rightarrow 7) = 7$	$r(1) - r(7) \leq 1$
1 $\rightarrow$ 8	$D_F(1 \rightarrow 8) = 5$	$r(1) - r(8) \leq 1$
3 $\rightarrow$ 1	$D_F(3 \rightarrow 1) = 0$	$r(3) - r(1) \leq 0$
4 $\rightarrow$ 2	$D_F(4 \rightarrow 2) = 0$	$r(4) - r(2) \leq 0$
5 $\rightarrow$ 3	$D_F(5 \rightarrow 3) = 0$	$r(5) - r(3) \leq 0$
6 $\rightarrow$ 4	$D_F(6 \rightarrow 4) = -4$	$r(6) - r(4) \leq -1$
7 $\rightarrow$ 3	$D_F(7 \rightarrow 3) = -3$	$r(7) - r(3) \leq -1$
8 $\rightarrow$ 4	$D_F(8 \rightarrow 4) = -3$	$r(8) - r(4) \leq -1$




# Register Minimization Techniques (1/8)

## ■ Lifetime analysis



- A procedure used to compute the minimum number of registers required to implement a DSP algorithm in hardware
- Ex:
  - a lives during time unit {1, 2, 3, 4}
  - b lives during time unit {2, 3, 4, 5, 6, 7}
  - c lives during time unit {5, 6, 7}

# Register Minimization Techniques (2/8)
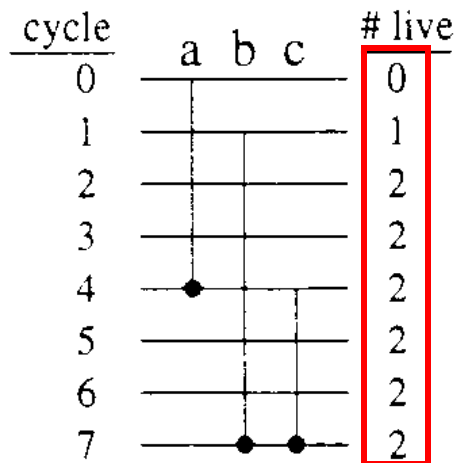
## ■ Lifetime analysis—linear lifetime chart



Minimum number of required registers

  

3 iterations with period N=6

# Register Minimization Techniques (3/8)

- Lifetime analysis—lifetime table
- Ex: transpose matrix

$$T_{output} = T_{z\text{out}} + \text{latency}$$


$$\begin{bmatrix} a & b & c \\ d & e & f \\ g & h & i \end{bmatrix}$$

Sample	$T_{input}$	$T_{z\text{out}}$	$T_{diff}$	$T_{output}$	Life Period ( $T_{input} \rightarrow T_{output}$ )
<i>a</i>	0	0	0	4	0 → 4
<i>b</i>	1	3	2	7	1 → 7
<i>c</i>	2	6	4	10	2 → 10
<i>d</i>	3	1	-2	5	3 → 5
<i>e</i>	4	4	0	8	4 → 8
<i>f</i>	5	7	2	11	5 → 11
<i>g</i>	6	2	-4	6	6 → 6
<i>h</i>	7	5	-2	9	7 → 9
<i>i</i>	8	8	0	12	8 → 12


Illegal! → add latency 4



# Register Minimization Techniques (4/8)

 

Linear lifetime chart

 


Circular lifetime chart




# Register Minimization Techniques (6/8)

cycle	input	R1	R2	R3	R4	output
0	a					
1	b	a				
2	c	b	a			
3	d	c	b	a		
4	e	d	c	b	a	a
5	f	e	d	c	b	d
6	g	f	e	b	c	g
7	h	c	f	e	b	b
8	i	h	c	f	e	e
9		i	h	c	f	h
10			i	f	c	c
11				i	f	f
12					i	i

 



# Register Minimization Techniques (7/8)

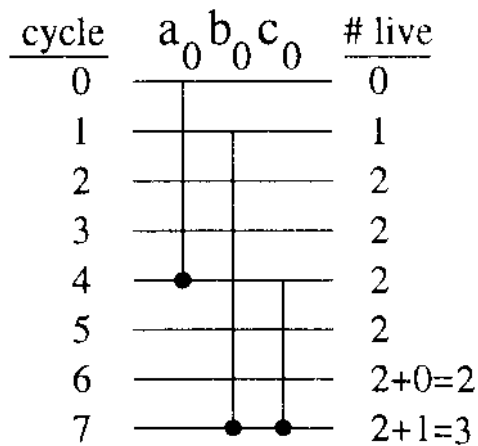


cycle	input	R1	R2	R3	output
0	a				
1	b	a			
2		b	a		
3			b	a	
4	c			b	
5				c	
6					
7					c

cycle	input	R1	R2	R3	output
0	a				
1	b	a			
2		b	a		
3			b	a	
4	c		(a)	b	a
5			b		
6			c	b	
7			(b)	(c)	b,c



# Register Minimization Techniques (8/8)

cycle	input	R1	R2	R3	output
0	a				
1	b	a			
2		b	a		
3			b	a	
4	c		(a)	b	a
5		c	b		
6			c	b	
7			(b)	(c)	b,c

 

# Register Minimization in Folded Architecture (1/4)

- Perform retiming for folding
- Write the folding equations
- Use the folding equations to construct a lifetime table
- Draw the lifetime chart and determine the required number of registers
- Perform forward-backward register allocation
- Draw the folded architecture that uses the minimum number of registers

# Register Minimization in Folded Architecture (2/4)

## ■ Lifetime table

□  $T_{input}$  of node  $U$  is  $u + P_U$


□  $T_{output}$  of the node  $U$  is  $u + P_U + \max_V \{D_F(U \rightarrow V)\}$

$$\begin{aligned}
 D_F(1 \rightarrow 2) &= 4(1) - 1 + 1 - 3 = 1 \\
 D_F(1 \rightarrow 5) &= 4(1) - 1 + 0 - 3 = 0 \\
 D_F(1 \rightarrow 6) &= 4(1) - 1 + 2 - 3 = 2 \\
 D_F(1 \rightarrow 7) &= 4(1) - 1 + 3 - 3 = 3 \\
 D_F(1 \rightarrow 8) &= 4(2) - 1 + 1 - 3 = 5 \\
 D_F(3 \rightarrow 1) &= 4(0) - 1 + 3 - 2 = 0 \\
 D_F(4 \rightarrow 2) &= 4(0) - 1 + 1 - 0 = 0 \\
 D_F(5 \rightarrow 3) &= 4(0) - 2 + 2 - 0 = 0 \\
 D_F(6 \rightarrow 4) &= 4(1) - 2 + 0 - 2 = 0 \\
 D_F(7 \rightarrow 3) &= 4(1) - 2 + 2 - 3 = 1 \\
 D_F(8 \rightarrow 4) &= 4(1) - 2 + 0 - 1 = 1.
 \end{aligned}$$



node	$T_{input} \rightarrow T_{output}$
1	4 → 9
2	—
3	3 → 3
4	1 → 1
5	2 → 2
6	4 → 4
7	5 → 6
8	3 → 4
 
# Register Minimization in Folded Architecture (3/4)




cycle	input	R1	R2	output
0				
1				
2				
3	$n_8$			
4	$n_1$	$n_8$		$n_8$
5	$n_7$	$n_1$		
6		$n_7$	$n_1$	$n_7$
7			$n_1$	
8			$n_1$	
9			$n_1$	$n_1$



# Register Minimization in Folded Architecture (4/4)

- Number of registers: 6  $\rightarrow$  2

cycle	input	R1	R2	output
0				
1				
2				
3	$n_8$			
4	$n_1$	$(n_8)$		$n_8$
5	$n_7$	$(n_1)$		
6		$(n_7)$	$(n_1)$	$n_7$
7			$(n_7)$	
8			$(n_7)$	
9			$(n_1)$	$n_1$

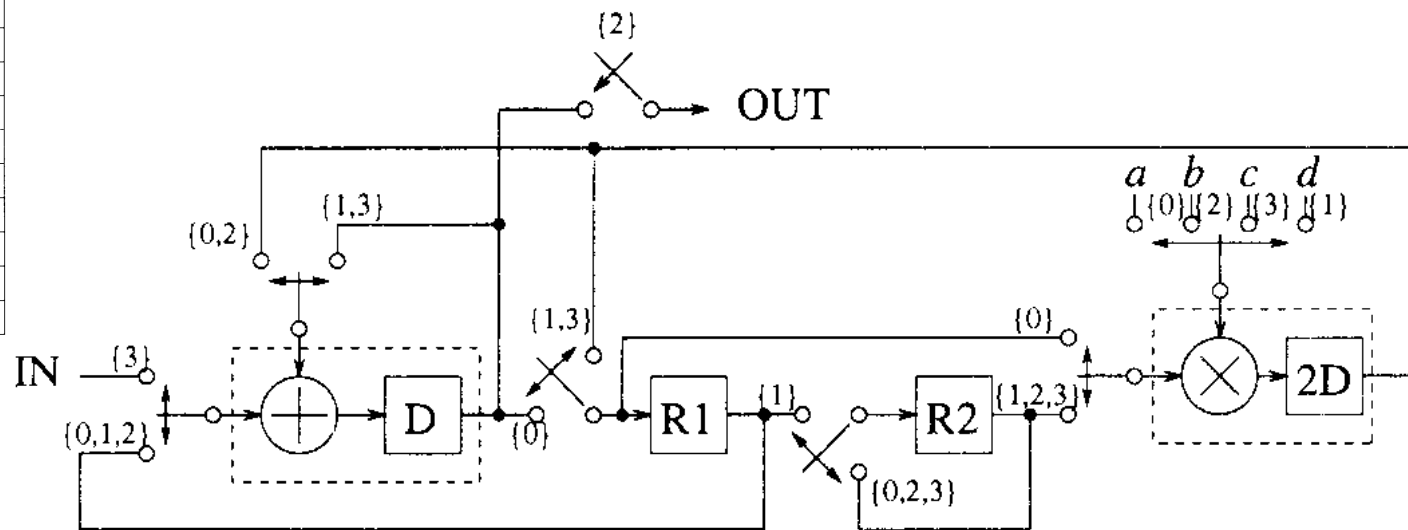

$\{p,q\}$  denotes  $4l+p$  and  $4l+q$