



Processing Elements Design

Shao-Yi Chien



Introduction

- Implementation of basic arithmetic operations
- Number systems
 - Conventional number systems
 - Redundant number systems
 - Residue number systems
- Arithmetic
 - Bit-parallel arithmetic
 - Bit-serial arithmetic
 - Serial-parallel arithmetic
 - Division
 - Distributed arithmetic
 - CORDIC



Conventional Number Systems

- Conventional number systems are nonredundant, weighted, positional number systems

$$x = \sum_{i=0}^{W_d-1} w_i x_i$$

Nonredundant: one number has only one representation

W_d : word length

w_i : weights \rightarrow **weighted**

w_i depends only on the position of the digit \rightarrow **positional**

For fix-radix systems, $w_i=r^i$

- Fix-point: the position of binary point is fixed
- Floating point: signed mantissa and signed exponent



Signed-Magnitude Representation

- Range

- $[-1+Q, 1-Q]$

- $Q=(0.00..01)$

$$x = (1 - 2x_0) \sum_{i=1}^{W_d-1} x_i 2^{-i}$$

- Complex for addition and subtraction

$$(+0.828125)_{10} = (0.110101)_{SM}$$

$$(-0.828125)_{10} = (1.110101)_{SM}$$

- Easy for multiplication and division

$$(0)_{10} = (0.000000)_{SM} \text{ or } (1.000000)_{SM}$$



One's Complement

- Range

 - $[-1+Q, 1-Q]$

$$x = -x_0(1 - Q) + \sum_{i=1}^{W_d - 1} x_i 2^{-i}$$

- Change sign is easy

$$(+0.828125)_{10} = (0.110101)_{1C}$$

- Addition, subtraction, and multiplication are complex

$$(-0.828125)_{10} = (1.001010)_{1C}$$

$$(0)_{10} = (0.000000)_{1C} \text{ or } (1.111111)_{1C}$$



Two's Complement

$$\mathbf{x} = -x_0 + \sum_{i=1}^{W_d-1} x_i 2^{-i}$$

$$(+0.828125)_{10} = (0.110101)_{2C}$$

$$(-0.828125)_{10} = (1.001010)_{2C} + (0.000001)_{2C} = (1.001011)_{2C}$$

$$(0)_{10} = (0.000000)_{2C}$$

- Range

- $[-1, 1-Q]$

- The most widely used representation



Binary Offset Representation

$$x = (x_0 - 1) + \sum_{i=1}^{W_d-1} x_i 2^{-i}$$

$$(+0.828125)_{10} = (1.110101)_{\text{BO}}$$

$$(-0.828125)_{10} = (0.001011)_{\text{BO}}$$

$$(0)_{10} = (1.000000)_{\text{BO}}$$

- Range

- [-1, 1-Q]

- The sequence of digits is equal to the two's complement representation, except for the sign bit



Redundant Number Systems

(1/2)

- Redundant: one number has more than one representation
- Advantages
 - Simply and speed up certain arithmetic operation
 - Addition and subtraction can be performed without carry (barrow) paths
- Disadvantages
 - Increase the complexity for other operations, such as zero detection, sign detection, and sign conversion



Redundant Number Systems (2/2)

- Signed-digit code
- Canonic signed digit code
- On-line arithmetic



Signed-Digit Code (1/4)

$$x = \sum_{i=0}^{W_d-1} x_i 2^{-i} \text{ where } x_i = -1, 0, \text{ or } +1$$

■ Range: $[-2+Q, 2-Q]$

■ Redundant

□ $(15/32)_{10} = (0.01111)_{2C} = (0.1000-1)_{SDC} = (0.01111)_{SDC}$

□ $(-15/32)_{10} = (1.10001)_{2C} = (0.-10001)_{SDC}$
 $= (0.0-1-1-1-1)_{SDC}$



Signed-Digit Code (2/4)

- SDC number is not unique
- Has problems to
 - Quantize
 - Compare
 - Overflow check
 - Change to conventional number systems for these operations



Signed-Digit Code (3/4)

- Example of addition
 - $(1-11-1)_{SDC}=(5)_{10}$
 - $(0-111)_{SDC}=(-1)_{10}$
- Rules for adding SDC numbers

$x_i y_i$ or $y_i x_i$	0 0	0 1	0 1	0 -1	0 -1	1 -1	1 1	-1 -1
$x_{i+1} y_{i+1}$	--	Neither is -1	At least one is -1	Neither is -1	At least one is -1	--	--	--
c_i	0	1	0	0	-1	0	1	-1
z_i	0	-1	1	-1	1	0	0	0

■ $S_i = Z_i + C_{i+1}$



Signed-Digit Code (4/4)

<i>i</i>	0	1	2	3
x_i	1	-1	1	-1
y_i	0	-1	1	1
c_{i+1}	0	-1	1	—
z_i	1	0	0	0
s_i	0	1	0	0

■ $(0100)_{\text{SDC}} = (4)_{10}$

Canonic Signed Digit Code (1/3)

$$\mathbf{x} = \sum_{i=0}^{W_d-1} x_i 2^{-i} \text{ where } x_i = -1, 0, \text{ or } +1$$

$$x_i \cdot x_{i+1} = 0, \quad 0 \leq i \leq W_d - 2$$

- Range: $[-4/3+Q, 4/3-Q]$
- CSDC is a special case of SDC having a minimum number of nonzero digits



Canonic Signed Digit Code (2/3)

■ Conversion of two's-complement to CSDC numbers

□ $2^{k+n+1} - 2^k = 2^{k+n} + 2^{k+n-1} + 2^{k+n-2} + \dots + 2^k$

□ $(0.011111)_{2C} = (0.10000-1)_{CSDC}$

□ Convert in iterative manner

□ Step1: $011\dots1 \rightarrow 100\dots-1$

□ Step2: $(-1, 1) \rightarrow (0, -1)$, $(0, 1, 1) \rightarrow (1, 0, -1)$

□ Ex: $(0.110101101101)_{2C}$
 $= (1.00-10-100-10-101)_{CSDC}$



Canonic Signed Digit Code (3/3)

- Conversion of SDC to two's complement numbers
 - Separate the SDC number into two parts
 - One parts holds the digit that are either 0 or 1
 - The other part has -1 digits
 - Subtract these two numbers



On-Line Arithmetic

- The number systems with the property that it is possible **to compute the i -th digit of the results using only the first $(i+d)$ -th digit**, where d is a small positive constant
- Favorable in recursive algorithm using numbers with very long word lengths
- SDC can be used for on-line addition and subtraction, $d=1$



Residue Number Systems (1/2)

- For a given number x and moduli set $\{m_i\}$, $i=1, 2, \dots, p$
 - $x=q_i m_i+r_i$
 - RNS representation: $x=(r_1, r_2, \dots, r_p)$
- Advantages
 - The arithmetic operations (+, -, *) can be performed for each residue independently
- Disadvantages
 - Hard for comparison, overflow detection, and quantization
 - Not easy to convert to other number systems



Residue Number Systems (2/2)

■ Example

□ Moduli set= $\{5,3,2\}$

□ Number range= $5*3*2=30$

□ $9+19=(4,0,1)_{RNS}+(4,1,1)_{RNS}$
 $=((4+4)_5, (0+1)_3, (1+1)_2)_{RNS}=(3,1,0)_{RNS}=28$

□ $8*3=(3,2,0)_{RNS}+(3,0,1)_{RNS}$
 $=((3*3)_5, (2*0)_3, (0*1)_2)_{RNS}=(4,0,0)_{RNS}=24$



Bit-Parallel Arithmetic (1/2)

- Addition and subtraction
 - Ripple carry adder (RCA) (carry propagation adder, CPA)
 - Carry-look-ahead adder (CLA)
 - Carry-save adder
 - Carry-select adder (CSA)
 - Carry-skip adder
 - Conditional-sum adder




Bit-Parallel Arithmetic (2/2)

■ Multiplication

- Shift-and-add multiplication
- Booth's algorithm
- Tree-based multipliers
- Array multipliers
- Look-up table techniques

Ripple Carry Adder (RCA) (1/2)

 
- Also called carry propagation adder (CPA)
 - Full adder




$$\begin{aligned} S &= A \oplus B \oplus D = \{\text{Parity}\} \\ &= A \cdot B \cdot D + A \cdot \bar{B} \cdot \bar{D} + \bar{A} \cdot \bar{B} \cdot D + \bar{A} \cdot B \cdot \bar{D} \\ C &= A \cdot B + A \cdot D + B \cdot D = A \cdot B + D \cdot (A + B) \end{aligned}$$

Ripple Carry Adder (RCA) (2/2)

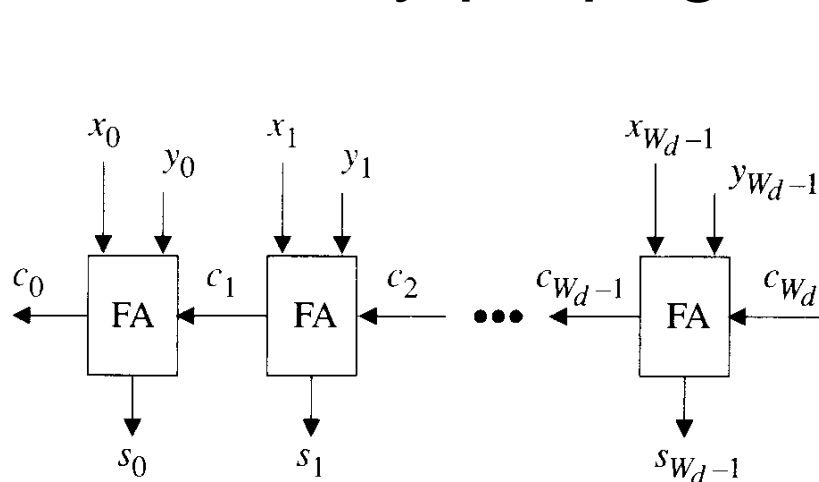- The speed of the RCA is determined by the carry propagation time




Ripple-carry adder

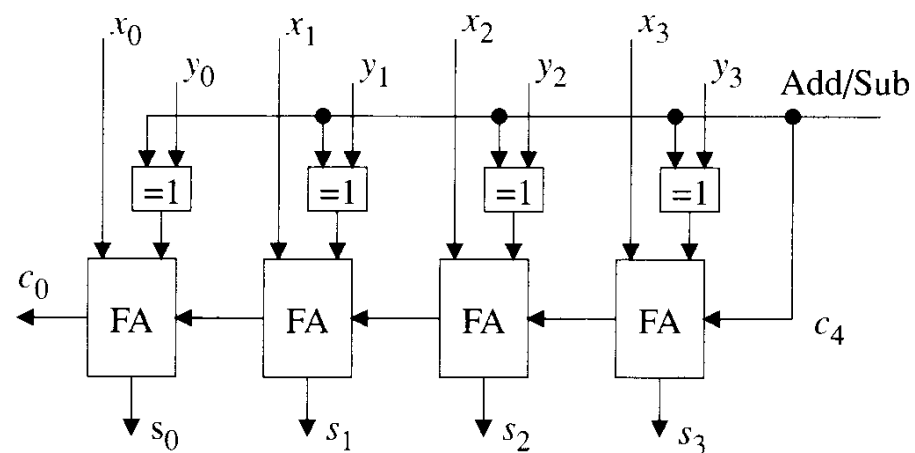

Ripple-carry adder/subtractor

Carry-Look-Ahead Adder (CLA)

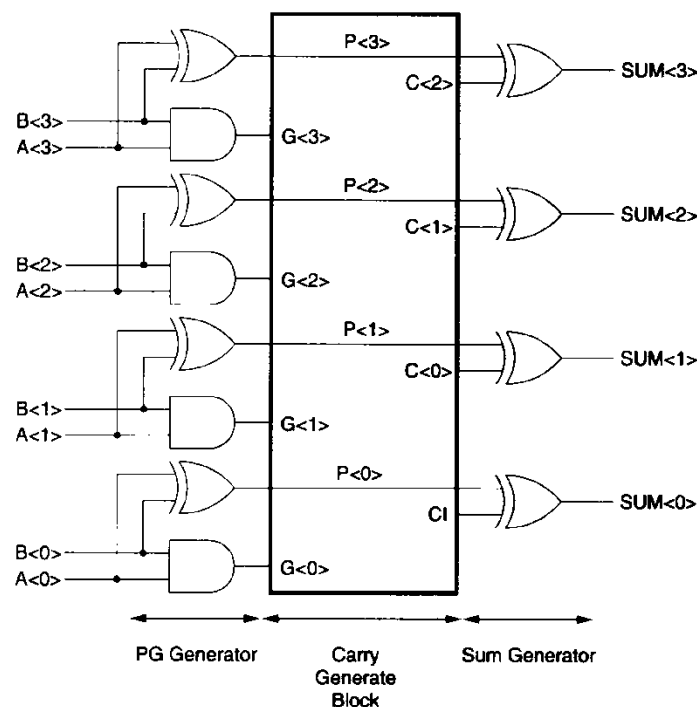
- Generate the carry with separate circuits
- $C_i = G_i + P_i \cdot C_{i-1}$
- $G_i = A_i \cdot B_i$
- $P_i = A_i + B_i$



*Different digit notation in this slide


Carry-Save Adder

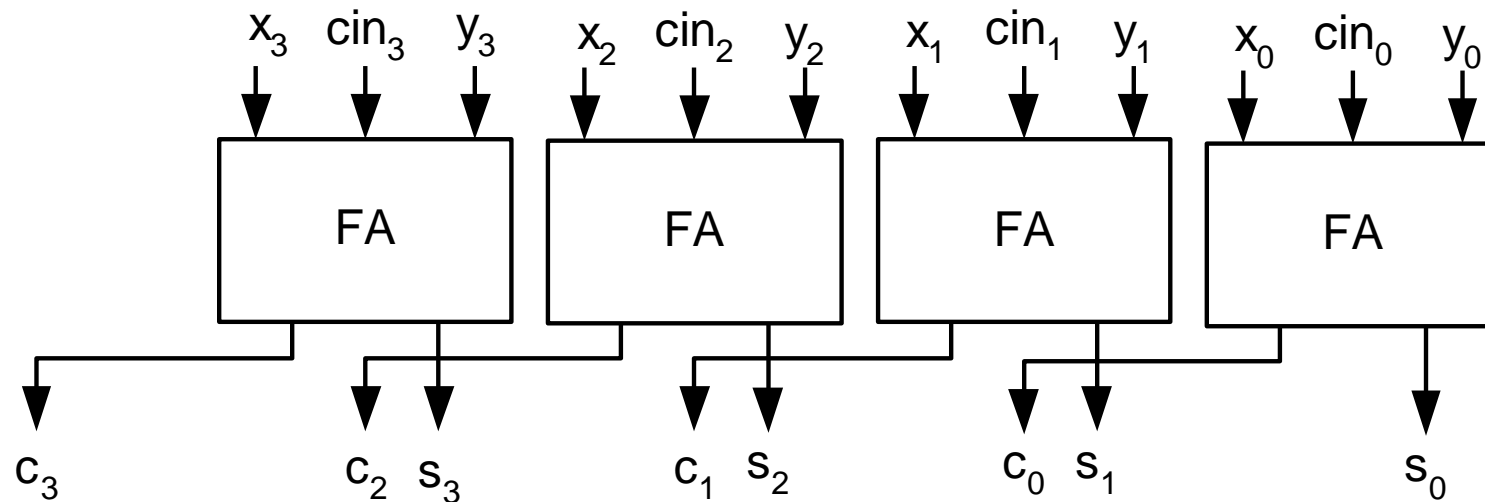- Used when adding three or more operands
- Reduce the number of operands by one for each stage




**Different digit notation in this slide*

Carry-Select Adder (CSA)

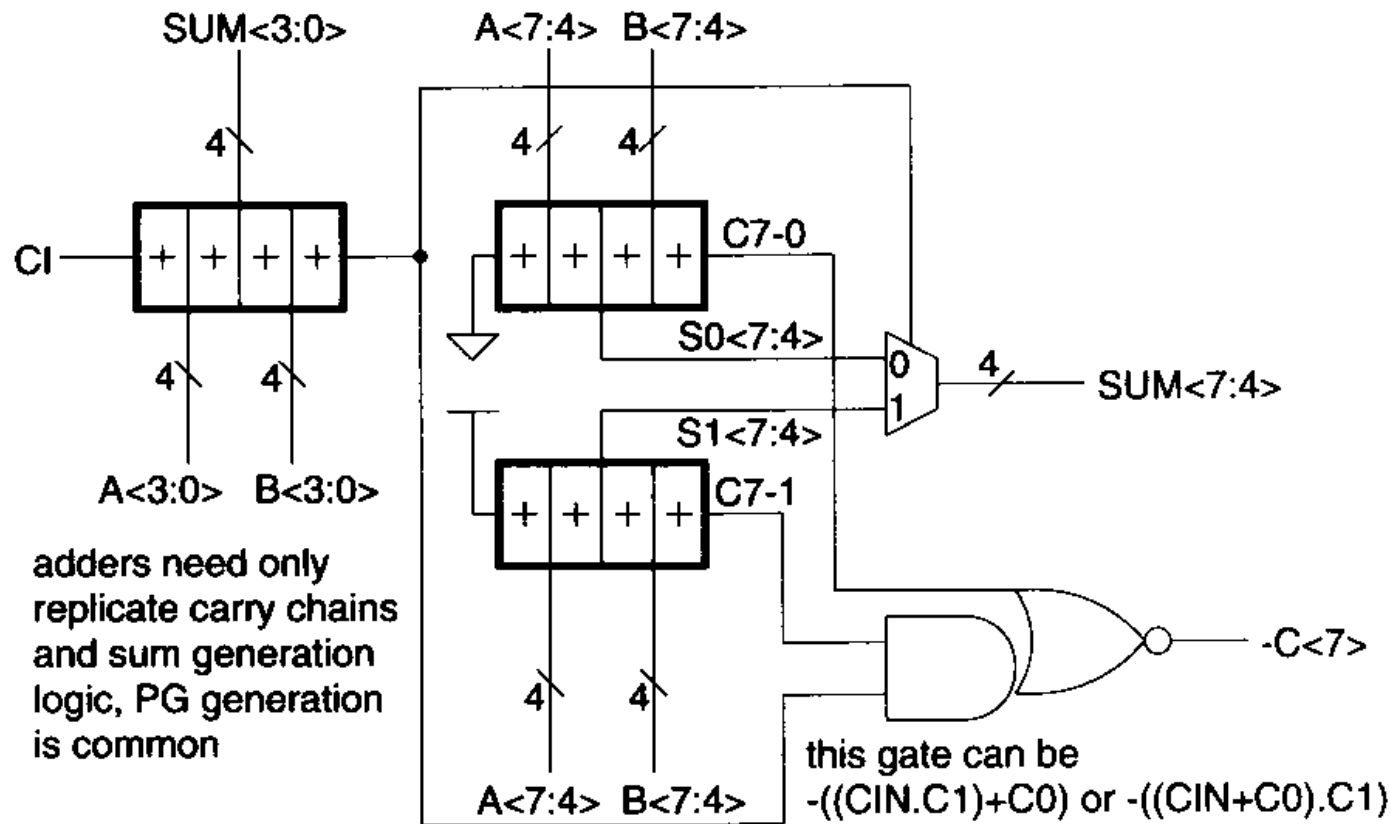

*Different digit notation in this slide

Carry-Skip Adder

 

*Different digit notation in this slide


Conditional-Sum Adder

$$S_0 = A \oplus B$$

$$S_1 = -(A \oplus B)$$

$$C_0 = A \cdot B$$


$$C_1 = A + B$$

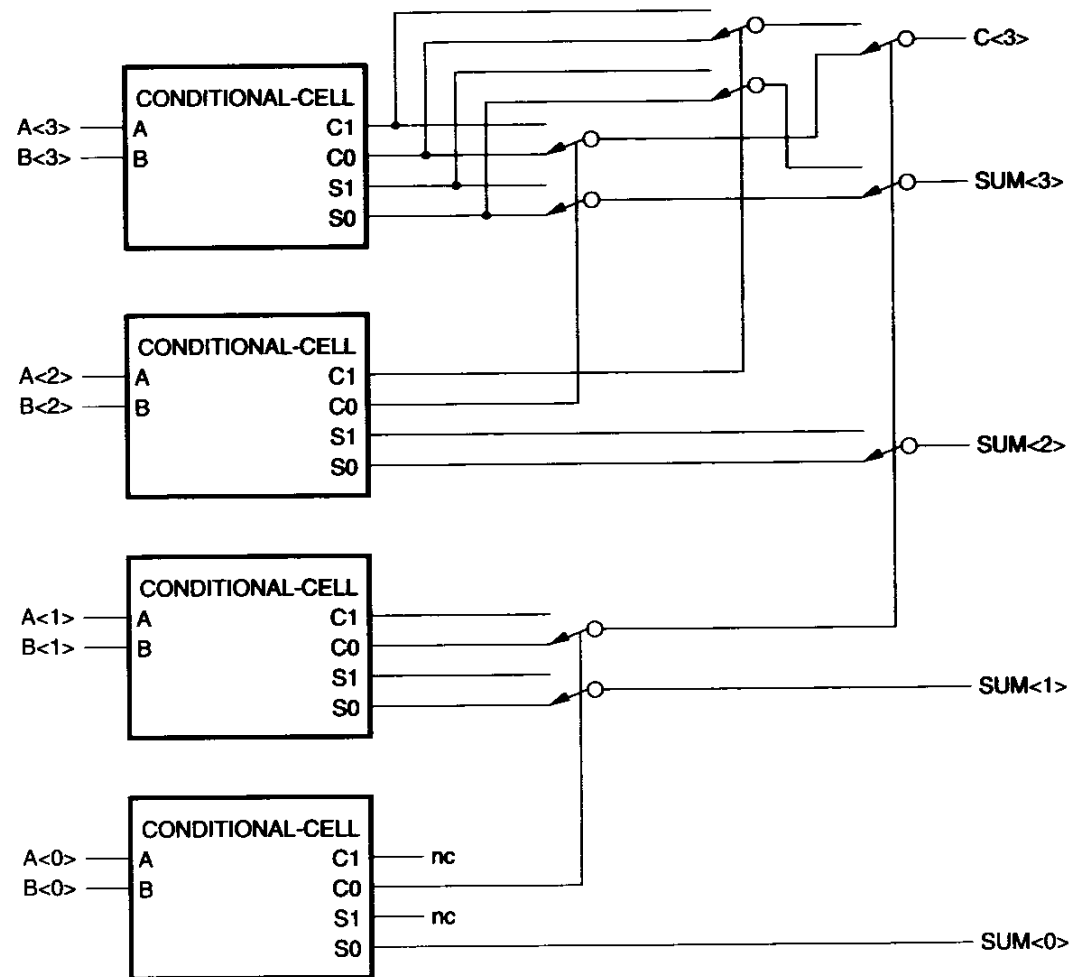

*Different digit notation in this slide


Shift-and-Add Multiplication (1/2)
 
$$y = a \left(-x_0 + \sum_{i=1}^{W_d-1} x_i 2^{-i} \right) = -ax_0 + \sum_{i=1}^{W_d-1} ax_i 2^{-i}$$



Shift-and-Add Multiplication (2/2)

 - The operation can be reduced with CSDC
- Can be used to design fix-operand multiplier





Booth's Algorithm (1/3)

- Used in modern general-purpose processors, such as MIPS R4000

$$\begin{aligned}x &= \sum_{i=1}^{15} x_i 2^{-i} - x_0 2^0 = \sum_{i=1}^8 x_{2i-1} 2^{-2i+1} + \sum_{i=1}^7 x_{2i} 2^{-2i} - x_0 2^0 \\&= \sum_{i=1}^8 x_{2i-1} 2^{-2i+1} + \sum_{i=1}^7 x_{2i} 2^{-2i+1} - 2 \sum_{i=1}^7 x_{2i} 2^{-2i-1} - x_0 2^0 \\&= \sum_{i=1}^8 x_{2i-1} 2^{-2i+1} + \sum_{i=1}^8 x_{2i} 2^{-2i+1} - 2 \sum_{i=2}^8 x_{2(i-1)} 2^{-2i+1} - x_0 2^0 \\&= \sum_{i=1}^8 \left[x_{2i-1} + x_{2i} - 2x_{2(i-1)} \right] 2^{-2i+1}\end{aligned}$$

$$\mathbf{x \cdot y = \sum_{i=1}^8 \left[x_{2i-1} + x_{2i} - 2x_{2(i-1)} \right] y 2^{-2i+1}}$$




Booth's Algorithm (2/3)

X_{2i-2}	X_{2i-1}	X_{2i}	X_{2i-1}'	Operation	Comments
0	0	0	0	+0	String of zeros
0	0	1	1	+y	Beginning of 1s
0	1	0	1	+y	A single 1
0	1	1	2	+2y	Beginning of 1s
1	0	0	-2	-2y	End of 1's
1	0	1	-1	-y	A single 0 (beginning/end of 1's)
1	1	0	-1	-y	End of 1's
1	1	1	0	-0	String of 1's




Booth's Algorithm (3/3)

 

X_{i+1}	X_i	X_{i-1}		
0	0	0	0	
0	0	1	+Y	(beginning of string)
0	1	0	+Y	(isolated)
0	1	1	+2Y	(beginning of string)
1	0	0	-2Y	(end of string)
1	0	1	-Y	(beginning / end of string)
1	1	0	-Y	(end of string)
1	1	1	0	

 Tree-Based Multipliers (Wallace Tree Multipliers)




Inputs to the second stage

Result of the second stage

Inputs to the third stage

Result of the third stage

 



Array Multipliers (1/3)

■ Baugh-Wooley's multiplier

$$\begin{aligned}
 P &= \mathbf{x} \cdot \mathbf{y} = \left(-x_0 + \sum_{i=1}^{W_d-1} x_i 2^{-i} \right) \left(-y_0 + \sum_{i=1}^{W_d-1} y_i 2^{-i} \right) \\
 &= x_0 \cdot y_0 + \sum_{i=1}^{W_d-1} \sum_{j=1}^{W_d-1} x_i \cdot y_j 2^{-i-j} - x_0 \sum_{i=1}^{W_d-1} y_i 2^{-i} - y_0 \sum_{i=1}^{W_d-1} x_i 2^{-i}
 \end{aligned}$$

Each of the two negative terms may be rewritten

$$- \sum_{i=1}^{W_d-1} x_0 \cdot y_i 2^{-i} = -1 + 2^{-W_d+1} + \sum_{i=1}^{W_d-1} (1 - x_0 \cdot y_i) 2^{-i}$$

and by using the overflow property of two's-complement representation we get

$$- \sum_{i=1}^{W_d-1} x_0 \cdot y_i 2^{-i} = 1 + 2^{-W_d+1} + \sum_{i=1}^{W_d-1} \overline{x_0 \cdot y_i} 2^{-i}$$

We get

$$\begin{aligned}
 P &= 2 + 2^{-W_d+2} + x_0 \cdot y_0 + \sum_{i=1}^{W_d-1} \sum_{j=1}^{W_d-1} x_i \cdot y_j 2^{-i-j} \\
 &\quad + \sum_{i=1}^{W_d-1} \overline{x_0 \cdot y_i} 2^{-i} + \sum_{i=1}^{W_d-1} \overline{y_0 \cdot x_i} 2^{-i}
 \end{aligned}$$




Array Multipliers (2/3)

■ Partial products

				x_0	x_1	x_2	x_3
				y_0	y_1	y_2	y_3
			1	$\overline{x_0 \cdot y_3}$	$x_1 \cdot y_3$	$x_2 \cdot y_3$	$x_3 \cdot y_3$
			$\overline{x_0 \cdot y_2}$	$x_1 \cdot y_2$	$x_2 \cdot y_2$	$x_3 \cdot y_2$	
		$\overline{x_0 \cdot y_1}$	$x_1 \cdot y_1$	$x_2 \cdot y_1$	$x_3 \cdot y_1$		
1	$x_0 \cdot y_0$	$\overline{x_1 \cdot y_0}$	$\overline{x_2 \cdot y_0}$	$\overline{x_3 \cdot y_0}$			
P_{-1}	P_0 ●	P_1	P_2	P_3	P_4	P_5	P_6



Array Multipliers (3/3)

 



Look-Up Table Techniques

- A multiplier $A \times B$ can be done with a large table with $2^{W_A+W_B}$ words
- Simplified method

$$x \cdot y = \frac{(x+y)^2}{4} - \frac{(x-y)^2}{4}$$

- Can be implemented with one addition, two subtraction, and two table look-up operations



Bit-Serial Arithmetic


■ Advantages

- Significantly reduce chip area
 - Eliminate wide bus
 - Small processing elements
- Higher clock frequency
- Often superior than bit-parallel


■ Disadvantages

- S/P P/S interface
- Complicated clocking scheme

Bit-Serial Addition and Subtraction

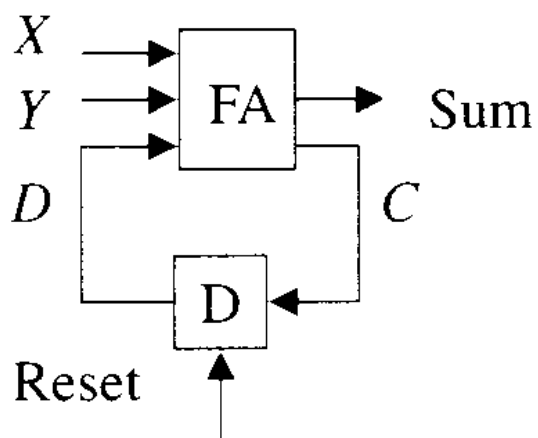


Addition

 


Subtraction

Serial/Parallel Multiplier

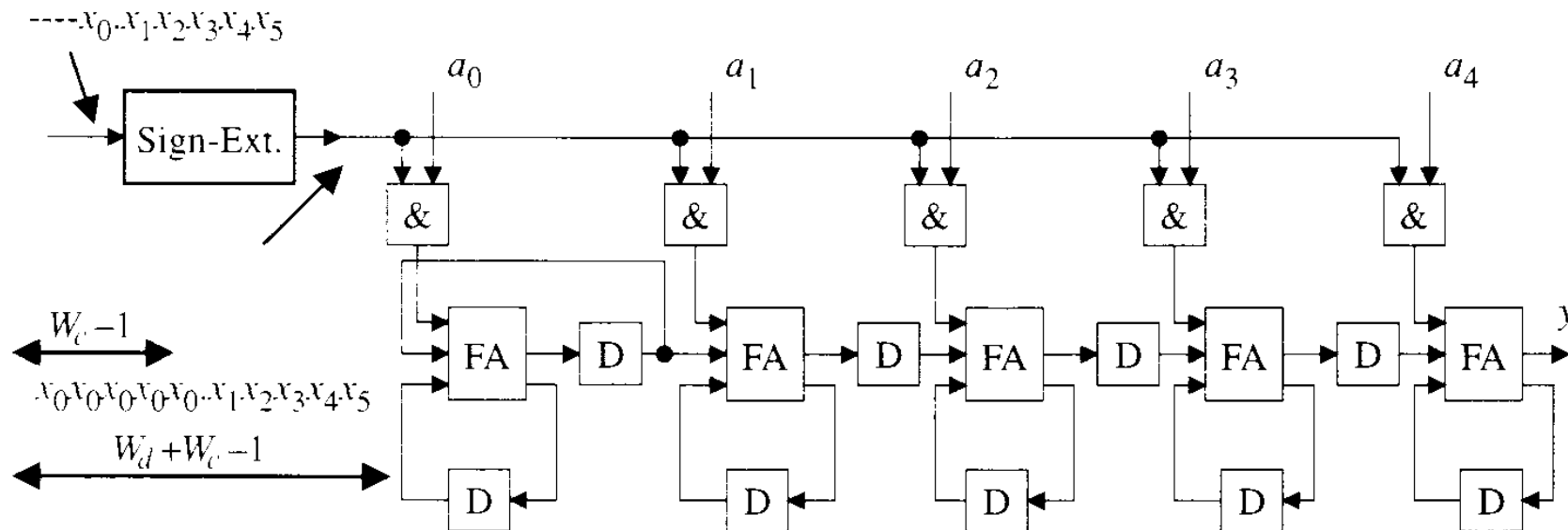- Use carry-save adders
- Need $W_d + W_c - 1$ cycles to compute the result




Modified Serial/Parallel Multiplier

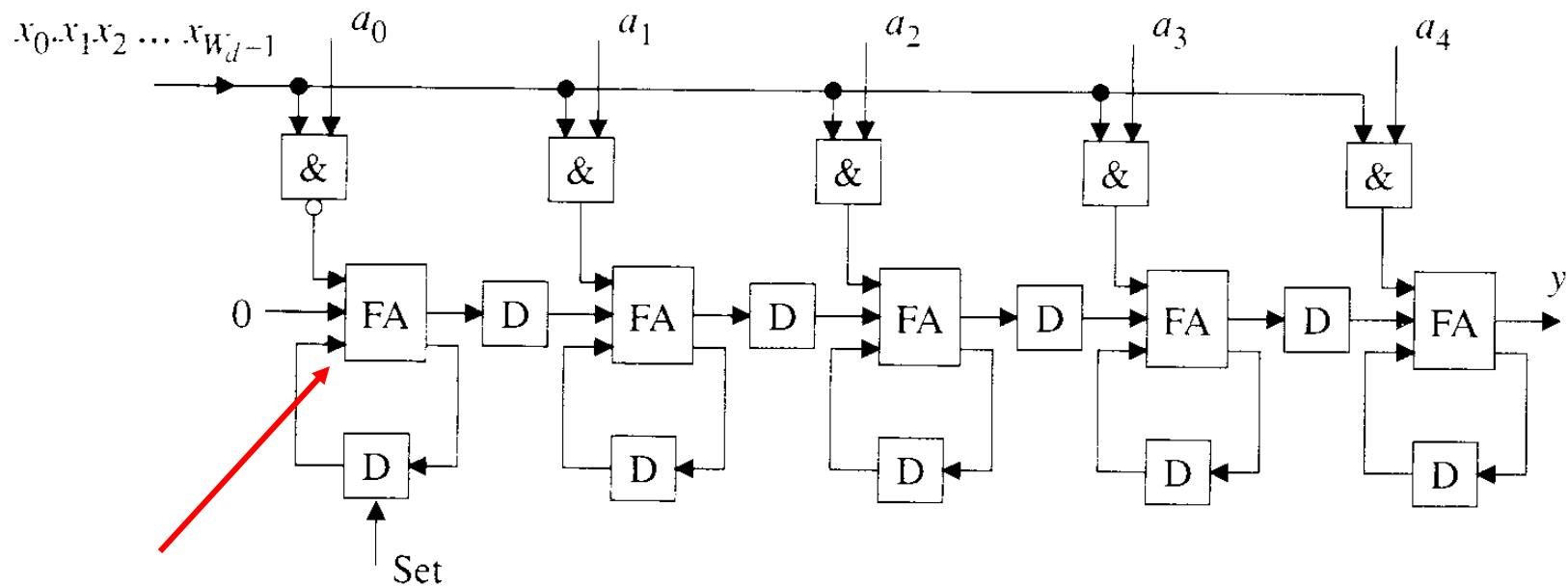


Can be implemented with a half adder

Transpose Serial/Parallel Multiplier

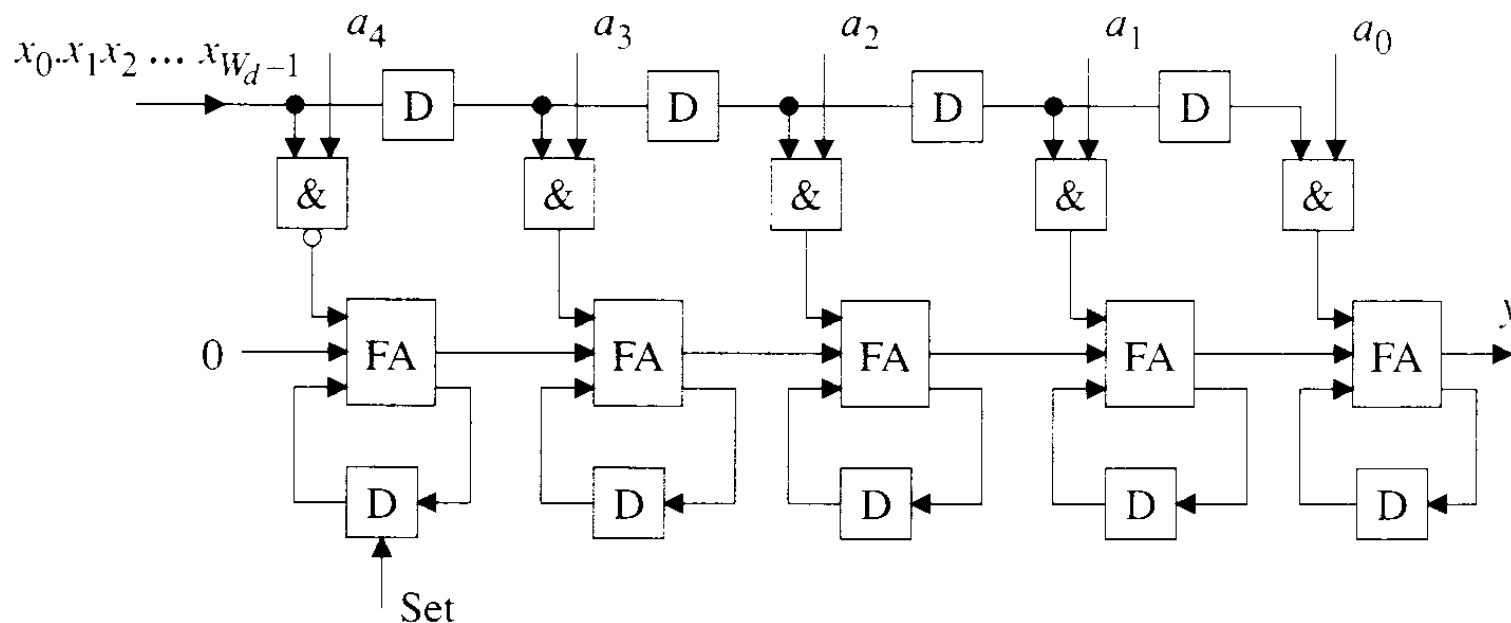

S/P Multiplier-Accumulator

■ $y = a * x + z$

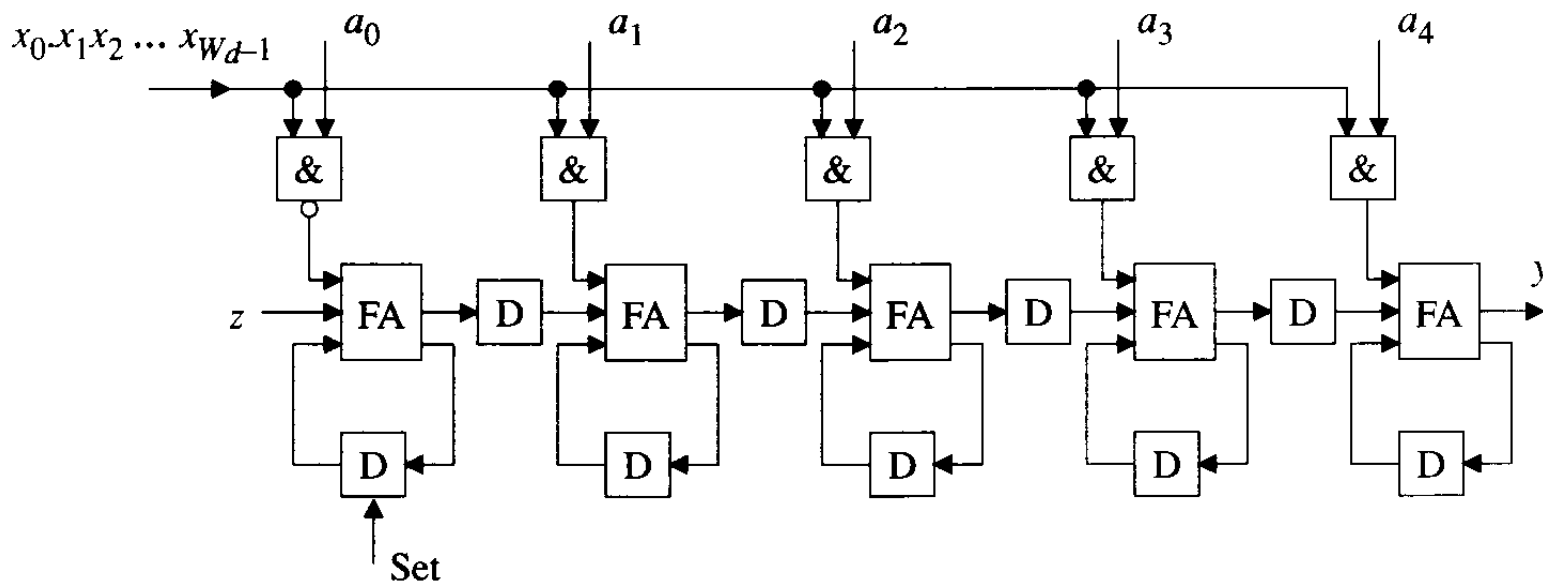





S/P Multiplier with Fixed Coefficients (1/3)

- Remove all AND gates
- Remove all FAs and corresponding D flip-flops, starting with the MSB in the coefficient, up to the first 1 in the coefficient
- Replace each FA that corresponds to a zero-bit in the coefficient with a feedthrough

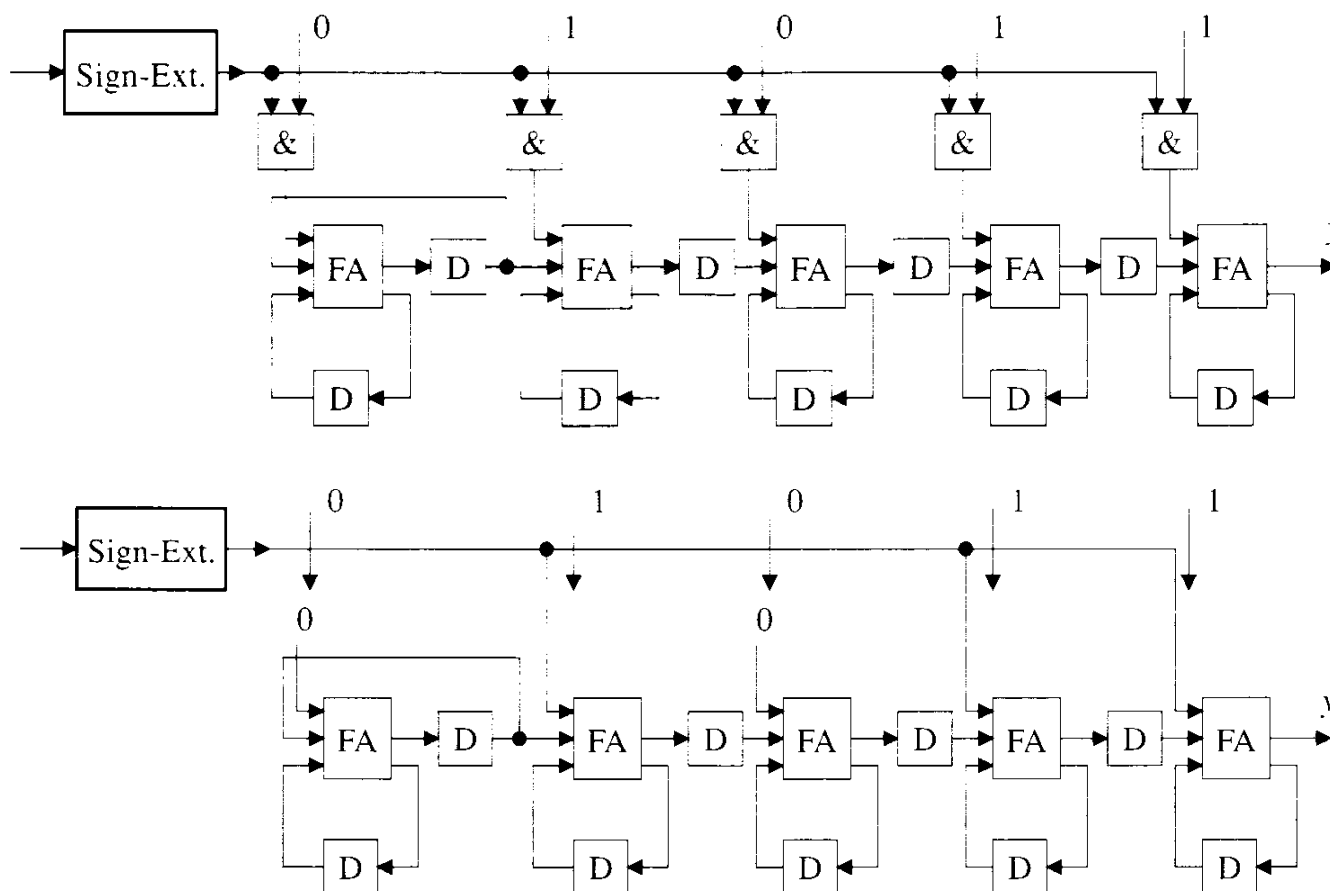S/P Multiplier with Fixed Coefficients (2/3)



 
S/P Multiplier with Fixed Coefficients (3/3)







- The number of FA = (the number of 1's)-1
- The number of D flip-flops = the number of 1-bit positions between the first and last bit positions

S/P Multiplier with CSDC Coefficients

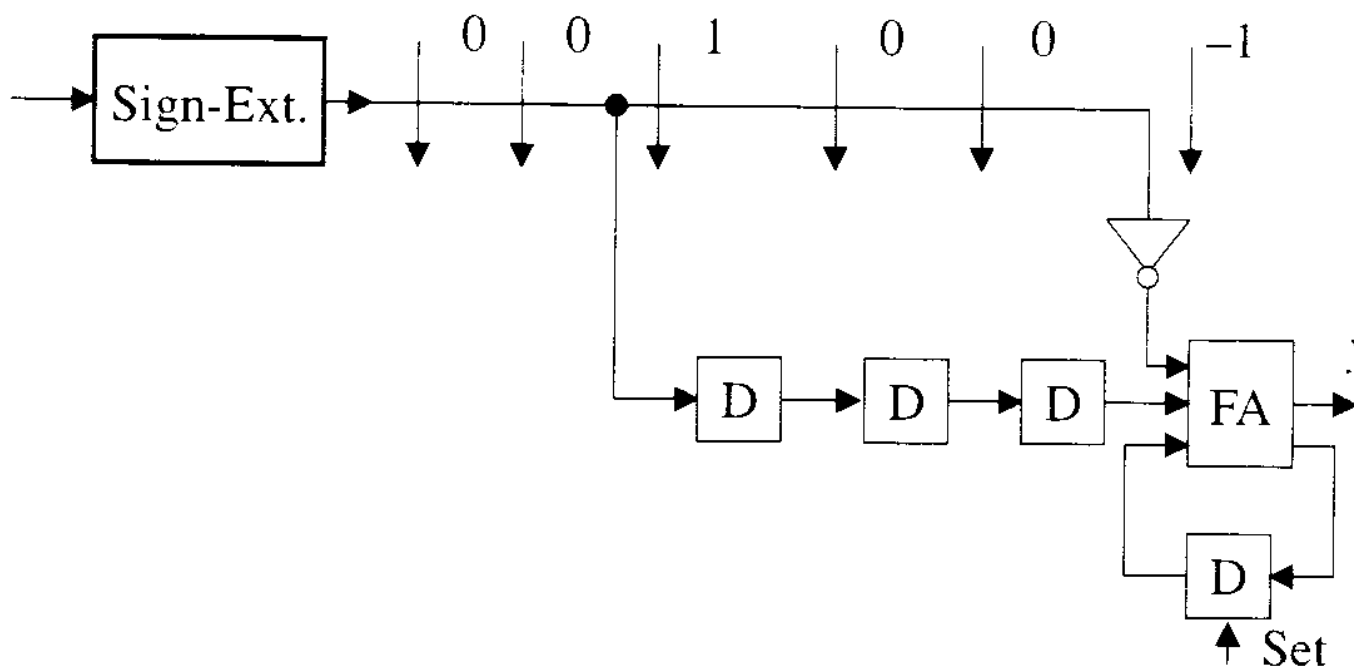■ $a = (0.00111)_{2C} = (0.0100-1)_{CSDC}$



Minimum Number of Basic Operations

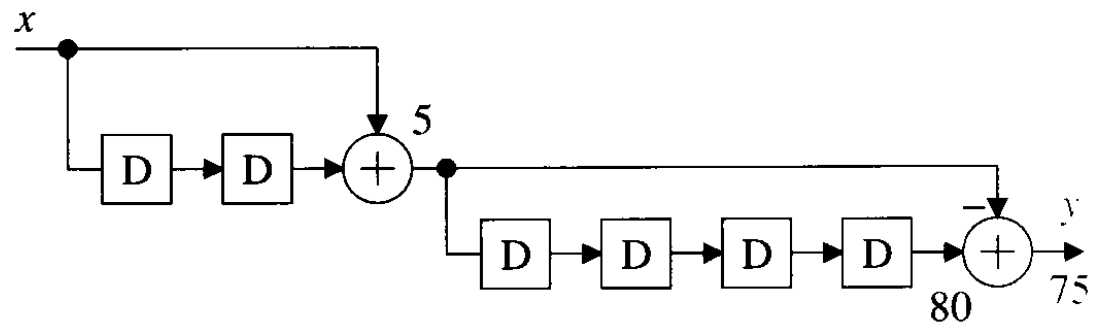 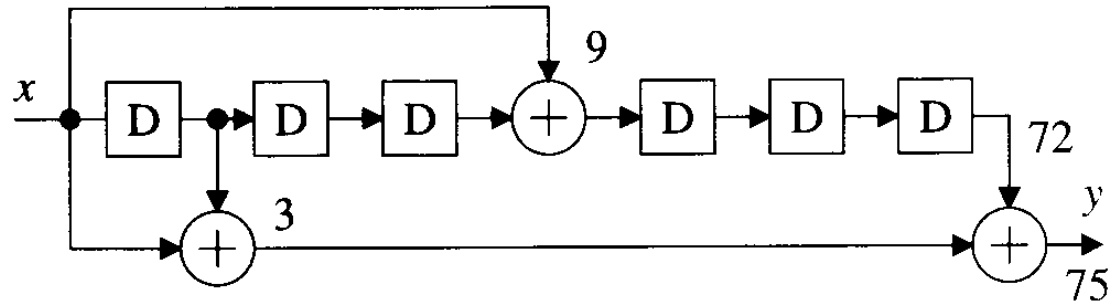 




Division

Major reference:

B. Parham, *Computer Arithmetic: Algorithms and Hardware Designs*, Oxford, 2000.

■ How to do binary division?

 

■ In the following slides, we define

- Dividend $\mathbf{z} = z_{2k-1}z_{2k-2}\dots z_1z_0$
- Divisor $\mathbf{d} = d_{k-1}d_{k-2}\dots d_1d_0$
- Quotient $\mathbf{q} = q_{k-1}q_{k-2}\dots q_1q_0$
- Remainder $\mathbf{s} = [z-(dxq)] = s_{k-1}s_{k-2}\dots s_1s_0$



What's Different?

- Added complication of requiring quotient digit selection or estimation
 - The terms to be subtracted from the dividend z are not known a priori but become known as the quotient digits are computed
 - The terms to be subtracted from the initial partial remainder must be produced from top to bottom
 - More difficult and slower than multiplication
 - Long critical path



Division

- Bit-serial division (sequential division algorithm)
- Programmed division
- Restoring bit-serial hardware divider
- Nonrestoring bit-serial hardware divider
- Division by constants
- Array divider

Bit-Serial division (Sequential Division) Algorithm

- $s^{(j)} = 2s^{(j-1)} - q_{k-j}(2^k d)$ with $s^{(0)} = z$ and $s^{(k)} = 2^k s$

- Or \longleftrightarrow

For $j=1$ to k

{

 If $(2s^{(j-1)} \geq 2^k d)$

 {

$q_{k-j} = 1;$

$s^{(j)} = 2s^{(j-1)} - (2^k d);$

 }

 Else


 {

$q_{k-j} = 0;$

$s^{(j)} = 2s^{(j-1)};$

 }

}

 


Integer division

z	0	1	1	1	0	1	0	1
$2^4 d$	1	0	1	0				
$s^{(0)}$	0	1	1	1	0	1	0	1
$2s^{(0)}$	0	1	1	1	0	1	0	1
$-q_3 2^4 d$	1	0	1	0				$\{q_3 = 1\}$
$s^{(1)}$	0	1	0	0	1	0	1	
$2s^{(1)}$	0	1	0	0	1	0	1	
$-q_2 2^4 d$	0	0	0	0				$\{q_2 = 0\}$
$s^{(2)}$	1	0	0	1	0	1		
$2s^{(2)}$	1	0	0	1	0	1		
$-q_1 2^4 d$	1	0	1	0				$\{q_1 = 1\}$
$s^{(3)}$	1	0	0	0	1			
$2s^{(3)}$	1	0	0	0	1			
$-q_0 2^4 d$	1	0	1	0				$\{q_0 = 1\}$
$s^{(4)}$	0	1	1	1				
s					0	1	1	1
q					1	0	1	1



Programmed Division

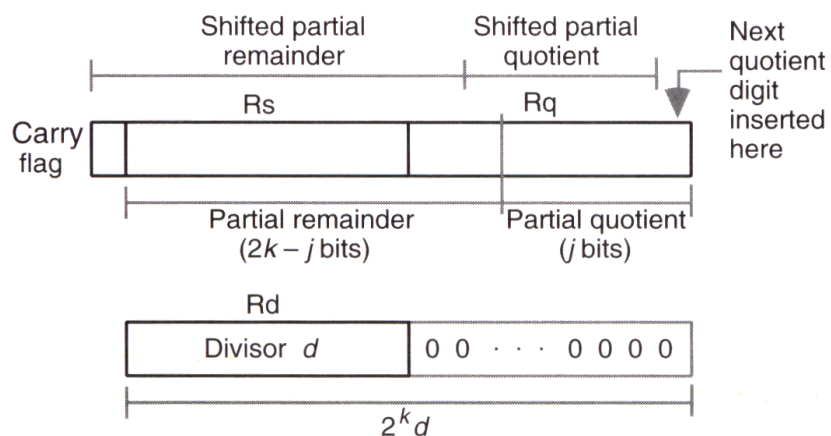

Need more than 200 instructions for a 32-bit division!!

{Using left shifts, divide unsigned $2k$ -bit dividend, z_highz_low , storing the k -bit quotient and remainder.
 Registers: R0 holds 0 Rc for counter
 Rd for divisor Rs for z_high & remainder
 Rq for z_low & quotient}

{Load operands into registers Rd, Rs, and Rq}

```
div:  load  Rd with divisor
      load  Rs with z_high
      load  Rq with z_low
```

{Check for exceptions}

```
branch d_by_0 if Rd = R0
branch d_ovfl if Rs > Rd
```

{Initialize counter}

```
load k into Rc
```

{Begin division loop}

```
d_loop:  shift  Rq left 1  {zero to LSB, MSB to carry}
         rotate Rs left 1  {carry to LSB, MSB to carry}
         skip  if carry = 1
         branch no_sub if Rs < Rd
         sub   Rd from Rs
         incr  Rq          {set quotient digit to 1}
no_sub:  decr  Rc          {decrement counter by 1}
         branch d_loop if Rc ≠ 0
```

{Store the quotient and remainder}

```
store  Rq into quotient
store  Rs into remainder
```


```
d_done:  ...
d_by_0:  ...
d_ovfl:  ...
```



Restoring Bit-Serial Hardware Divider (1/3)

- “Restoring division”
 - Assume $q=1$ first, do the trial difference
 - The remainder is restored to its correct value if the trial subtraction indicates that 1 was not the right choice for q

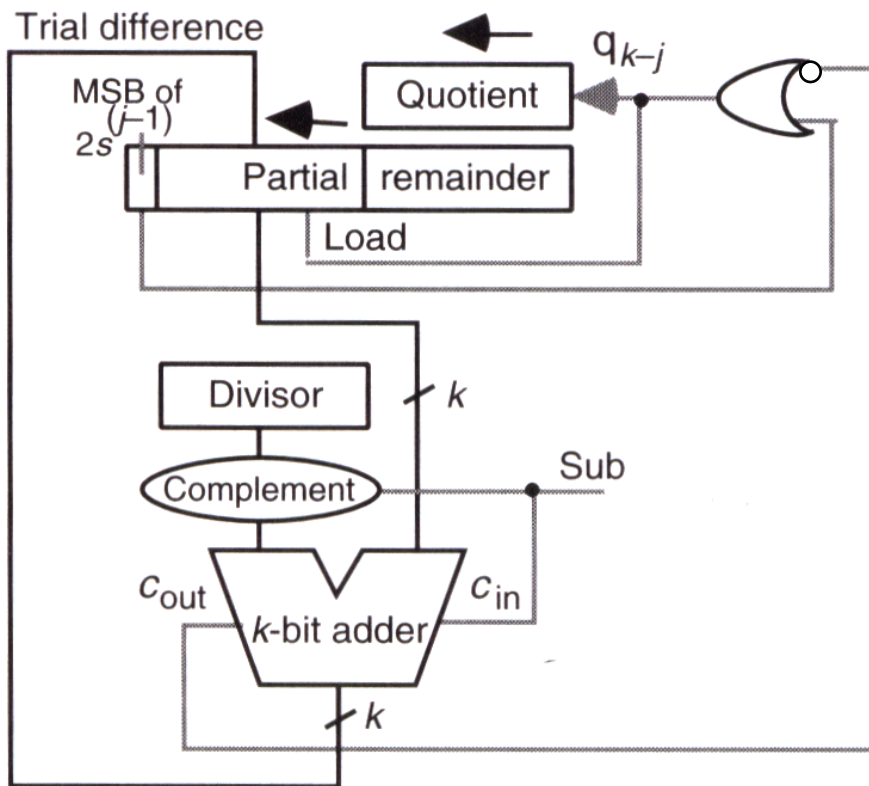Restoring Bit-Serial Hardware Divider (2/3)



Z	0	1	1	1	0	1	0	1
2^4d	0	1	0	1	0			
-2^4d	1	0	1	1	0			
$s^{(0)}$	0	0	1	1	1	0	1	0
$2s^{(0)}$	0	1	1	1	0	1	0	1
$+(-2^4d)$	1	0	1	1	0			
$s^{(1)}$	0	0	1	0	0	1	0	1
$2s^{(1)}$	0	1	0	0	1	0	1	
$+(-2^4d)$	1	0	1	1	0			
$s^{(2)}$	1	1	1	1	1	0	1	
$s^{(2)} = 2s^{(1)}$	0	1	0	0	1	0	1	
$2s^{(2)}$	1	0	0	1	0	1		
$+(-2^4d)$	1	0	1	1	0			
$s^{(3)}$	0	1	0	0	0	1		
$2s^{(3)}$	1	0	0	0	1			
$+(-2^4d)$	1	0	1	1	0			
$s^{(4)}$	0	0	1	1	1			
s						0	1	1
q						1	0	1

No overflow, since:
 $(0111)_{\text{two}} < (1010)_{\text{two}}$

Positive, so set $q_3 = 1$


Negative, so set $q_2 = 0$
 and restore

Positive, so set $q_1 = 1$

Positive, so set $q_0 = 1$

Restoring Bit-Serial Hardware Divider (3/3)

Can be shared together

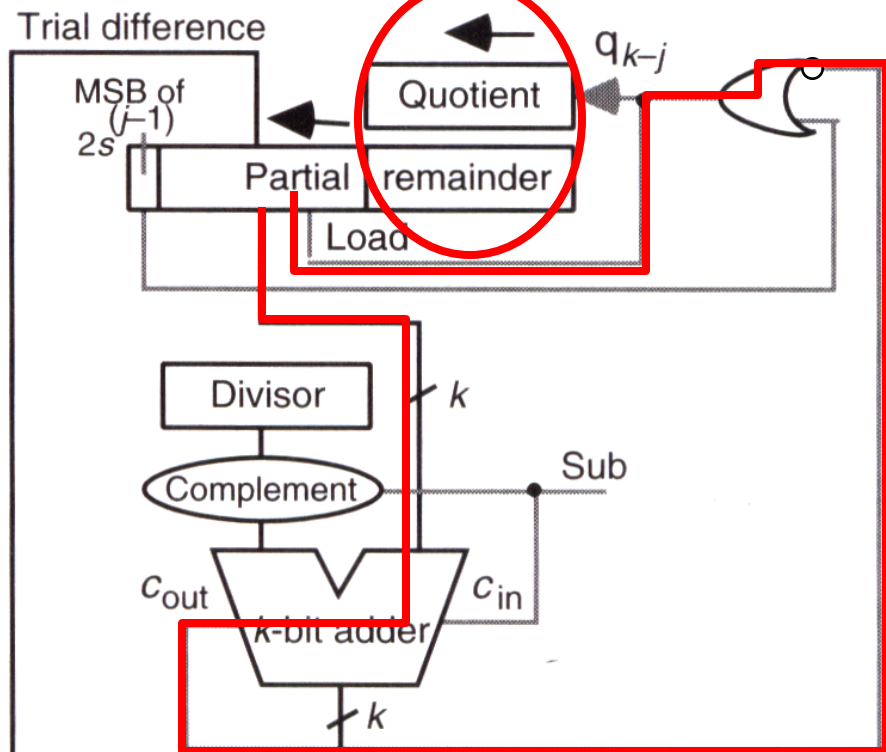

Critical path

Z	0	1	1	1	0	1	0	1
2^4d	0	1	0	1	0			
-2^4d	1	0	1	1	0			
$s(0)$	0	0	1	1	1	0	1	0
$2s(0)$	0	1	1	1	0	1	0	1
$+(-2^4d)$	1	0	1	1	0			
$s(1)$	0	0	1	0	0	1	0	1
$2s(1)$	0	1	0	0	1	0	1	
$+(-2^4d)$	1	0	1	1	0			
$s(2)$	1	1	1	1	1	0	1	
$s(2) = 2s(1)$	0	1	0	0	1	0	1	
$2s(2)$	1	0	0	1	0	1		
$+(-2^4d)$	1	0	1	1	0			
$s(3)$	0	1	0	0	0	1		
$2s(3)$	1	0	0	0	1			
$+(-2^4d)$	1	0	1	1	0			
$s(4)$	0	0	1	1	1			
s						0	1	1
q						1	0	1

No overflow, since:
 $(0111)_{\text{two}} < (1010)_{\text{two}}$

Positive, so set $q_3 = 1$

Negative, so set $q_2 = 0$
 and restore

Positive, so set $q_1 = 1$


Positive, so set $q_0 = 1$



Nonrestoring Bit-Serial Hardware Divider (1/4)

- Always store $u-2^k d$ back to the register
- If the value q in this stage is 1 \rightarrow correct!
 - Next stage: $2(u-2^k d)-2^k d=2u-3 \times 2^k d$
- If the value q in this stage is 0 \rightarrow incorrect!
 - Next stage should be: $2u-2^k d$
 - Is equal to $2(u-2^k d)+2^k d$
- Always store the result of trail difference
 - If $q=1 \rightarrow$ use subtraction; if $q=0 \rightarrow$ use addition
- Can reduce critical path

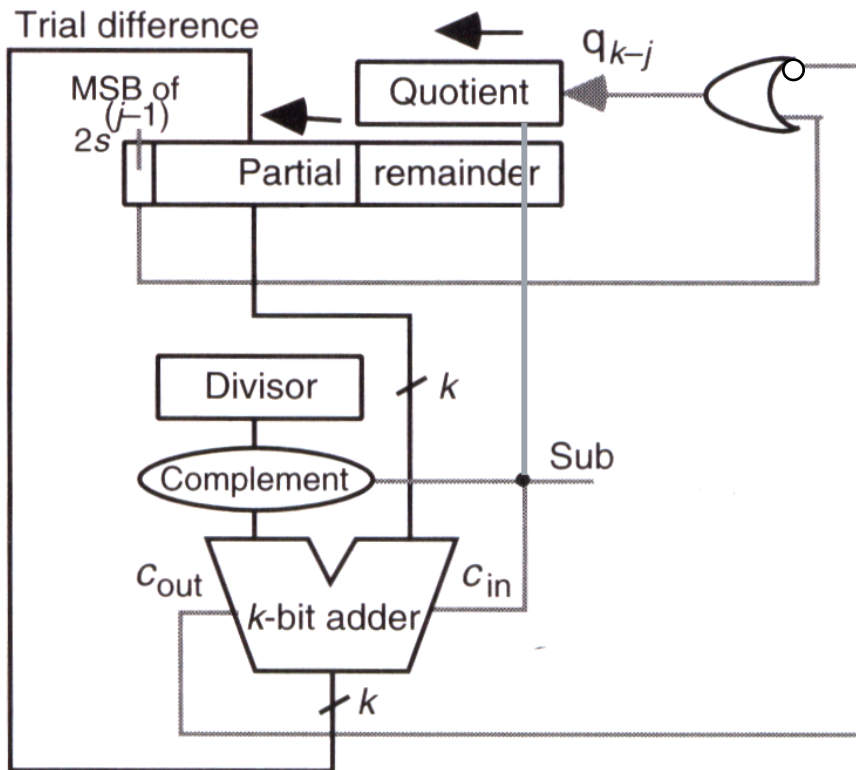Nonrestoring Bit-Serial Hardware Divider (2/4)



z	0	1	1	1	0	1	0	1
2^4d	0	1	0	1	0			
-2^4d	1	0	1	1	0			
$s(0)$	0	0	1	1	1	0	1	0
$2s(0)$	0	1	1	1	0	1	0	1
$+(-2^4d)$	1	0	1	1	0			
$s(1)$	0	0	1	0	0	1	0	1
$2s(1)$	0	1	0	0	1	0	1	
$+(-2^4d)$	1	0	1	1	0			
$s(2)$	1	1	1	1	1	0	1	
$2s(2)$	1	1	1	1	0	1		
$+2^4d$	0	1	0	1	0			
$s(3)$	0	1	0	0	0	1		
$2s(3)$	1	0	0	0	1			
$+(-2^4d)$	1	0	1	1	0			
$s(4)$	0	0	1	1	1			
s						0	1	1
q						1	0	1

No overflow, since:
 $(0111)_{two} < (1010)_{two}$

Positive,
so subtract

Positive, so set $q_3 = 1$
and subtract


Negative, so set $q_2 = 0$
and add

Positive, so set $q_1 = 1$
and subtract

Positive, so set $q_0 = 1$



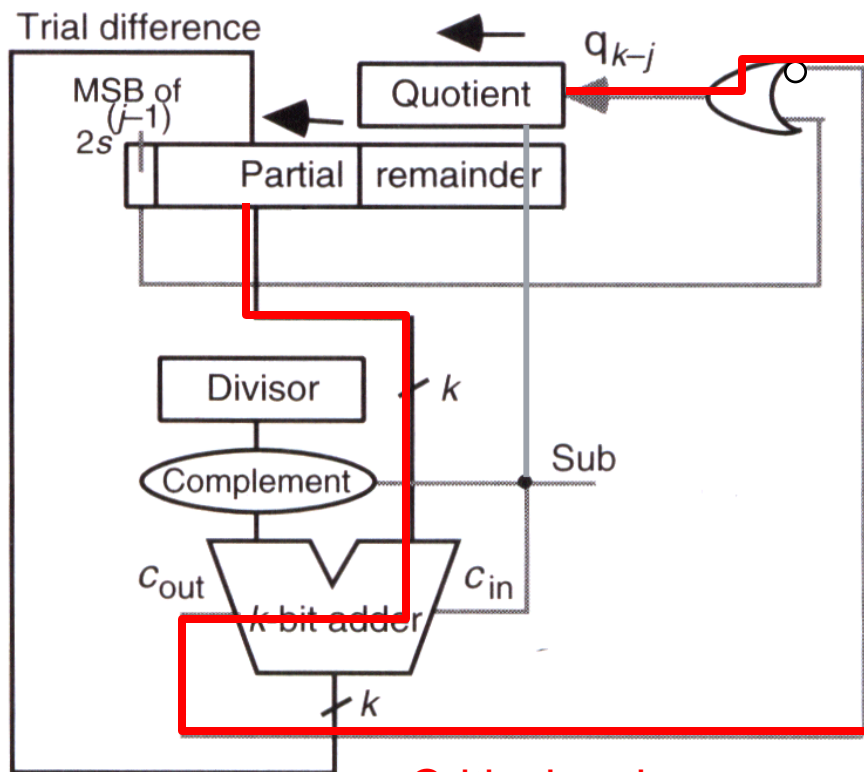Nonrestoring Bit-Serial Hardware Divider (3/4)



Critical path

z	0	1	1	1	0	1	0	1
2^4d	0	1	0	1	0			
-2^4d	1	0	1	1	0			
$s(0)$	0	0	1	1	1	0	1	0
$2s(0)$	0	1	1	1	0	1	0	1
$+(-2^4d)$	1	0	1	1	0			
$s(1)$	0	0	1	0	0	1	0	1
$2s(1)$	0	1	0	0	1	0	1	
$+(-2^4d)$	1	0	1	1	0			
$s(2)$	1	1	1	1	1	0	1	
$2s(2)$	1	1	1	1	0	1		
$+2^4d$	0	1	0	1	0			
$s(3)$	0	1	0	0	0	1		
$2s(3)$	1	0	0	0	1			
$+(-2^4d)$	1	0	1	1	0			
$s(4)$	0	0	1	1	1			
s						0	1	1
q						1	0	1

No overflow, since:
 $(0111)_{two} < (1010)_{two}$

Positive,
so subtract

Positive, so set $q_3 = 1$
and subtract


Negative, so set $q_2 = 0$
and add

Positive, so set $q_1 = 1$
and subtract


Positive, so set $q_0 = 1$



 Nonrestoring Bit-Serial Hardware Divider (4/4)



(a) Restoring.

 

(b) Nonrestoring.



Division by Constants (1/2)

- Use **lookup table** + constant multiplier
- Exploit the following equations
 - Consider **odd divisor** only since even divisor can be performed by first dividing by an odd integer and then shifting the result
 - For an odd integer d , there exists an odd integer m such that $d \times m = 2^n - 1$



Division by Constants (2/2)

□
$$\frac{1}{d} = \frac{m}{2^n - 1} = \frac{m}{2^n(1 - 2^{-n})} = \frac{m}{2^n} (1 + 2^{-n})(1 + 2^{-2n})(1 + 2^{-4n}) \dots$$

□ For example, for 24-bit precision:

$$d = 5, \Rightarrow m = 3, n = 4$$

Easy for hardware implementation


$$\frac{z}{5} = \frac{3z}{2^4 - 1} = \frac{3z}{16(1 - 2^{-4})} = \frac{3z}{16} (1 + 2^{-4})(1 + 2^{-8})(1 + 2^{-16})$$

Next term $(1 + 2^{-32})$ does not contribute anything to 24-bit precision

Array Divider (1/2)


Restoring array divider

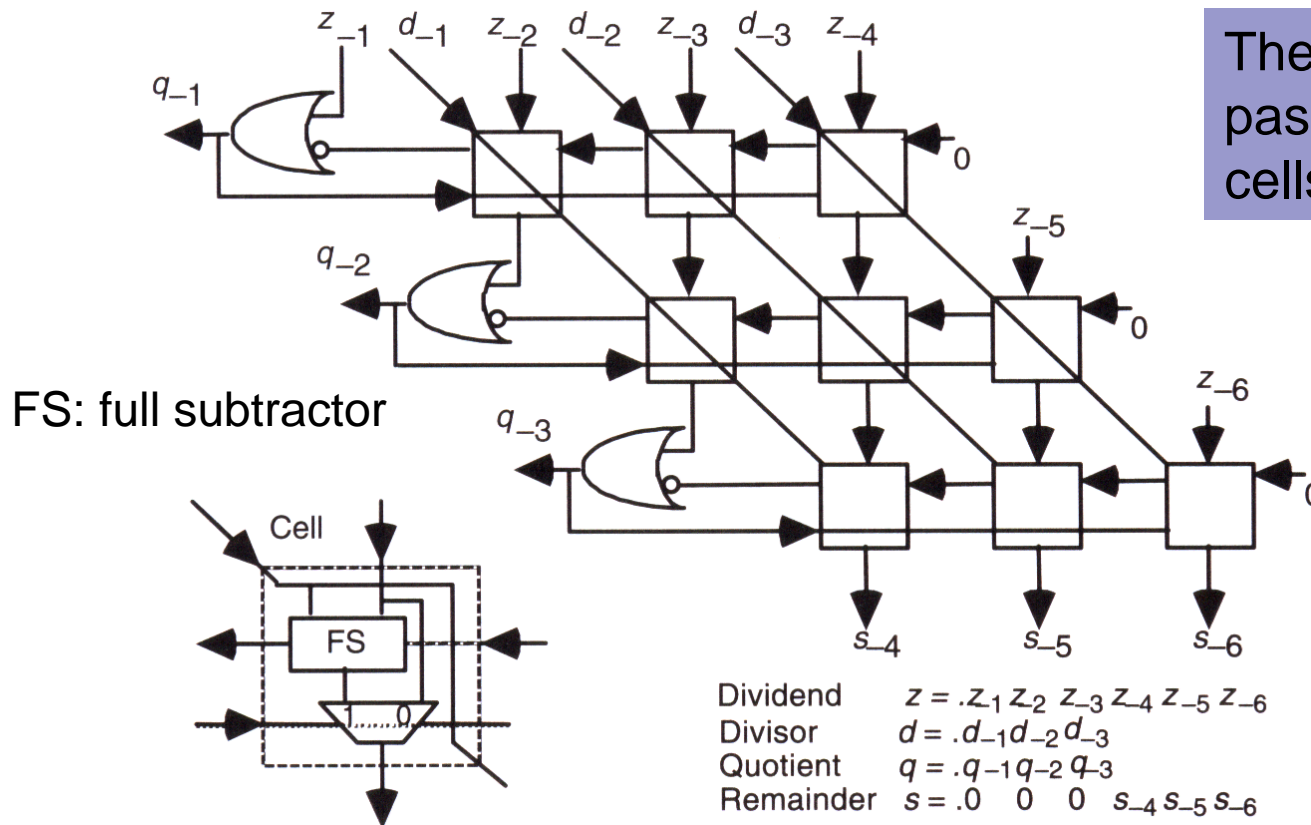The critical path passes through all k^2 cells



Array Divider (2/2)

■ Nonrestoring array divider

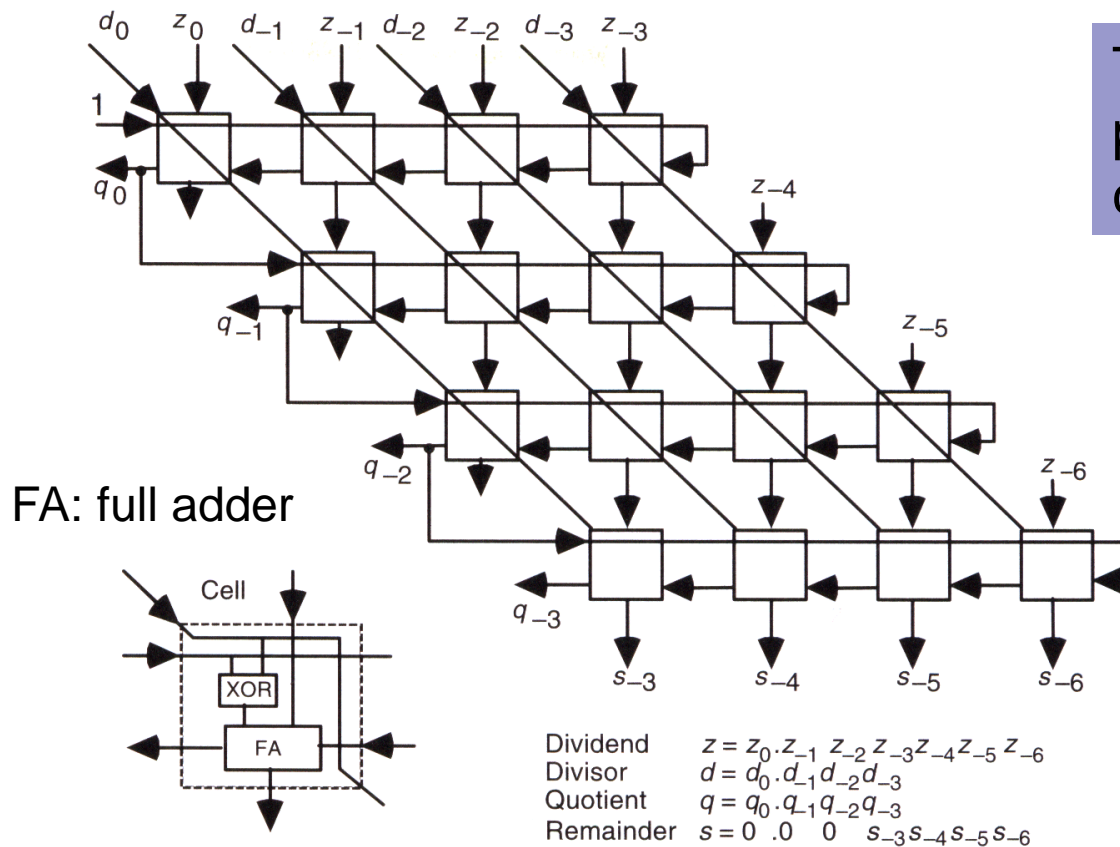

The critical path passes through all k^2 cells



Distributed Arithmetic (1/7)

- Most DSP algorithms involve sum-of-products (inner products)

$$\mathbf{y} = \mathbf{a} \cdot \mathbf{x} = \sum_{i=1}^N \mathbf{a}_i \mathbf{x}_i$$

Fixed coefficient

- **Distributed arithmetic (DA)** is an efficient procedure for computing inner products between a fixed and a variable data vector



Distributed Arithmetic (2/7)

$$y = \sum_{i=1}^N \mathbf{a}_i \left[-x_{i0} + \sum_{k=1}^{W_d-1} x_{ik} 2^{-k} \right]$$

$$y = - \sum_{i=1}^N \mathbf{a}_i x_{i0} + \sum_{k=1}^{W_d-1} \left[\sum_{i=1}^N \mathbf{a}_i x_{ik} \right] 2^{-k}$$


$$y = -F_0(x_{10}, x_{20}, \dots, x_{N0}) + \sum_{k=1}^{W_d-1} F_k(x_{1k}, x_{2k}, \dots, x_{Nk}) 2^{-k}$$

where $F_k(x_{1k}, x_{2k}, \dots, x_{Nk}) = \sum_{i=1}^N \mathbf{a}_i x_{ik}$

Put F_k in ROM

Distributed Arithmetic (3/7)
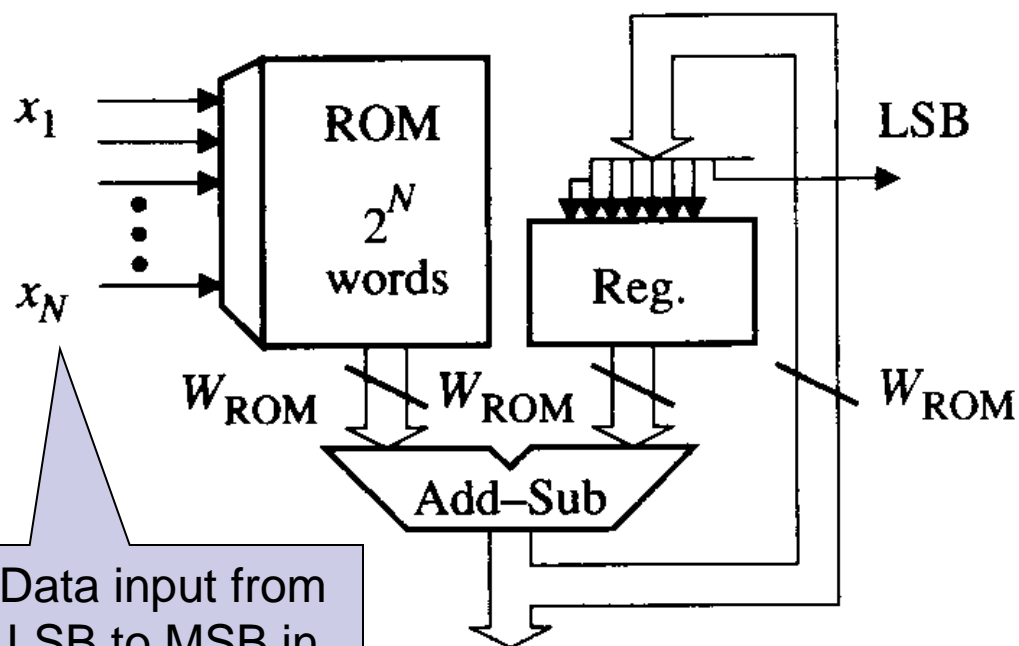
$$y = (((\dots((0 + F_{W_d - 1})2^{-1} + F_{W_d - 2})2^{-1} + \dots + F_2)2^{-1} + F_1)2^{-1} - F_0$$



Data input from LSB to MSB in bit-serial

- DA can be implemented with a ROM and a shift-accumulator
- The computation time: W_d cycles
- Word length of ROM: $W_{ROM} \leq W_C + \log_2(N)$



Distributed Arithmetic (4/7)

■ Example

□ $y = a_1x_1 + a_2x_2 + a_3x_3$

□ $a_1 = (0.0100001)_{2C}$

□ $a_2 = (0.1010101)_{2C}$

□ $a_3 = (1.1110101)_{2C}$

- (a) The table? (b) The word length of the shift-accumulator?



Distributed Arithmetic (5/7)

■ Ans:

□ (a)


$x_1 x_2 x_3$	F_k	F_k	F_k
0 0 0	0	0.0000000	0.0000000
0 0 1	a_3	1.1110101	0.0859375
0 1 0	a_2	0.1010101	0.6640625
0 1 1	$a_2 + a_3$	0.1001010	0.5781250
1 0 0	a_1	0.0100001	0.2578125
1 0 1	$a_1 + a_3$	0.0010110	0.1718750
1 1 0	$a_1 + a_2$	0.1110110	0.9218750
1 1 1	$a_1 + a_2 + a_3$	0.1101011	0.8359375

□ (b) Word length=7 bits + 1 bit (sign bit) +1 bit (guard bit) = 9 bits

$$|y| = (((...((0 + F_{max})2^{-1} + F_{max})2^{-1} + ... + F_{max})2^{-1} + F_{max})2^{-1} \leq F_{max}$$


Distributed Arithmetic (6/7)

- Example: linear-phase FIR filter

 


Distributed Arithmetic (7/7)

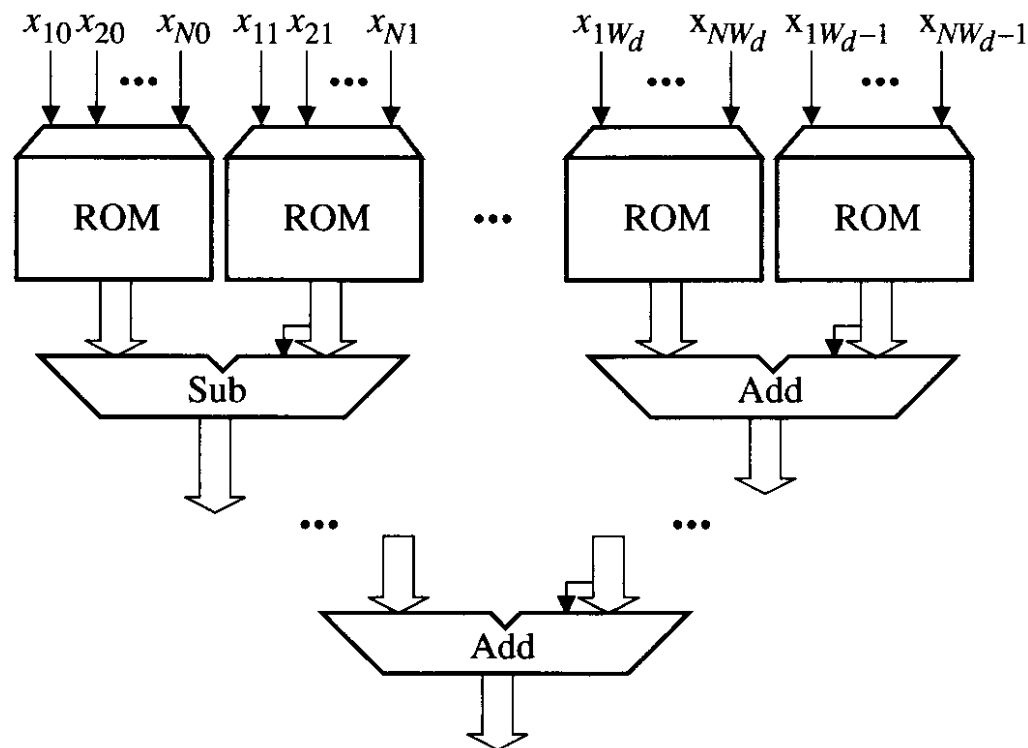- Parallel implementation of distributed arithmetic




Shift-Accumulator (1/4)

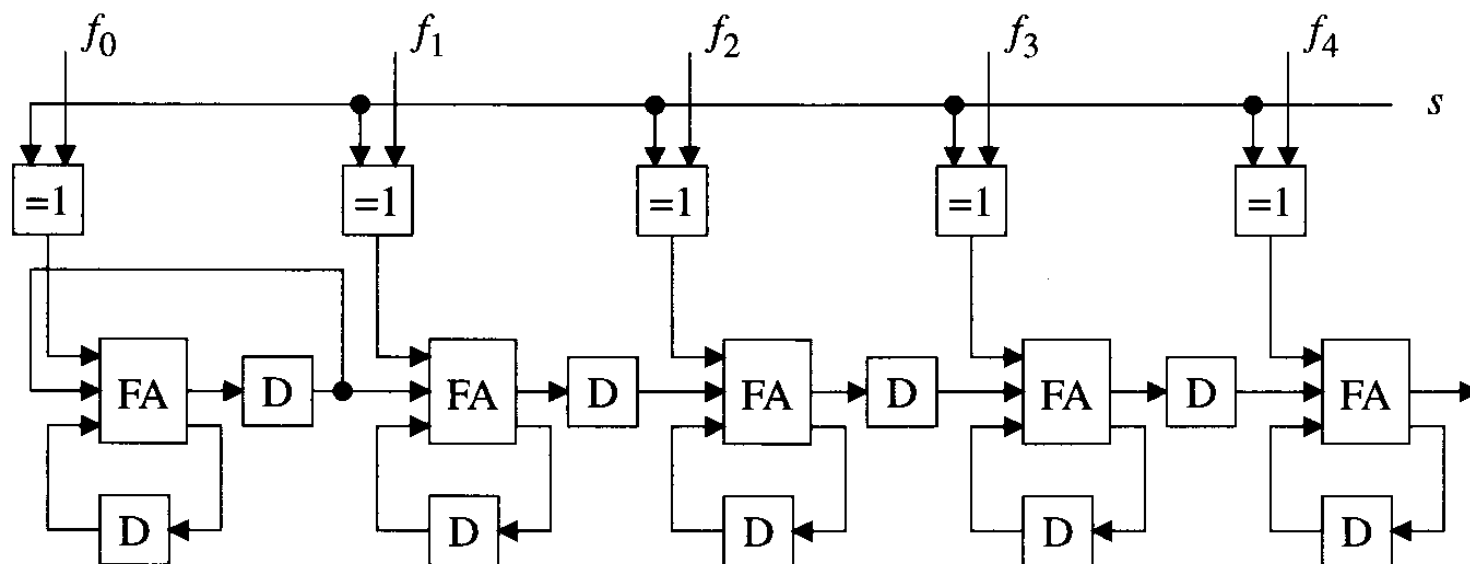

- The number of cycles for one inner product is $W_d + W_{ROM}$
 - First W_d cycles: input data
 - Last W_{ROM} cycles: shift out the results


Shift-Accumulator (2/4)

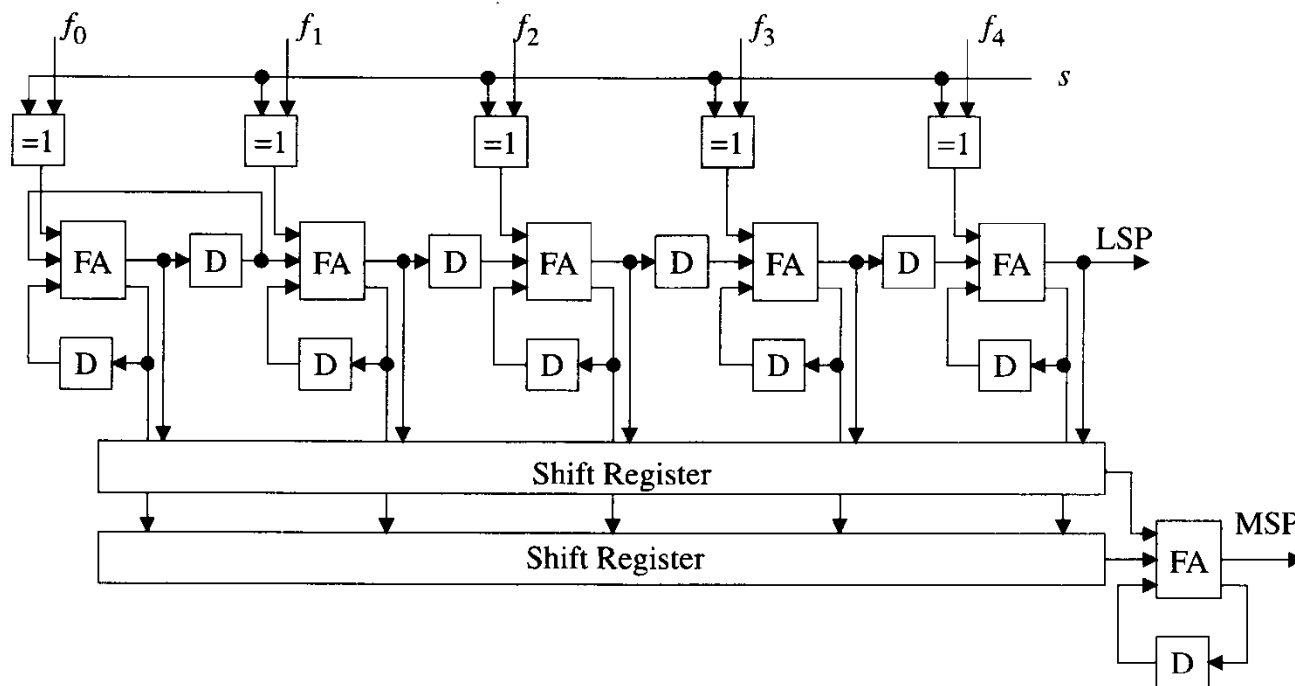- Shift-accumulator augmented with two shift registers



Shift-Accumulator (4/4)

■ Detailed architecture

 


Reducing the Memory Size (1/4)

■ Method 1: memory partition

□ $2 * 2^{N/2} < 2^N$

□ Ex: $2 * 2^5 = 64 < 2^{10} = 1024$

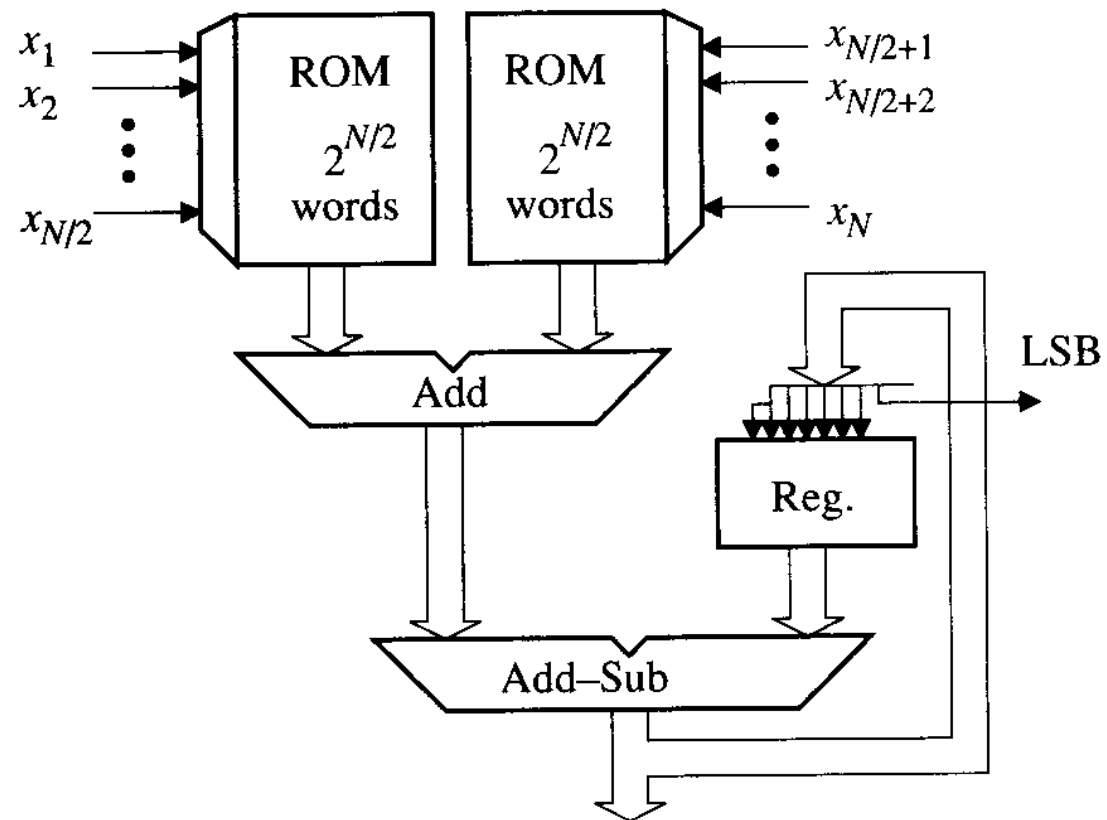



Reducing the Memory Size (2/4)

■ Method 2: memory coding

$$x = \frac{1}{2}[x - (-x)]$$

$$= \frac{1}{2} \left[-x_0 + \sum_{k=1}^{W_d-1} x_k 2^{-k} - \left(-\bar{x}_0 + \sum_{k=1}^{W_d-1} \bar{x}_k 2^{-k} + 2^{-(W_d-1)} \right) \right]$$

$$= -(x_0 - \bar{x}_0) 2^{-1} + \sum_{k=1}^{W_d-1} (x_k - \bar{x}_k) 2^{-k-1} - 2^{-W_d}$$

$$y = \sum_{k=1}^{W_d-1} F_k(x_{1k}, \dots, x_{Nk}) 2^{-k-1} - F_0(x_{10}, \dots, x_{N0}) 2^{-1} + F(0, \dots, 0) 2^{-W_d}$$

$$\text{where } F_k(x_{1k}, x_{2k}, \dots, x_{Nk}) = \sum_{i=1}^N \mathbf{a}_i (x_k - \bar{x}_k)$$

Reducing the Memory Size (3/4)

$$u_1 = x_1 \otimes x_2$$

$$A/S = x_1 \otimes x_{\text{sign-bit}}$$


$$u_2 = x_1 \otimes x_3$$

Complement



x_1	x_2	x_3	F_k	u_1	u_2	A/S
0	0	0	$-a_1 - a_2 - a_3$	0	0	A
0	0	1	$-a_1 - a_2 + a_3$	0	1	A
0	1	0	$-a_1 + a_2 - a_3$	1	0	A
0	1	1	$-a_1 + a_2 + a_3$	1	1	A
1	0	0	$+a_1 - a_2 - a_3$	1	1	S
1	0	1	$+a_1 - a_2 + a_3$	1	0	S
1	1	0	$+a_1 + a_2 - a_3$	0	1	S
1	1	1	$+a_1 + a_2 + a_3$	0	0	S

Reducing the Memory Size (4/4)

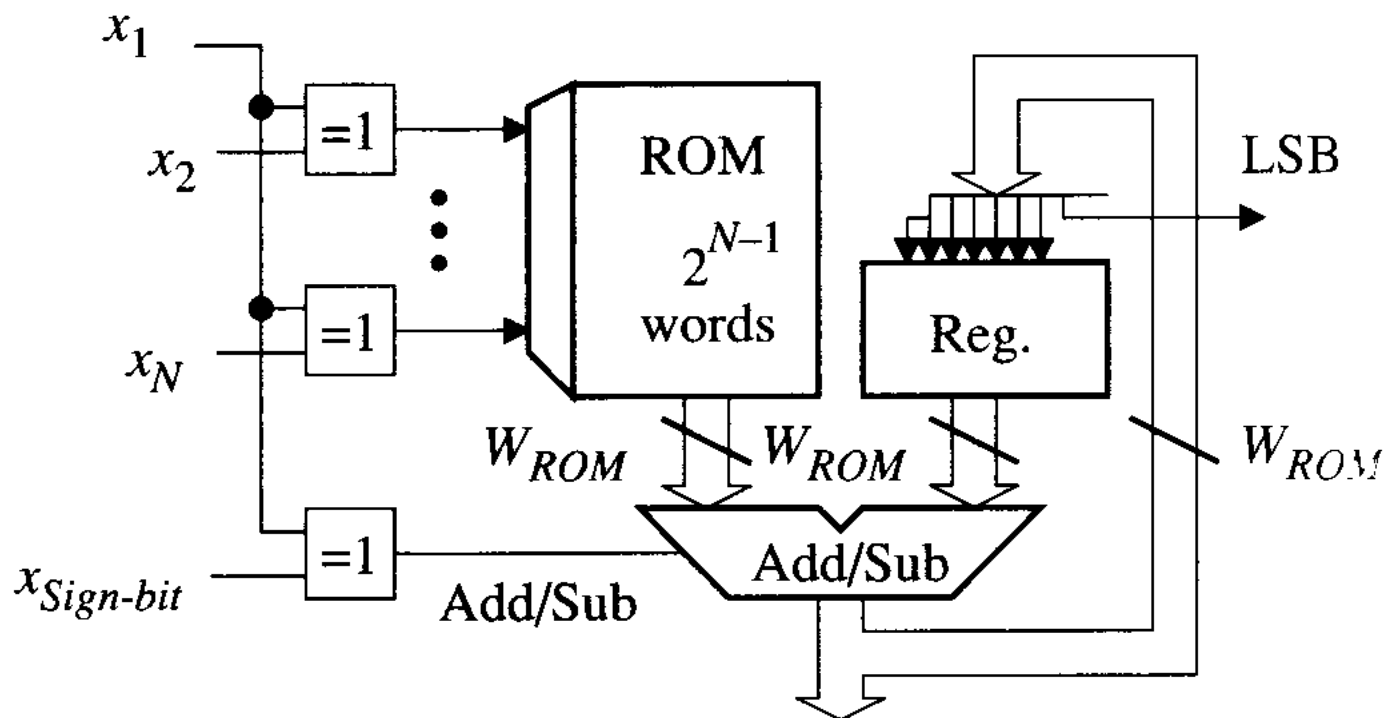



CORDIC


Major reference:

- [1] A.-Y. Wu, "CORDIC," Slides of *Advanced VLSI*
- [2] Y. H. Hu, "CORDIC-based VLSI architectures for digital signal processing," *IEEE Signal Processing Magazine*, pp. 16—35, July 1992.
- [3] J. E. Volder, "The Birth of CORDIC," *J. VLSI Signal Processing*, vol.25, pp. 101—105, 2000.


■ CORDIC (**CO**ordinate **R**otation **D**igital **C**omputer)

- An **iterative arithmetic algorithm** introduced by Volder in 1956
- Can handle many elementary functions, such as trigonometric, exponential, and logarithm **with only shift-and-add** arithmetic
- For these functions CORDIC based architecture is much efficient than multiplier and accumulator (MAC) based architecture
- Suitable for transformations and matrix based filters


The Birth of CORDIC

 

B-58 Supersonic Bomber

 

CORDIC I

 


CORDIC II

Simple Concepts of CORDIC

(1/2)


- Originally, CORDIC is invented to deal with rotation problem with shift-and-add arithmetic
 
$$\begin{bmatrix} x' \\ y' \end{bmatrix} = \begin{bmatrix} \cos \theta & -\sin \theta \\ \sin \theta & \cos \theta \end{bmatrix} \begin{bmatrix} x \\ y \end{bmatrix}$$



Simple Concepts of CORDIC (2/2)

 - How to make it with shift-and-add?
- Decompose the desired rotation angle into small rotation angles (micro-rotation)
- Rotate finite times (by “elementary angles” $\{a_i \mid 0 \leq i \leq n-1\}$) to achieve the desired rotation θ





Conventional CORDIC Algorithm (1/2)

$$\begin{bmatrix} x(i+1) \\ y(i+1) \end{bmatrix} = \begin{bmatrix} \cos a_i & -\sin a_i \\ \sin a_i & \cos a_i \end{bmatrix} \begin{bmatrix} x(i) \\ y(i) \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} x(i+1) \\ y(i+1) \end{bmatrix} = \cos a_i \begin{bmatrix} 1 & -\tan a_i \\ \tan a_i & 1 \end{bmatrix} \begin{bmatrix} x(i) \\ y(i) \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} x(i+1) \\ y(i+1) \end{bmatrix} = \cos a_i \begin{bmatrix} 1 & -2^{-i} \\ 2^{-i} & 1 \end{bmatrix} \begin{bmatrix} x(i) \\ y(i) \end{bmatrix}$$

$$a_i = \tan^{-1} 2^{-i}, \cos a_i = \frac{1}{\sqrt{1+2^{-2i}}}$$

Conventional CORDIC Algorithm (2/2)


$$\begin{bmatrix} x' \\ y' \end{bmatrix} = \begin{bmatrix} \cos \theta & -\sin \theta \\ \sin \theta & \cos \theta \end{bmatrix} \begin{bmatrix} x \\ y \end{bmatrix}$$

$$= S \times \begin{bmatrix} 1 & -\mu_0 2^{-0} \\ \mu_0 2^{-0} & 1 \end{bmatrix} \times \dots$$

$$\times \begin{bmatrix} 1 & -\mu_i 2^{-i} \\ \mu_i 2^{-i} & 1 \end{bmatrix} \times \dots \times \begin{bmatrix} 1 & -\mu_{n-1} 2^{-(n-1)} \\ \mu_{n-1} 2^{-(n-1)} & 1 \end{bmatrix} \times \begin{bmatrix} x \\ y \end{bmatrix}$$

$$\text{Scaling factor: } S = \frac{1}{\prod_{i=0}^{n-1} \sqrt{1 + \mu_i^2 2^{-2i}}}$$

Mode of rotation: $\mu_i \in \{-1, 1\}$

 

$$\theta_0 = 1 \cdot \tan^{-1} 2^{-0} = \mu_0 a_0$$

$$\theta_1 = -1 \cdot \tan^{-1} 2^{-1} = \mu_1 a_1$$

$$\theta_2 = 1 \cdot \tan^{-1} 2^{-2} = \mu_2 a_2$$

Can be implemented
with shift-and-add
arithmetic



Generalized CORDIC (1/2)

- Target: $\theta = \sum_{i=0}^{n-1} \mu_i a_m(i)$
- i -th elementary rotation angle is defined by

$$a_m(i) = \frac{1}{\sqrt{m}} \tan^{-1} \left[\sqrt{m} 2^{-s(m,i)} \right] = \begin{cases} -2^{s(0,i)} & m \rightarrow 0 \text{ Linear coordinate} \\ \tan^{-1} 2^{-s(1,i)} & m = 1 \text{ Circular coordinate} \\ \tanh^{-1} 2^{-s(-1,i)} & m = -1 \text{ Hyperbolic coordinate} \end{cases}$$


norm of a vector $[x \ y]^T$ is $\sqrt{x^2 + my^2}$

$\mu_i \in \{-1, 1\}$: mode of rotation


$s(m, i)$: non - decreasing integer shift sequence

Generalized CORDIC (2/2)


Circular Rotation
($m=1$)

 

Linear Rotation
($m > 0$)

 

Hyperbolic Rotation
($m = -1$)

 



CORDIC Algorithm

Initiation : Given $x(0), y(0), z(0)$

For $i = 0$ to $n - 1$, Do

/* CORDIC iteration equation */

$$\begin{bmatrix} x(i+1) \\ y(i+1) \end{bmatrix} = \begin{bmatrix} 1 & -\mu_i 2^{-s(m,i)} \\ \mu_i 2^{-s(m,i)} & 1 \end{bmatrix} \begin{bmatrix} x(i) \\ y(i) \end{bmatrix}$$

/* Angle updating equation */

$$z(i+1) = z(i) - \mu_i a_m(i)$$

End i - loop

/* Scaling operation (required for $m = \pm 1$ only) */

$$\begin{bmatrix} x_f \\ y_f \end{bmatrix} = \frac{1}{K_m(n)} \cdot \begin{bmatrix} x(n) \\ y(n) \end{bmatrix} = \frac{1}{\prod_{i=0}^{n-1} \sqrt{1 + m\mu_i^2 2^{-2s(m,i)}}} \cdot \begin{bmatrix} x(n) \\ y(n) \end{bmatrix}$$

Remained problems:

μ_i

$s(m, i)$

Scaling

Mode of Operation (1/2)

■ Vector rotation mode (θ is given)

$$z(0) = \theta$$


After n iterations, the total angle rotated is :

$$z(0) - z(n) = \theta - z(n) = \sum_{i=0}^{n-1} \mu_i a_m(i)$$

we want to make $|z(n)| \rightarrow 0$

$$\mu_i = \text{sign of } z(i)$$

 - For many DSP problems, θ is know in advance, and sequence $\{\mu_i\}$ can be stored instead





Mode of Operation (2/2)

- Angle accumulation mode (θ is not given)

- The objective is to rotate the given initial vector $[x(0) \ y(0)]^T$ back to the x-axis

set $z(0) = 0$

$$\mu_i = -\text{sign of } x(i) \cdot y(i)$$

- Summary

$$\mu_i = \begin{cases} \text{sign of } z(i) & \text{Vector rotation mode} \\ -\text{sign of } x(i) \cdot y(i) & \text{Angle accumulation mode} \end{cases}$$



Shift Sequence

- Usually defined in advance
- Walther has proposed a set of shift sequence for each of the three coordinate systems
 - For $m=0$ or 1 , $s(m,i)=i$
 - For $m=-1$, $s(-1, i)=1, 2, 3, 4, 4, 5, \dots, 12, 13, 13, 14, \dots$




Scaling Operation $\frac{1}{K_m(n)}$

- Significant computation overhead of CORDIC
- Fortunately, since $|\mu_i| = 1$, and assume $\{s(m, i)\}$ is given, $K_m(n)$ can be computed in advance
- Two approaches to compute scaling


□ CSD representation $\frac{1}{K_m(n)} = \sum_{p=1}^P \kappa_p 2^{-i_p}$ $\kappa_q = \pm 1$

□ Project of factors $\frac{1}{K_m(n)} = \prod_{q=1}^Q (1 + \kappa_q 2^{-i_q}) + \varepsilon_q$

Basic CORDIC Processor (1/3)

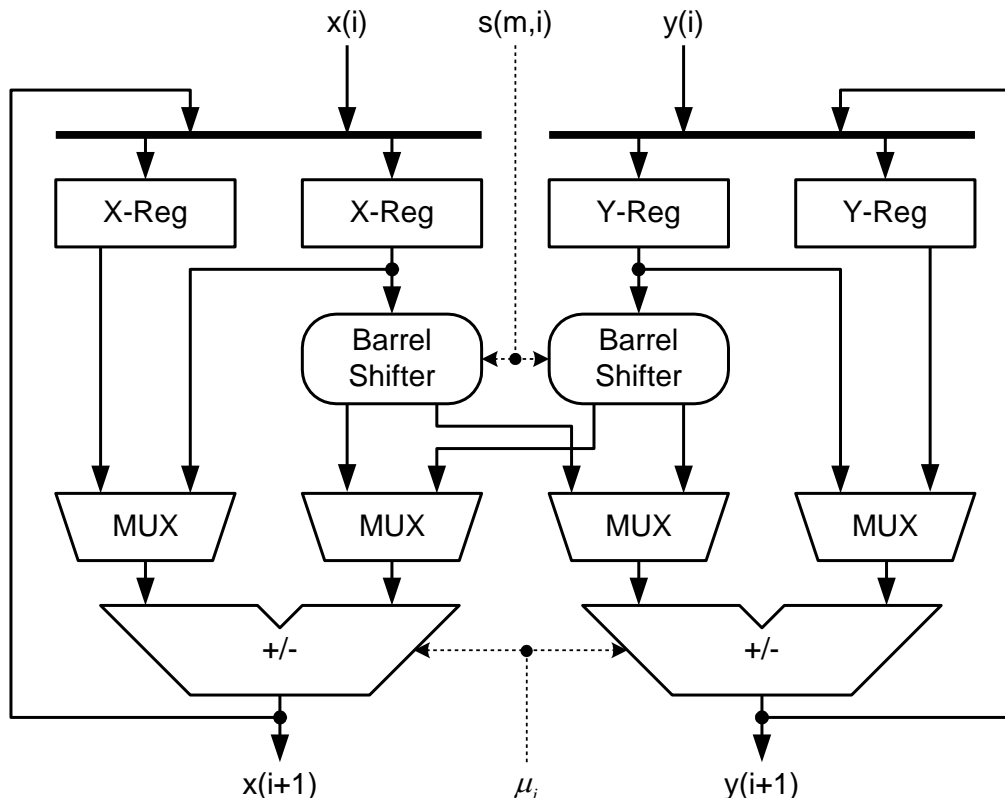


For CORDIC Iteration and Scaling

 

For Angle Update

Basic CORDIC Processor (2/3)


CORDIC Iteration

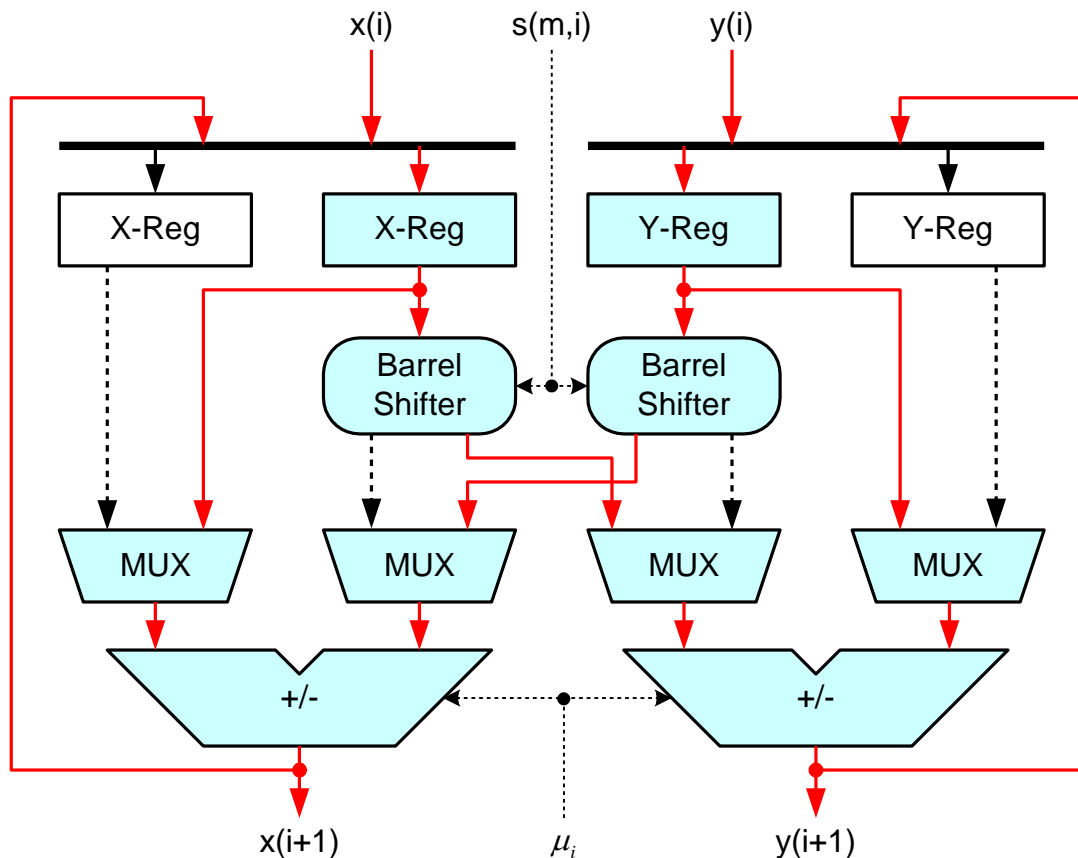

$$\begin{bmatrix} x(i+1) \\ y(i+1) \end{bmatrix} = \begin{bmatrix} 1 & -\mu_i 2^{-s(m,i)} \\ \mu_i 2^{-s(m,i)} & 1 \end{bmatrix} \begin{bmatrix} x(i) \\ y(i) \end{bmatrix}$$

Basic CORDIC Processor (3/3)

Scaling

 

$$I: \frac{1}{K_m(n)} = \sum_{p=1}^P \kappa_p 2^{-i_p}$$

$$II: \frac{1}{K_m(n)} = \prod_{q=1}^Q (1 + \kappa_q 2^{-i_q})$$

Given $x'(0) = x(n)$, $y'(0) = y(n)$

Type I:


$$\begin{cases} x'(p+1) = x'(p) + \kappa_p 2^{-i_p} x(n) \\ y'(p+1) = y'(p) + \kappa_p 2^{-i_p} x(n) \end{cases}$$

Type II:


$$\begin{cases} x'(q+1) = x'(q) + \kappa_q 2^{-i_q} x'(q) \\ y'(q+1) = y'(q) + \kappa_q 2^{-i_q} x'(q) \end{cases}$$

Parallel and Pipelined Arrays

 - n stages for CORDIC, and s stages for scaling
- Parallel



- Pipelined

 



Discrete Fourier Transform (DFT) with CORDIC (1/2)

■ DFT

$$Y(K) = X(0)e^{\frac{-j2\pi k \cdot 0}{N}} + X(1)e^{\frac{-j2\pi k \cdot 1}{N}} + \dots + X(N-1)e^{\frac{-j2\pi k \cdot (N-1)}{N}}$$

■ DFT with CORDIC

Initiation : $Y(0, k) = 0$ for $0 \leq k \leq N-1$

For $k = 0$ to $N-1$, Do

For $m = 0$ to $N-1$, Do

$$\begin{bmatrix} Y_r(m+1, k) \\ Y_i(m+1, k) \end{bmatrix} = K_1(n) \cdot \begin{bmatrix} \cos \frac{-2\pi mk}{N} & -\sin \frac{-2\pi mk}{N} \\ \sin \frac{-2\pi mk}{N} & \cos \frac{-2\pi mk}{N} \end{bmatrix} \begin{bmatrix} x_r(m) \\ x_i(m) \end{bmatrix} + \begin{bmatrix} Y_r(m, k) \\ Y_i(m, k) \end{bmatrix}$$

End m - loop

/* Scaling operation */

$$Y(k) = \frac{Y(N, k)}{K_1(n)}$$

End k - loop



Discrete Fourier Transform (DFT) with CORDIC (2/2)

