
## **DSP** in VLSI Design

## Homework (IV)


## **Retiming**

Deadline: Oct. 25

 
- 1. Consider the wave digital filter shown below. Assume that each multiply operation requires 20 ns and each add operation required 10 ns.
  - (a) Calculate the iteration period bound of this filter by inspection.
  - (b) Where is the critical path?
  - (c) Manually pipeline and/or retime this filter to achieve a critical path equal to the iteration period bound.



 - 2. Consider the IIR filter DFG shown in below. Assume that addition and multiplication require 1 and 2 u.t., respectively.
  - (a) By inspection, calculate the iteration bound.
  - (b) Compute the critical path time of the circuit.
  - (c) Pipeline and/or retime this system to achieve a critical path of 2 u.t. Do this by inspection (manually).
  - (d) Pipeline and/or retime this system to achieve sample period of 1 u.t., where Fine-grain retiming is allowed. Do this by inspection (manually).



 - 3. The two IIR filter DFGs shown below are equivalent.
  - (a) Prove the two circuits are equivalent.
  - (b) Transform the left circuit to the right circuit by pipelining and/or retiming.



Please deliver the homework to the TA:

MD-431, 郭品宏, setsunil@media.ee.ntu.edu.tw

除非為程式作業,作業盡量繳交紙本格式,不過要交電子檔也沒關係