



# VLSI Architecture Design ABC

---


Shao-Yi Chien




# Outline

- Pipeline
- Parallel
- Folding
- Unfolding
- Important concepts:
  - scheduling/resource allocation/design space exploration


# An Example: Car Production Line

 

 Cost: 1  
Throughput:  $1/mT$   
Latency:  $mT$



 Cost:  $>1$   
Throughput:  $1/T$   
Latency:  $>mT$




Cost:  $>n$   
Throughput:  $(1/mT)*n$   
Latency:  $>mT$

**Throughput:** how many cars produced in one hour  
**Latency:** how long will it take to produce one car

# Pipelining of Digital Filters (1/3)
 
## ■ FIR filter

$$y(n] = ax(n) + bx(n - 1) + cx(n - 2).$$




□ Critical path:  $T_M + 2T_A$

$$T_{sample} \geq T_M + 2T_A \quad f_{sample} \leq \frac{1}{T_M + 2T_A}$$

# Pipelining of Digital Filters (2/3)


## ■ Pipelined FIR filter

 

$$T_{sample} \geq T_M + T_A \quad f_{sample} \leq \frac{1}{T_M + T_A}$$

# Pipelining of Digital Filters (3/3)

## ■ Schedule

 

Clock	Input	Node 1	Node 2	Node 3	Output
0	$x(0)$	$ax(0) + bx(-1)$	—	—	—
1	$x(1)$	$ax(1) + bx(0)$	$ax(0) + bx(-1)$	$cx(-2)$	$y(0)$
2	$x(2)$	$ax(2) + bx(1)$	$ax(1) + bx(0)$	$cx(-1)$	$y(1)$
3	$x(3)$	$ax(3) + bx(2)$	$ax(2) + bx(1)$	$cx(0)$	$y(2)$

# Pipeline

- Can reduce the critical path to increase the working frequency and sample rate

- $T_M + 2T_A \rightarrow T_M + T_A$



# Drawbacks of Pipelining

- Increasing latency (in cycle)
  - For M-level pipelined system, the number of delay elements in any path from input to output is (M-1) greater than the origin one
- Increase the number of latches (registers)







# How to Do Pipelining?

- Put pipelining latches across any feed-forward cutset of the graph
- Cutset
  - A cutset is a set of edges of a graph such that if these edges are removed from the graph, the graph becomes disjoint
- Feed-forward cutset
  - The data move in the forward direction on all the edges of the cutset

# How to Do Pipelining?

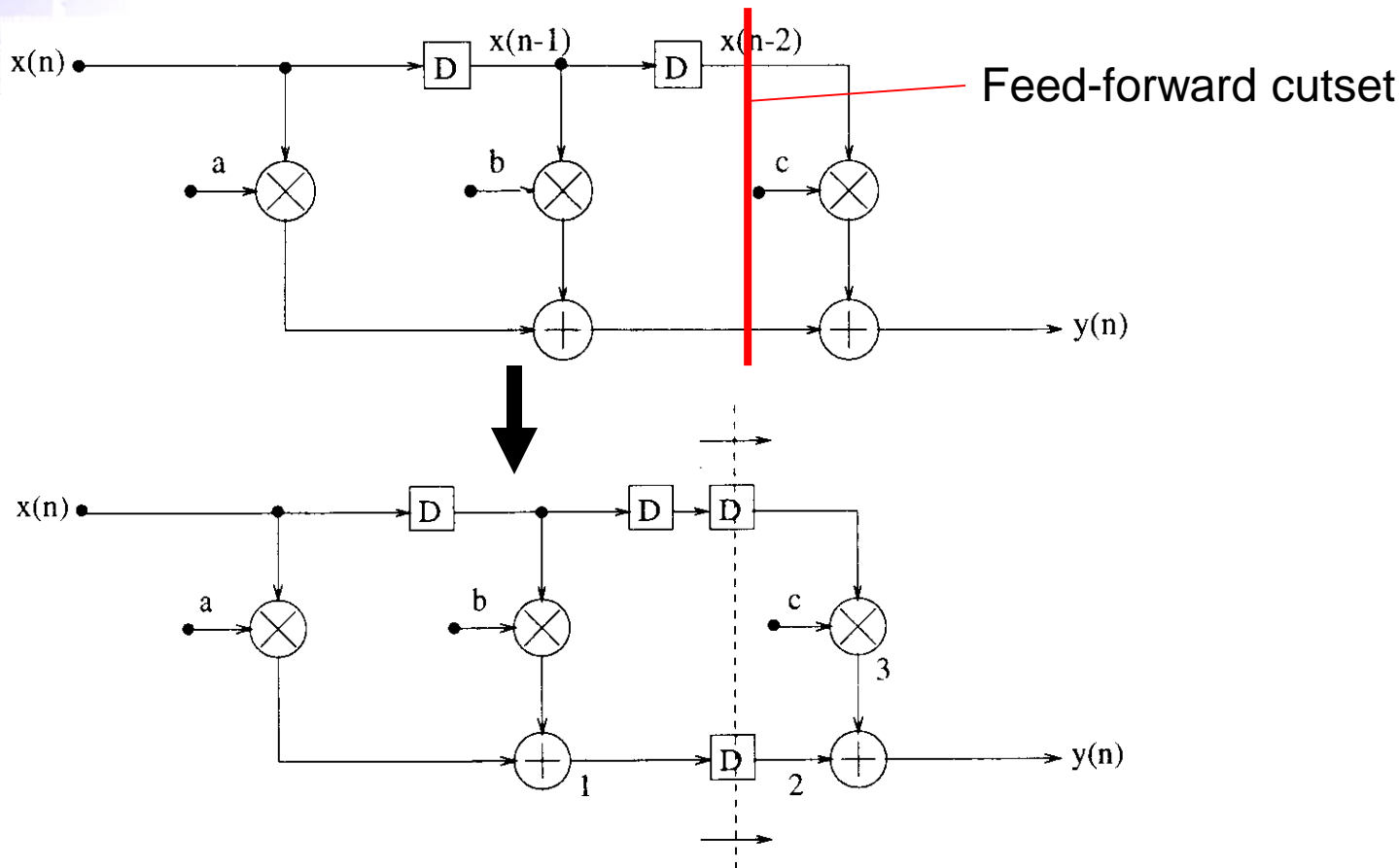

# Fine-Grain Pipelining

 

- Critical path ( $T_M=10$ ,  $T_A=2$ )

- $T_M+2T_A=14$
- $T_M+T_A=12$
- $T_{M1}=6$  or  $T_{M2}+T_A=6$



# Notes for Pipelining (1/2)

- Pipelining is a very simple design technique which can maintain the input output data configuration and sampling frequency
- $T_{\text{clk}} = T_{\text{sample}}$
- Supported in many EDA tools
- Still has some limitations
  - Pipeline bubbles
  - Has some problems for recursive system
  - Introduces large hardware cost for 2-D or 3-D data
  - Communication bound



# Notes for Pipelining (2/2)

- Effective pipelining

- Put pipelining registers on the critical path

- Balance pipelining

- $10 \rightarrow (2+8)$ : critical path=8

- $10 \rightarrow (5+5)$ : critical path=5


# Parallel of Digital Filters (1/5)

- Single-input single-output (SISO) system

$$y(n) = ax(n) + bx(n - 1) + cx(n - 2).$$

- Multiple-input multiple-output (MIMO) system
 
$$\begin{aligned} y(3k) &= ax(3k) + bx(3k - 1) + cx(3k - 2) \\ y(3k + 1) &= ax(3k + 1) + bx(3k) + cx(3k - 1) \quad \text{3-Parallel System!} \\ y(3k + 2) &= ax(3k + 2) + bx(3k + 1) + cx(3k). \end{aligned}$$



Sequential System


3-Parallel System



# Parallel of Digital Filters (2/5)

- Parallel processing, block processing
- Block size ( $L$ ): the number of data to be processed at the same time
- Block delay ( $L$ -slow)
  - A latch is equivalent to  $L$  clock cycles at the sample rate

# Parallel of Digital Filters (3/5)

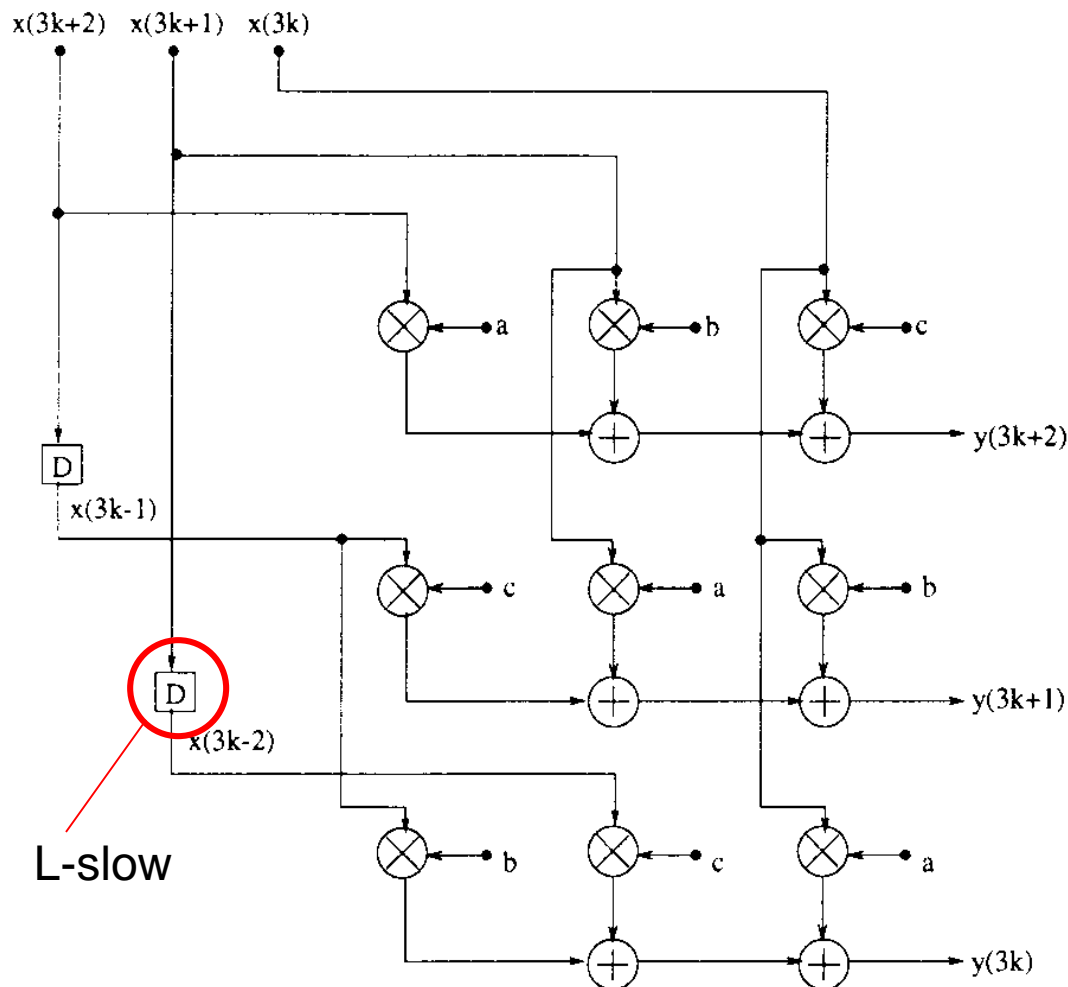

$$T_{clk} \geq T_M + 2T_A$$

The critical path is the same

$$T_{iter} = T_{sample} = \frac{1}{L} T_{clk} \geq \frac{1}{3} (T_M + 2T_A)$$

$T_{clk}$  is not equal to  $T_{sample}$


L-slow






# Parallel of Digital Filters (4/5)


## ■ Whole system

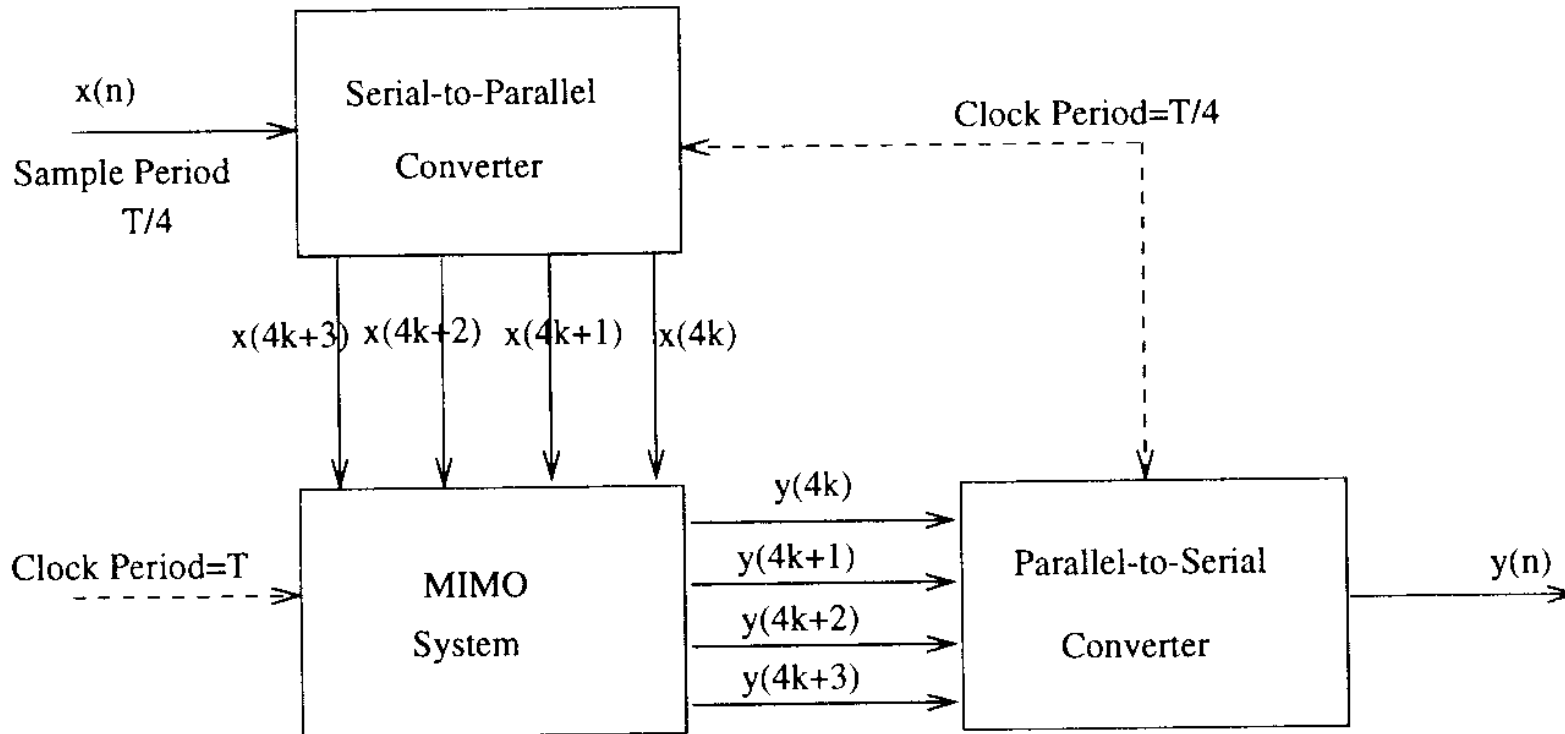

# Parallel of Digital Filters (5/5)

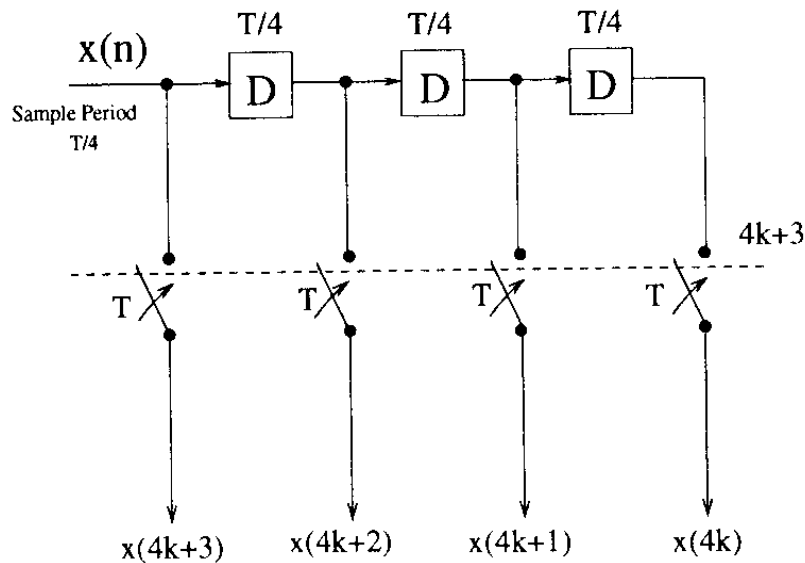


Serial-to-parallel converter

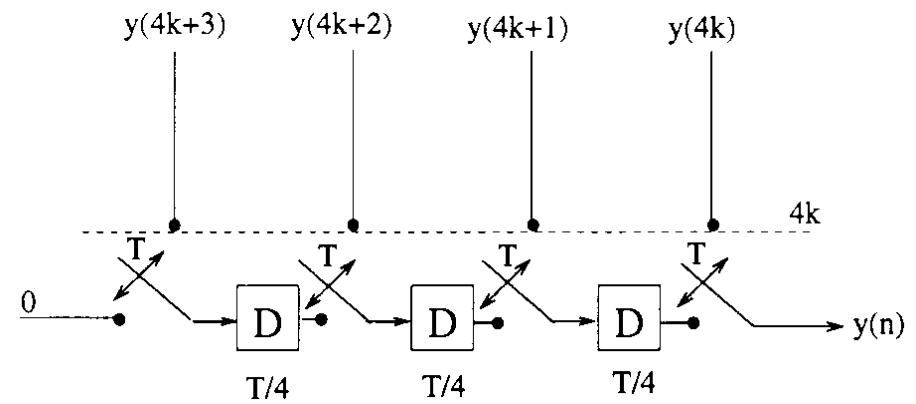

Parallel-to-serial converter

# Pipelining-Parallel Architecture

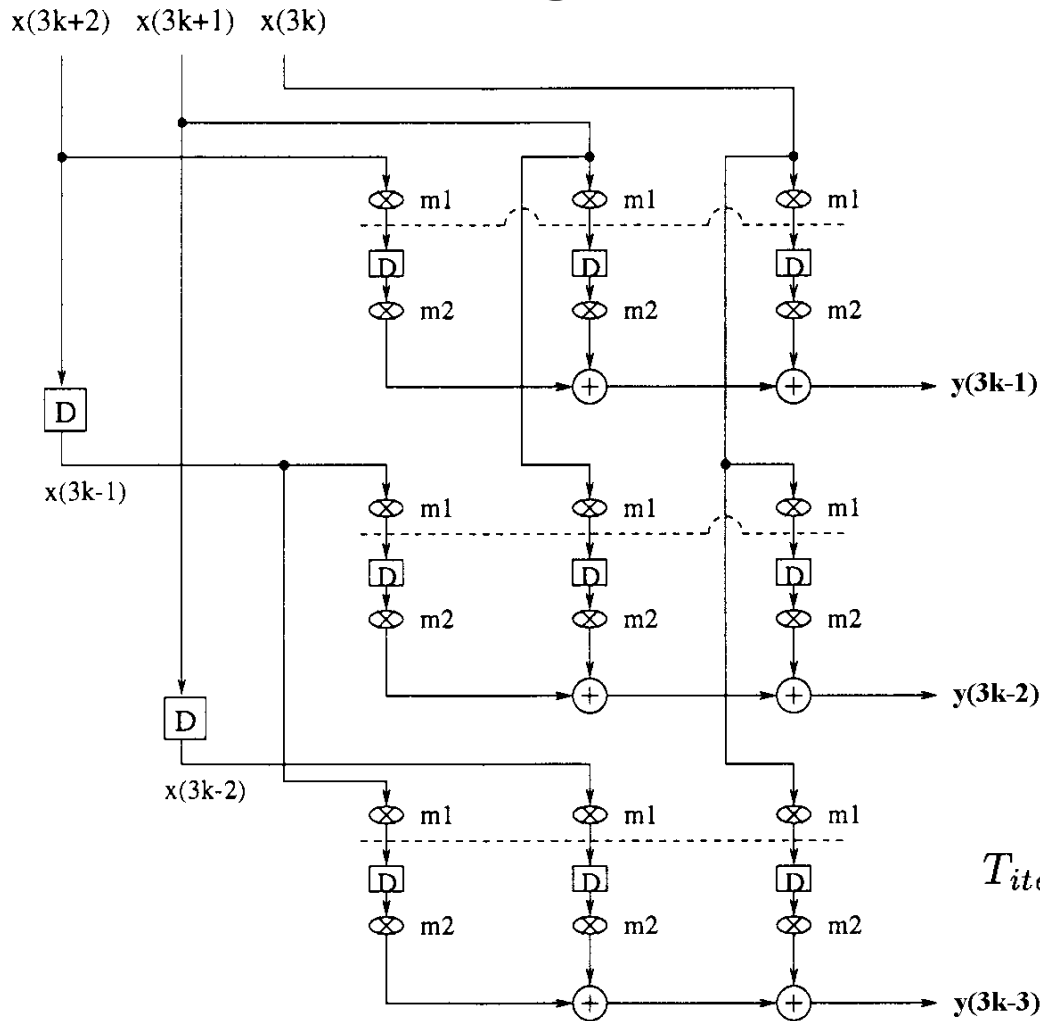

$$T_{iter} = T_{sample} = \frac{1}{LM} T_{clk} = \frac{1}{6} (T_M + 2T_A)$$



# Notes for Parallel Processing

- The input/output data access scheme should be carefully designed, it will cost a lot sometimes
- $T_{\text{clk}} > T_{\text{sample}}$ ,  $f_{\text{clk}} < f_{\text{sample}}$
- Large hardware cost
- Combined with pipelining processing



# Low Power Issues

- Pipelining and parallel processing are also beneficial for low power design

- Propagation delay

$$T_{pd} = \frac{C_{charge} V_0}{k(V_0 - V_t)^2}$$

- Power consumption

$$P = C_{total} V_0^2 f \quad f = \frac{1}{T_{seq}}$$



- Assume the sampling frequency is the same


  
# Pipelining for Low Power (1/2)

- For M-level pipelining

- Critical path is reduced to  $1/M$
- The capacitance is also reduced to  $C_{\text{charge}}/M$
- The supply voltage can be reduced to  $\beta V_0$ , and the propagation delay remains unchanged



# Pipelining for Low Power (2/2)

- Power consumption:

$$P_{pip} = C_{total} \beta^2 V_0^2 f = \beta^2 P_{seq}$$

- How about the parameter  $\beta$  ?

$$T_{seq} = \frac{C_{charge} V_0}{k(V_0 - V_t)^2}$$

||

$$T_{pip} = \frac{\frac{C_{charge}}{M} \beta V_0}{k(\beta V_0 - V_t)^2}$$



$$\longrightarrow M(\beta V_0 - V_t)^2 = \beta(V_0 - V_t)^2$$

Solve this equation to get  $\beta$

# Example
  
## Parameters

- $T_M = 10$  u.t.
  - $T_A = 2$  u.t.
  - $T_{m1} = 6$  u.t.
  - $T_{m2} = 4$  u.t.
  - $C_M = 5C_A$
  - $V_t = 0.6V$
  - Normal  $V_{CC} = 5V$
- (a) New supply voltage?
  - (b) Power saving percentage?





# Answer

(a)

Origin system:  $C_{charge} = C_M + C_A = 6C_A$

Pipelined system:  $C_{charge} = C_{m1} = C_{m2} + C_A = 3C_A$

→  $50\beta^2 - 31.36\beta + 0.72 = 0$

$\beta = 0.6033$ , or  $\beta = 0.0239$

Invalid value, less than threshold voltage

$V_{pip} = \beta V_0 = 3.0165 \text{ V}$ .

(b)


$Ratio = \beta^2 = 36.4\%$ .


 
# Parallel Processing for Low Power (1/2)

- For L-parallel system

- Clock period:  $T_{seq} \rightarrow LT_{seq}$
- $C_{charge}$  remains unchanged
- $C_{total} \rightarrow LC_{total}$
- Have more time to charge the capacitance, the supply voltage can be lower  $\beta V_0$





# Parallel Processing for Low Power (2/2)

## ■ Power consumption

$$\begin{aligned} P_{par} &= (LC_{total}) (\beta V_0)^2 \frac{f}{L} \\ &= \beta^2 C_{total} V_0^2 f \\ &= \beta^2 P_{seq} \end{aligned}$$

## ■ To derive the parameter $\beta$

$$\begin{aligned} T_{seq} &= \frac{C_{charge} V_0}{k(V_0 - V_t)^2} \\ \downarrow \\ LT_{seq} &= \frac{C_{charge} \beta V_0}{k(\beta V_0 - V_t)^2} \longrightarrow L(\beta V_0 - V_t)^2 = \beta(V_0 - V_t)^2 \end{aligned}$$



# Example

## Parameters

- $T_M = 8$  u.t.
- $T_A = 1$  u.t.
- $T_{\text{sample}} = 9$  u.t.
- $C_M = 8C_A$
- $V_t = 0.45V$
- Normal  $V_{CC} = 3.3V$

■ (a) New supply voltage?

■ (b) Power saving percentage?

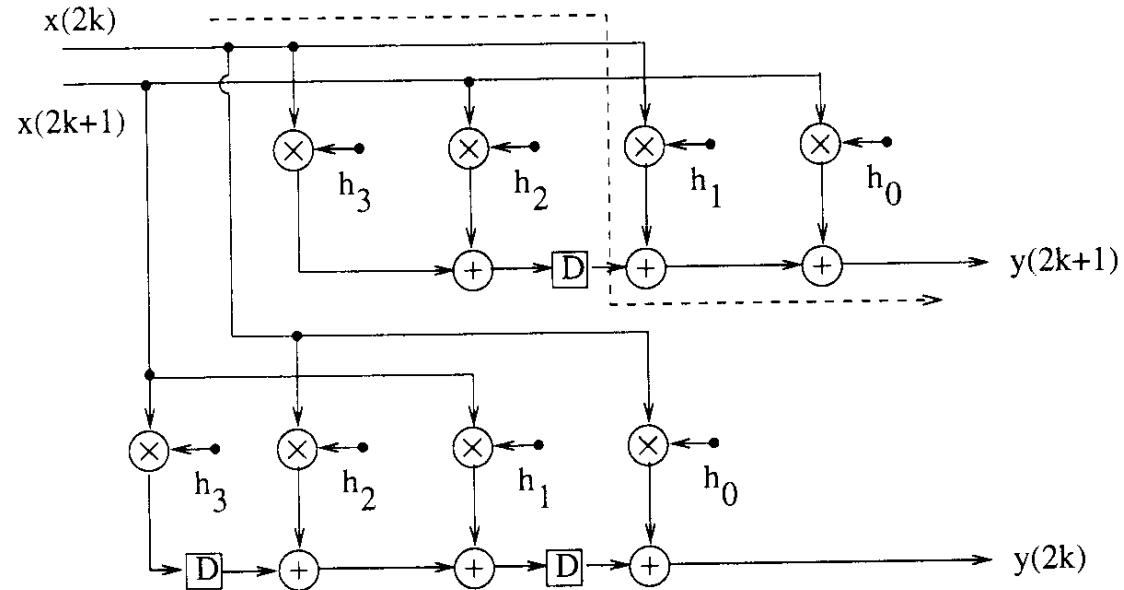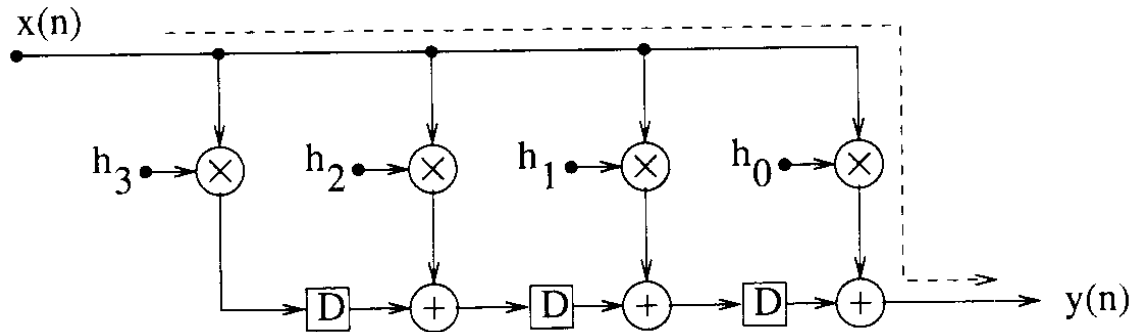

# Answer

(a)

Origin:  $C_{charge} = C_M + C_A = 9C_A$

2-parallel system:  $C_{charge} = C_M + 2C_A = 10C_A$

$$T_{seq} = \frac{9C_A V_0}{k(V_0 - V_t)^2},$$

$$5\beta(V_0 - V_t)^2 = 9(\beta V_0 - V_t)^2$$

$$T_{par} = \frac{10C_A \beta V_0}{k(\beta V_0 - V_t)^2}.$$

$$\beta = 0.6589, \text{ or } \beta = 0.0282.$$


Invalid value, less than threshold voltage

(b)

$$Ratio = \beta^2 = 43.41\%.$$



# Pipelining-Parallel for Low Power

 

$$LT_{pd} = \frac{(C_{charge}/M)\beta V_o}{k(\beta V_o - V_t)^2} = \frac{LC_{charge}V_o}{k(V_o - V_t)^2}$$

$$ML(\beta V_o - V_t)^2 = \beta(V_o - V_t)^2$$



# Unfolding (1/4)


- **Unfolding** is a transformation technique that can be applied to a DSP program to create a new program describing more than one iterations of the original program
- Unfolding factor  $J$ :  $J$  consecutive iterations
- Also called as loop unrolling

# Unfolding (2/4)

- For the DSP algorithm
  - $y(n) = ay(n-9) + x(n)$
- Replace  $n$  with  $2k$  and  $2k+1$ 
  - $y(2k) = ay(2k-9) + x(2k)$
  - $y(2k+1) = ay(2k-8) + x(2k+1)$
- It is an unfolded algorithm with  $J=2!$



# Unfolding (3/4)

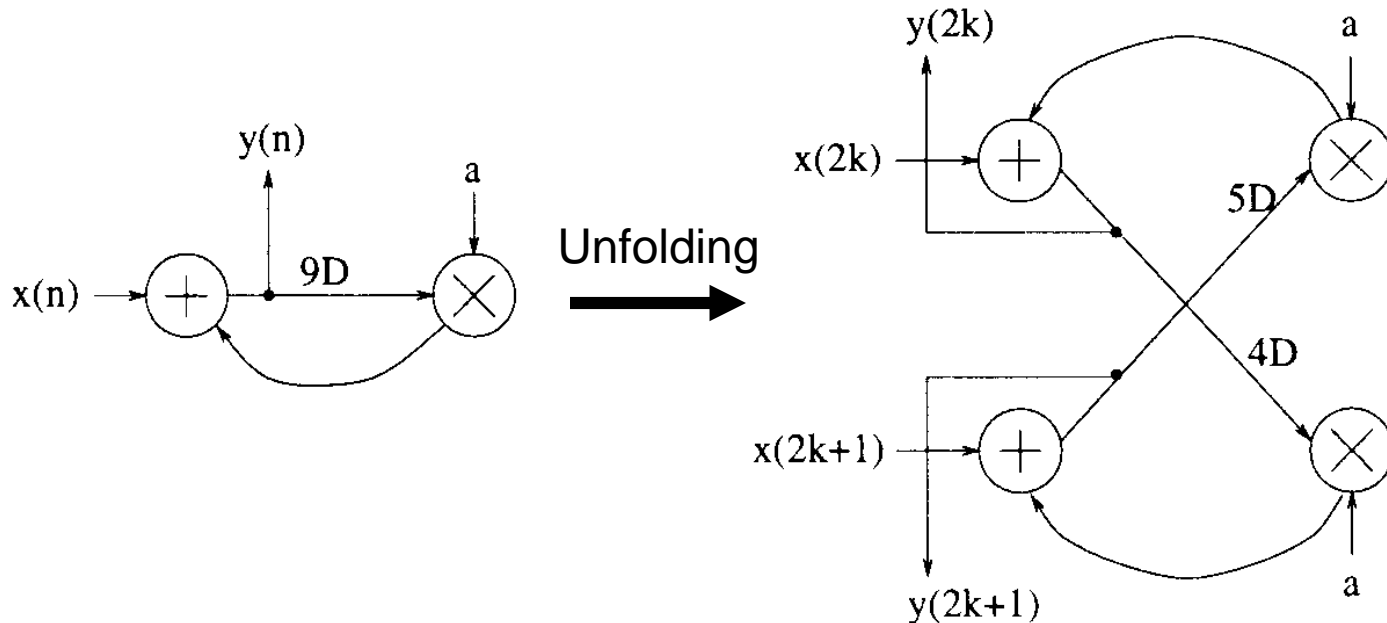

- Note that, in unfolded systems, each delay is J-slow



# Unfolding (4/4)

## ■ Applications of unfolding


- To reveal hidden concurrent so that the program can be scheduled to a smaller iteration period
- To design parallel architecture



# Folding (1/2)

- Folding transform is used to systematically determine the control circuits in DSP architectures where multiple algorithm operations are **time-multiplexed** to a single functional unit
  - Trading area for time in a DSP architecture
  - Reducing the number of hardware functional units by a factor of  $N$  at the expense of increasing the computation time by a factor of  $N$

# Folding (2/2)

 

## Scheduling

Cycle	Adder Input (left)	Adder Input (top)	System Output
0	$a(0)$	$b(0)$	—
1	$a(0) + b(0)$	$c(0)$	—
2	$a(1)$	$b(1)$	$a(0) + b(0) + c(0)$
3	$a(1) + b(1)$	$c(1)$	—
4	$a(2)$	$b(2)$	$a(1) + b(1) + c(1)$
5	$a(2) + b(2)$	$c(2)$	—



# Scheduling and Resource Allocation

- **Scheduling** and **resource allocation** are two important tasks in hardware or software synthesis of DSP systems
- Scheduling – **when** to do the process?
  - Assign every node of the DFG to a control time step, the fundamental sequencing units in synchronous systems and correspond to clock cycles
- Resource allocation – **who** to execute the process?
  - Assign operations to hardware with the goal of minimizing the amount of hardware required to implement the desired behavior



# Scheduling

## ■ Static scheduling

- If all processes are known in advance
- Perform scheduling before run time
- Most DSP algorithms are amenable to static scheduling

## ■ Dynamic scheduling

- When the process characteristics are not completely known
- Decide dynamically at run time by scheduler that runs concurrently with the program

# Design Space Exploration

- Resource v.s. sample rate for different schedules

