

Verilog Coding Guidelines

Digital Circuit Lab


TA: Po-Chen Wu

Outline

- Introduction to Verilog HDL
- Verilog Syntax
- Combinational and Sequential Logics
- Module Hierarchy
- Write Your Design
- Finite State Machine

Introduction to Verilog HDL

What is Verilog Doing...

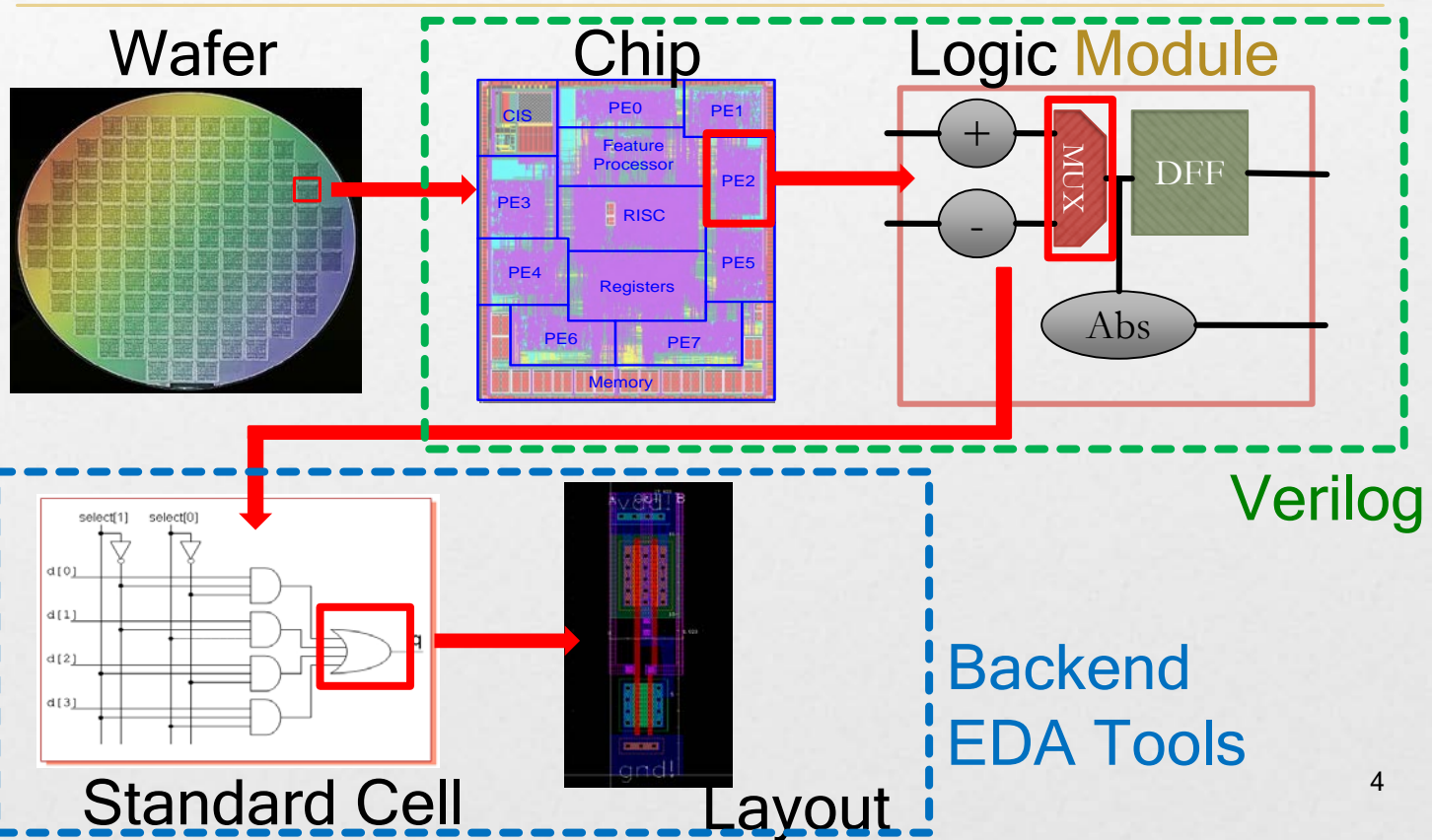


Verilog HDL

- Verilog HDL
 - Hardware Description Language
 - Programming language
 - Describes a hardware design
- Other hardware description language
 - VHDL

Represent a Circuit (1/2)


- In software

- `max_abcd = max(max(a,b), max(c,d));`

 

- In verilog ??

Represent a Circuit (2/2)

 

```
wire [3:0] a, b, c, d;  
reg [3:0] max_ab; max_cd;  
reg [3:0] max_abcd;
```

data declaration

```
always@(*) begin  
    max_ab = (a > b)? a: b;  
    max_cd = (c > d)? c: d;  
    max_abcd = (max_ab > max_cd)? max_ab: max_cd;  
end
```

logic behavior

Verilog Syntax

Blocking and Nonblocking Statements (1/2)

- Blocking Statements "="
 - A blocking statement must be executed before the execution of the statements that follow it in a sequential block.
- Nonblocking Statements "<=" "
 - Nonblocking statements allow you to schedule assignments without blocking the procedural flow.

Blocking and Nonblocking Statements (2/2)

```
module block_nonblock();
  reg a, b, c, d, e, f;

  // Blocking assignments
  initial begin
    a = #10 1'b1; // The simulator assigns 1 to a at time 10
    b = #20 1'b0; // The simulator assigns 0 to b at time 30
    c = #40 1'b1; // The simulator assigns 1 to c at time 70
  end

  // Nonblocking assignments
  initial begin
    d <= #10 1'b1; // The simulator assigns 1 to d at time 10
    e <= #20 1'b0; // The simulator assigns 0 to e at time 20
    f <= #40 1'b1; // The simulator assigns 1 to f at time 40
  end
endmodule
```

Data Types (1/3)

- **wire**
 - Used as **inputs** and **outputs** within an actual module declaration.
 - Must be driven by something, and cannot store a value without being driven.
 - Cannot be used as the left-hand side of an = or <= sign in an **always@** block.
 - The only legal type on the left-hand side of an **assign** statement.
 - Only be used to model combinational logic.

Data Types (2/3)

- **reg**
 - Can be connected to the **input** port (but not **output** port) of a module instantiation.
 - Can be used as **outputs** (but not **input**) within an actual module declaration.
 - The only legal type on the left-hand side of an **always@** (or **initial**) block = or <= sign.
 - Can be used to create registers when used in conjunction with **always@(posedge Clock)** blocks.
 - Can be used to create both **combinational** and **sequential** logic.

Data Types (3/3)

data declaration

```
wire [15:0] longdata; // 16-bit wire  
wire shortvalue; // 1-bit wire  
reg [3:0] areg; //4-bit reg
```


wire { assign longdata = areg + 88;

reg {
always@(*) begin
 if(shortvalue == 1'b1)
 areg = shortvalue + 3;
 else
 areg = shortvalue + 7;
end

logic behavior

Value Set

 - 0 - logic zero, or **false** condition
- 1 - logic one, or **true** condition
- z - **high-impedance** state
- x - **unknown** logic value - **unrealistic value in design**



Numbers

- binary('b), decimal('d), hexadecimal('h), octal('o)
- Format
 - <number>: reg data = 127;
 - '<base><number>: reg data = 'd127;
 - <width>'<base><number> → complete format

reg data =

```
659 // decimal
'o7460 // octal
4'b1001 // 4-bit binary
3'b01x // 3-bit with unknown
16'hz // 16-bit high impedance
-8'd6 // two's complement of 6
8'd-6 // illegal syntax
4af // illegal (requires 'h)
```

Case-Sensitive Control

- Suspends subsequent statement execution until any of the specified list of events occurs
 - Support **event driven simulation**
- Sensitivity list
 - `always@(... or ... or ... or...)`
 - `always@(a or b or c)`
 - `always@(*)`
 - verilog 2001, automatic list generation

Operators (1/6)

- Arithmetic operators
 - +, -, *, /, %
- Bitwise operators
 - Perform the operation one bit of a operand and its equivalent bit on the other operand to calculate one bit for the result
 - ~, &, |, ^, ~^

operator	operation
+	arithmetic addition
-	arithmetic subtraction
*	arithmetic multiplication
/	arithmetic division
%	arithmetic modulus

Arithmetic operators

operator	operation
~	bit-wise NOT
&	bit-wise AND
	bit-wise OR
^	bit-wise XOR
~^	bit-wise XNOR

Bitwise operators

Operators (2/6)

- Unary reduction operators
 - Perform the operation on each bit of the operand and get a one-bit result
 - $\&$, $\sim\&$, $|$, $\sim|$, \wedge , $\sim\wedge$

operator	operation
$\&$	unary reduction AND
$\sim\&$	unary reduction NAND
$ $	unary reduction OR
$\sim $	unary reduction NOR
\wedge	unary reduction XOR
$\sim\wedge$	unary reduction XNOR

Unary reduction operators

$\&4'b1110 \rightarrow 0$
 $\&4'b1111 \rightarrow 1$

Unary reduction AND

$|4'b0000 \rightarrow 0$
 $|4'b0001 \rightarrow 1$

Unary reduction OR

$\wedge 4'b1111 \rightarrow 0$
 $\wedge 4'b1110 \rightarrow 1$

Unary reduction XOR

Operators (3/6)

- Logical operators operate with logic values
 - Equality operators
 - Logical equality
 - ==, !=
 - Case equality
 - ===, !==
 - Logical negation
 - !
 - Logical
 - &&, ||

example

!4'b0100 → 0
!4'b0000 → 1
!4'b00z0 → x

Operators (cont.)

- logical operators

operator	operation
!	logical NOT
&&	logical AND
	logical OR
==	logical equality
!=	logical inequality
===	logical identity
!==	the inverse of ===

– logical operator operate with logic values. (non-zero is true, and zero value is false).

if(sel == 4'h03) else

Logical operators

Operators (4/6)

Operators (cont.)

- Example

opa = 0010

opb = 1100

opc = 0000

unary reduction

& opa = 0

0 & 0 & 1 & 0 = 0

logical operation

opa && opc = 0

opa = 0010 → true

opc = 0000 → false

true && false = false

bit-wise operation

opa & opb = 0000

```
  0000
& 1100
-----
  0000
```

bit-wise operation

~ opa = 1101

logical operation

opa && opb = 1

opa = 0010 → true

opb = 1100 → true

true && true = true


logical operation

! opa = 0

Operators (5/6)

- Concatenation operator

 - `{}`
- Join bits from two or more expressions together
- Very convenient
- Multiple layers



$$y = \{a[1:0], b[2], c[4,3], d[7:5]\}$$

- Replication operator

- `{n{}}`



$$y = \{\{4\{a[3]\}\}, a\}$$

Operators (6/6)

- Shift operators

- `<<, >>`

- Relational operators

- `<, <=, >=, >` if(a <= b) d = 0;
else d = 1;

- Conditional operator

- `?:` d = (a<=b) ? 0 : 1

➤ Operator precedence


Operator Precedence Rules	
<code>+ - ! ~ (unary)</code>	highest precedence
<code>* / %</code>	
<code>+ - (binary)</code>	
<code><< >></code>	
<code>< <= > >=</code>	
<code>== != === !==</code>	
<code>&</code>	
<code>^ ~</code>	
<code> </code>	
<code>&&</code>	
<code> </code>	
<code>?: (ternary operator)</code>	lowest precedence

Combinational and Sequential Logics

Two Types of Logics (1/2)



- Combinational Logics

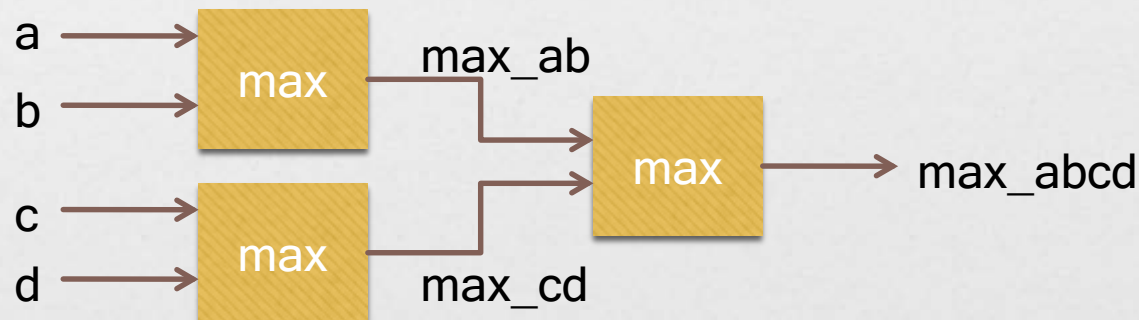- data-in \rightarrow data-out
- instant response
- fixed arrangement



Two Types of Logics (2/2)

  - Sequential Logics
 - **always** and only update at **clock edges**
 - posedge / negedge
 - **memory**



Case-Sensitive Control (1/2)

- register in sequential changes only at clock edges

```
always@(posedge clk) begin
    .....
end
```

```
always@(negedge clk) begin
    .....
end
```

- with reset signal

```
always @(posedge clk or negedge rst_n) begin
    .....
end
```

Case-Sensitive Control (2/2)

- Sequential Logics
 - `always` and only update at `clock edges`
 - `posedge` / `negedge`


```
reg [3:0] a, b; // declaration

always @(posedge clk or negedge rst_n) begin
    if(rst_n == 1'b0) begin //registers
        a <= 4'd0;
        b <= 4'd0;
    end
    else begin
        a <= next_a;
        b <= next_b;
    end
end
```

The Use of Sequential Circuits?

- Temporal storage (memory)
- Split long computation lines
 - timing issue
 - divide circuits into independent stages
 - work at the same time !!
- Combinational logics handle the **computation**
- Sequential logics **store** inter-stage temporal data


Sequential and Combinational Logics

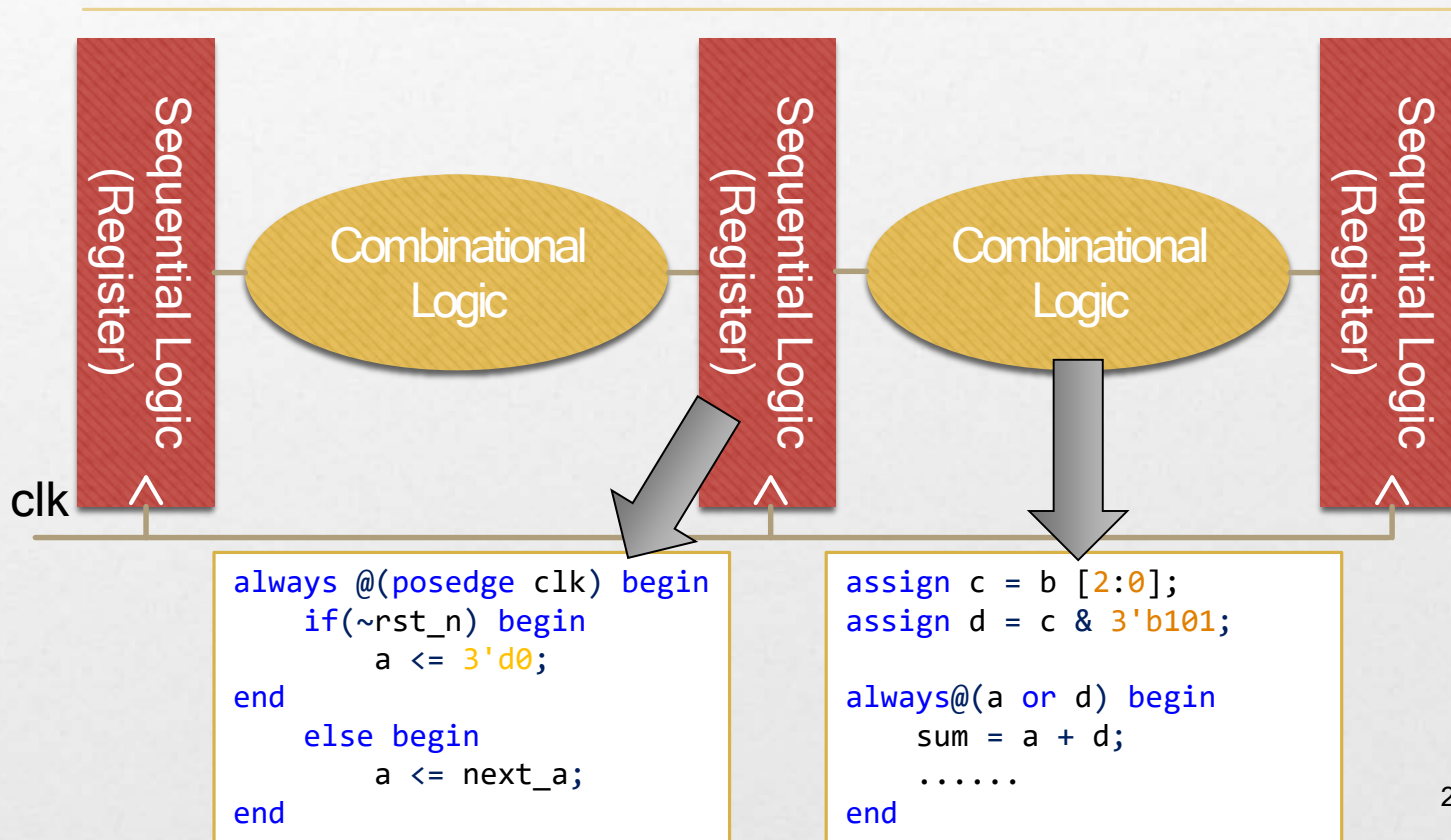

Sequential Circuit (1/3)

- Synchronous reset

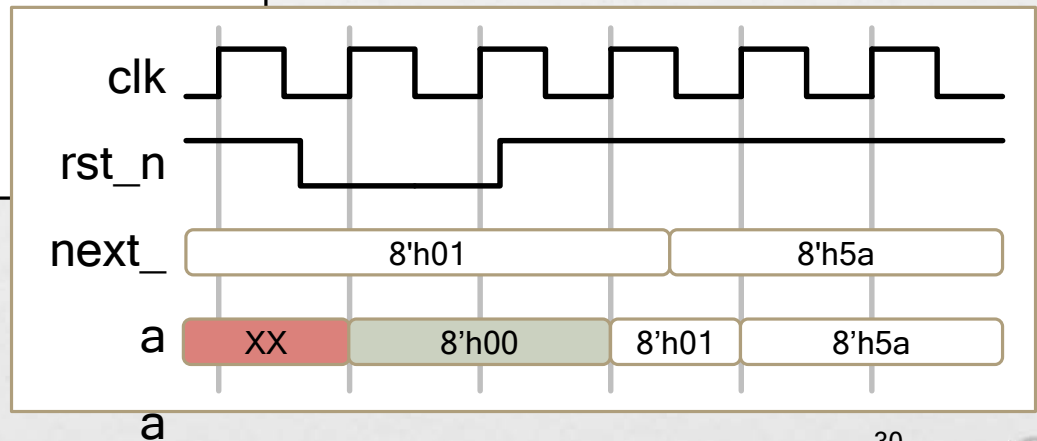
```
always @(posedge clk) begin
    if(~rst_n) begin
        a <= 8'd0;
    end
    else begin
        a <= next_a;
    end
end
```



Sequential Circuit (2/3)

- Asynchronous reset
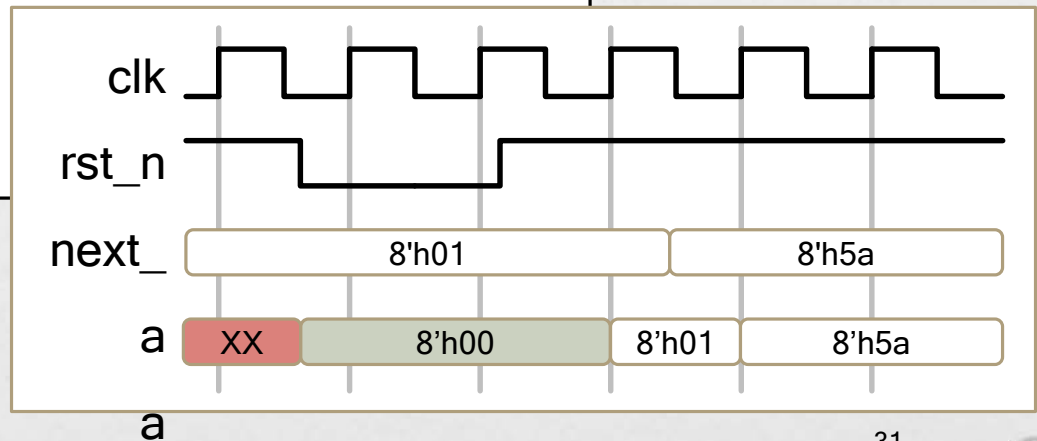
```
always @(posedge clk or negedge rst_n) begin
    if(~rst_n) begin
        a <= 8'd0;
    end
    else begin
        a <= next_a;
    end
end
```



Sequential Circuit (3/3)


Synchronous reset	Pros	<ul style="list-style-type: none">• Easy to synthesize, just another synchronous input to the design
	Cons	<ul style="list-style-type: none">• Require a free-running clock, especially at power-up, for reset to occur
Asynchronous reset	Pros	<ul style="list-style-type: none">• Does not require a free-running clock• Uses separate input on FF, so it does not affect FF data timing
	Cons	<ul style="list-style-type: none">• Harder to implement, usually a tree of buffers is inserted at P&R• Makes static timing analysis and cycle-based simulation more difficult, and can make the automatic insertion of test structures more difficult

Prefer


Module Hierarchy

What is a Module?

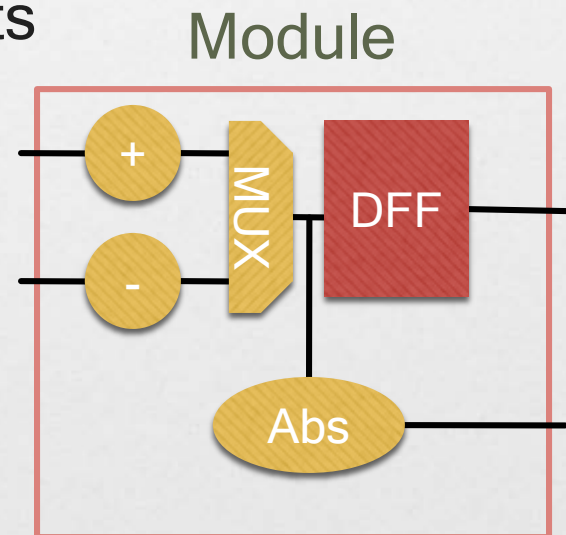- Group circuits into meaningful building blocks
- Combine highly-related circuits
- Leave simple i/o interface
- Easier to reuse / maintain



A Module

 

```
module maxab(clk,rst_n,a,b,maxab);  
input clk;  
input rst_n;  
input [3:0] a;  
input [3:0] b;  
output [3:0] maxab;
```

module port
definition

```
reg [3:0] maxab;  
wire [3:0] next_maxab;
```

wire, reg
declaration

```
assign next_maxab = (a>b)? a: b;
```

combinational logics

```
always@(posedge clk or negedge  
rst_n) begin  
    if (rst_n == 1'b0) begin  
        maxab <= 4'd0;  
    end  
    else begin  
        maxab <= next_maxab;  
    end  
end  
endmodule
```


sequential logics

ending your module!

Connection Between Modules

(1/2)


- Where you "cut" your design.

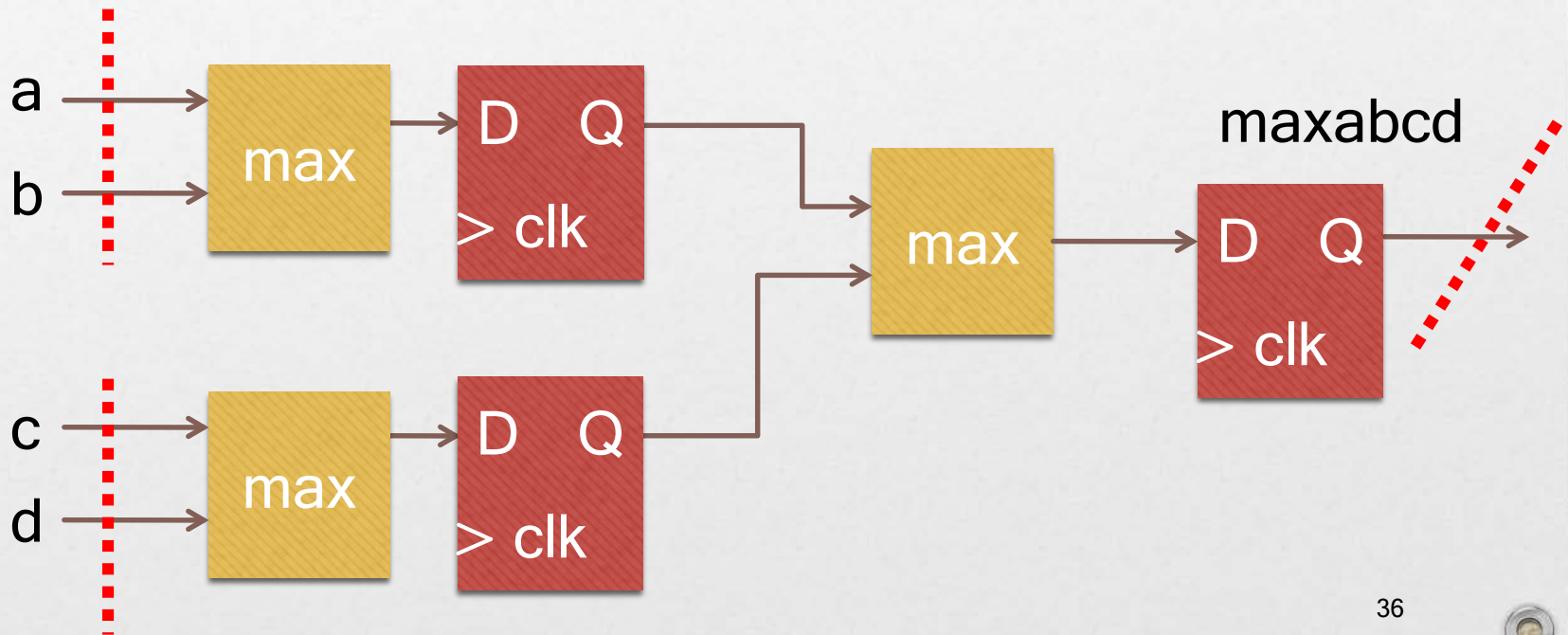

Connection Between Modules

(2/2)

- Where you "cut" your design.

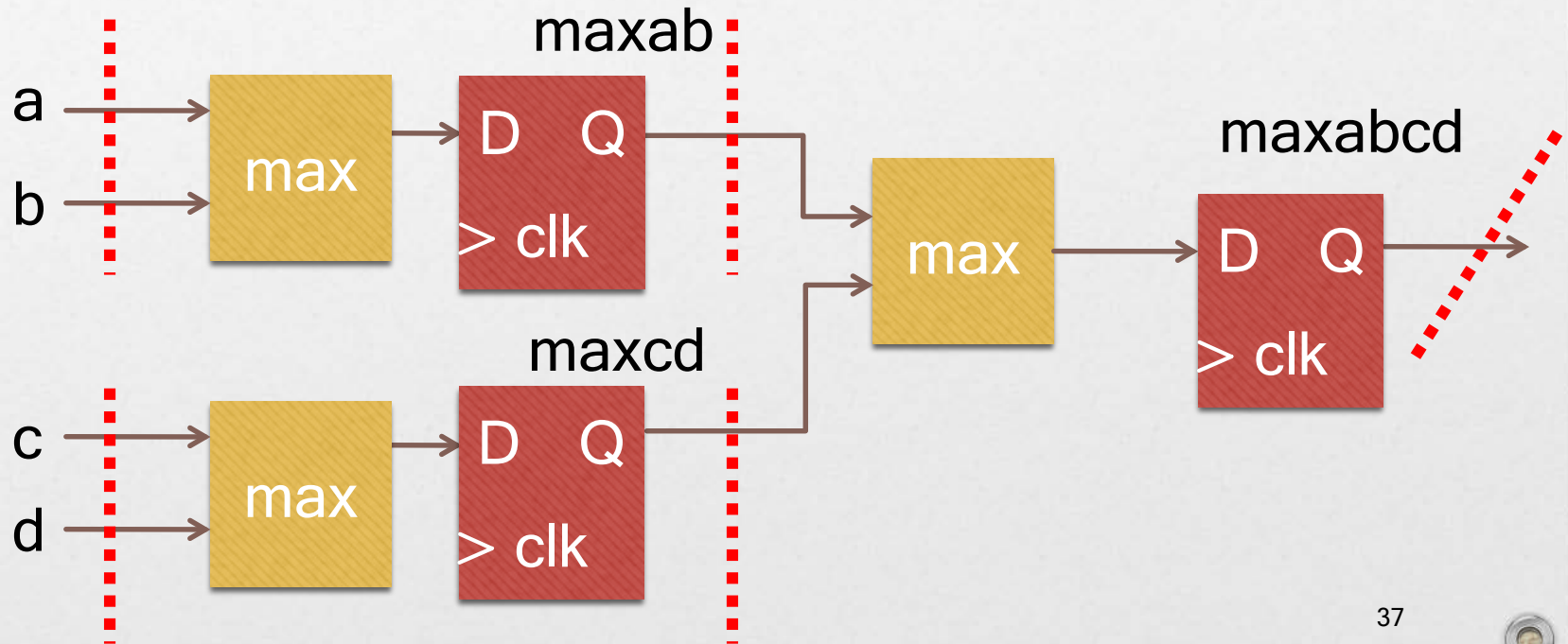


Module Instantiation

- Build a module by smaller modules

```
module maxabcd(clk,rst_n,a,b,c,d,maxabcd);  
input clk;  
input rst_n;  
input [3:0] a, b, c, d;  
output [3:0] maxabcd;  
  
wire [3:0] maxab, maxcd;
```

```
maxab m1(.clk(clk), .rst_n(rst_n), .a(a), .b(b), .maxab(maxab));  
maxab m2(.clk(clk), .rst_n(rst_n), .a(c), .b(d), .maxab(maxcd));  
maxab m3(.clk(clk), .rst_n(rst_n), .a(maxab), .b(maxcd), .maxab(maxabcd));
```

```
endmodule
```

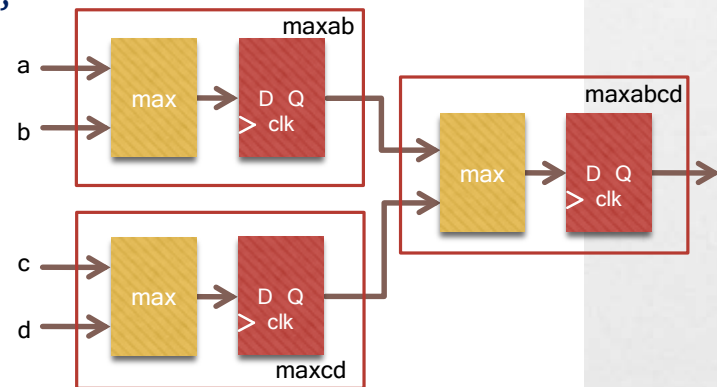

Write Your Design

Use Parameters (1/2)

- Build a module by smaller modules

```
`define INST_WakeUp 0
`define INST_GoToSleep 1
`define BUS_WIDTH 64
input [`BUS_WIDTH-1:0] databus;
case (instruction)
    `INST_WakeUp:
    ...
    `INST_GoToSleep:
    ...
endcase
```


Use Parameters (2/2)

- Use **parameter** for reusable modules

```
parameter [4:0] FA_BitSize = 8;  
reg [FA_BitSize-1:0] = datain;
```

- Use **localparam** for inner-module variables


```
localparam FSM_StateSize = 5;  
localparam [FSM_StateSize-1:0] FSM_Idle = 5'd0;
```

Finite State Machine

Finite State Machine (1/2)

- Synchronous (i.e. clocked) finite state machines (FSMs) have widespread application in digital systems
 - **Controllers** in computational units and processors.
- Synchronous FSMs are characterized by
 - A finite number of states
 - Clock-driven state transitions.

Finite State Machine (2/2)

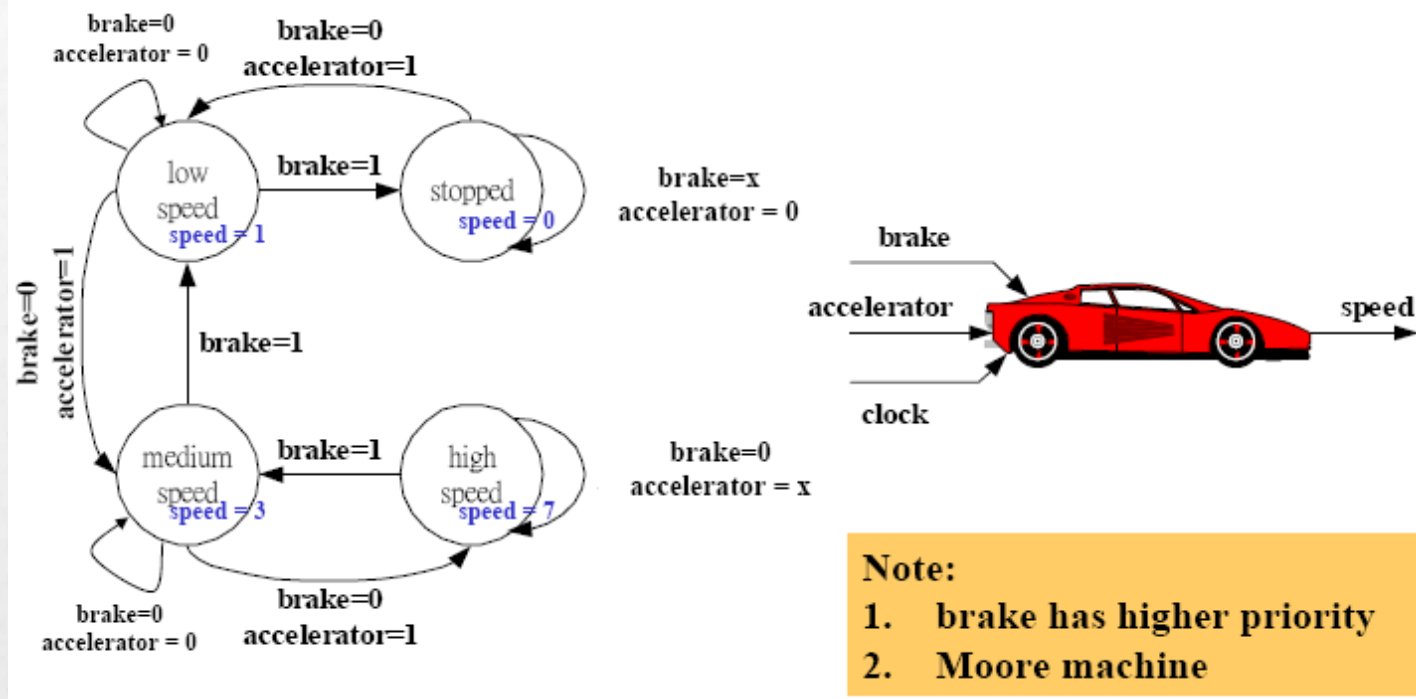

Elements of FSM (1/2)


- Memory elements (ME)
 - Memorize current state (CS)
 - Usually consist of FF or latch
 - N-bit FF have 2^N possible states
- Next-state logic (NL)
 - Combinational logic
 - Produce next state
 - Based on current state (CS) and input (X)

Elements of FSM (2/2)

- Output logic (OL)
 - Combinational logic
 - Produce outputs (Z)
 - Based on current state (Moore)
 - Based on current state and input (Mealy)


Moore Machine

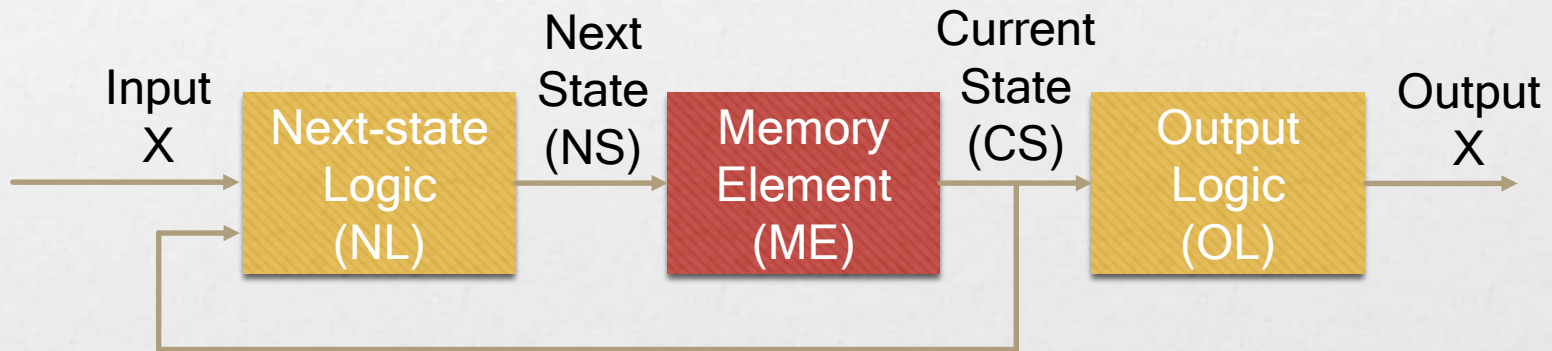- Output is function of CS only
 - Not function of inputs



Mealy Machine

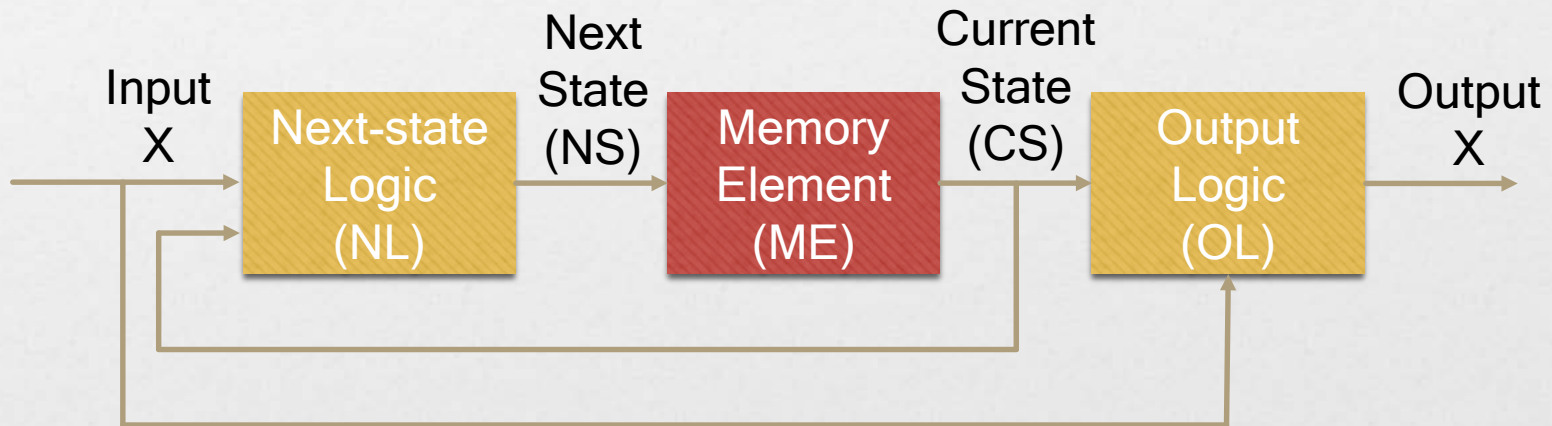- Output is function of both
 - Input and current state



Modeling FSM in Verilog

- Sequential circuits
 - Memory elements of current state (CS)
- Combinational circuits
 - Next-state logic (NL)
 - Output logic (OL)

The End.

Any question?

Reference

1. "Verilog_Coding_Guideline_Basic" by members of DSP/IC Design Lab
2. <http://inst.eecs.berkeley.edu/~cs150/Documents/Nets.pdf> by Chris Fletcher, UC Berkeley
3. CIC training course : "Verilog_9807.pdf"
4. <http://www.asic-world.com/>